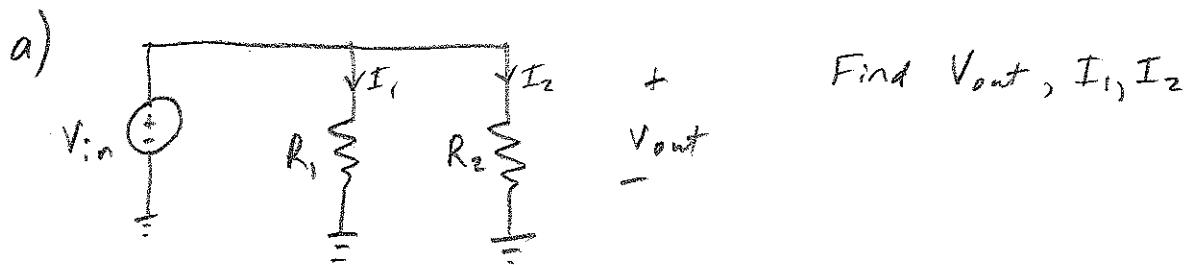


Given $R_1 = 1\text{ k}\Omega$
 $R_2 = 10\text{ k}\Omega$
 $R_3 = 10\text{ k}\Omega$
 $I_{in} = 1\text{ mA}$
 $V_{in} = 1\text{ V}$




$V_{out} = V_{in} = 1\text{ V}$ $\rightarrow R_1$ and R_2 are in parallel with the voltage source

Ohm's Law $\rightarrow V = IR$

$$\therefore I_1 = \frac{V_{out}}{R_1} = \frac{1\text{ V}}{1\text{ k}\Omega} = 1\text{ mA}$$

$$I_2 = \frac{V_{out}}{R_2} = \frac{1\text{ V}}{10\text{ k}\Omega} = 0.1\text{ mA}$$

b)

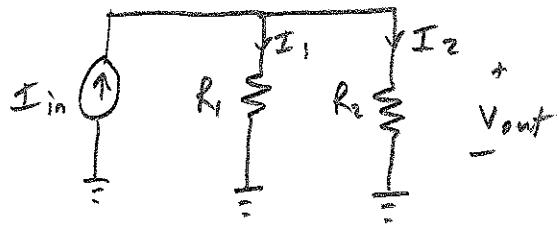Find V_{out} , I_1 , I_2 Derive the expression for $I_1 + I_2$

Current Divider Derivation

Using KCL

$$I_{in} = I_1 + I_2 = I_1 + \frac{V_{out}}{R_2}$$

$$I_1 = I_{in} - \frac{V_{out}}{R_2}$$


$$V_{out} = I_{in} R_1 // R_2 = \boxed{I_{in} \frac{R_1 R_2}{R_1 + R_2}} = \frac{(1mA)(1k\Omega)(10k\Omega)}{(1k\Omega + 10k\Omega)} =$$

$$\therefore I_1 = I_{in} - \frac{I_{in} \frac{R_1 R_2}{R_1 + R_2}}{R_2} = I_{in} \left(1 - \frac{\frac{R_1 R_2}{R_1 + R_2}}{R_2} \right) = \\ = I_{in} \left(\frac{R_1 + R_2 - R_1}{R_1 + R_2} \right)$$

$$\boxed{I_1 = I_{in} \frac{R_2}{R_1 + R_2}} = (1mA) \left(\frac{10k\Omega}{11k\Omega} \right) = 0.9091 \text{ mA}$$

$$\boxed{I_2 = I_{in} \frac{R_1}{R_1 + R_2}} = (1mA) \left(\frac{1k\Omega}{11k\Omega} \right) = 0.0909 \text{ mA}$$

This is the current divider equation set

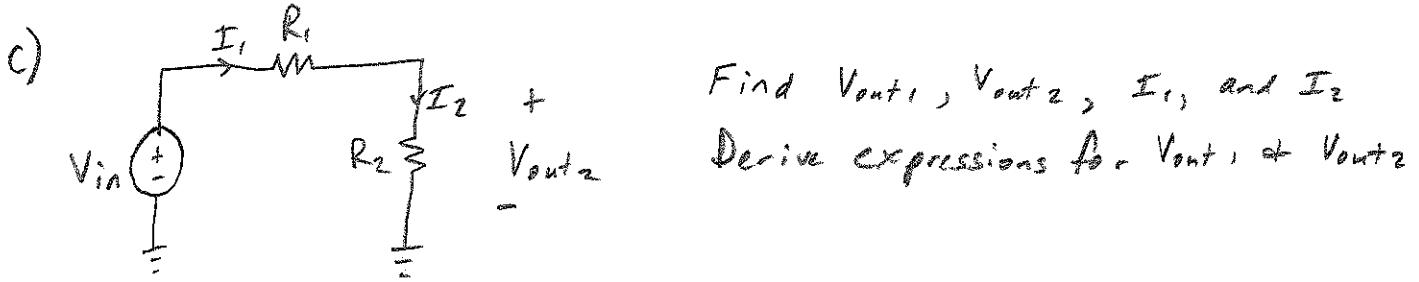

Find V_{out1} , V_{out2} , I_1 , and I_2
Derive expressions for V_{out1} & V_{out2}

Voltage Divider Derivations

For V_{out2} , use KVL

$$V_{in} = I_1 R_1 + I_2 R_2, \quad I_1 = I_2 \quad (\text{same loop})$$


$$V_{in} = I_1 R_1 + V_{out2} \quad \therefore I_1 = \frac{V_{in}}{R_1 + R_2} = \frac{1V}{1k\Omega + 10k\Omega} = 0.0909mA$$

$$\begin{aligned} V_{out2} &= V_{in} - I_1 R_1 = V_{in} - \frac{V_{in}}{R_1 + R_2} R_1 = V_{in} \left(1 - \frac{R_1}{R_1 + R_2} \right) \\ &= V_{in} \left(\frac{R_1 + R_2 - R_1}{R_1 + R_2} \right) = V_{in} \frac{R_2}{R_1 + R_2} \end{aligned}$$

$$\therefore V_{out2} = V_{in} \frac{R_2}{R_1 + R_2} = (1V) \frac{10k\Omega}{11k\Omega} = 0.9091V$$

$$V_{out1} = V_{in} \frac{R_1}{R_1 + R_2} = (1V) \frac{1k\Omega}{11k\Omega} = 0.0909V$$

This is the voltage divider equation set

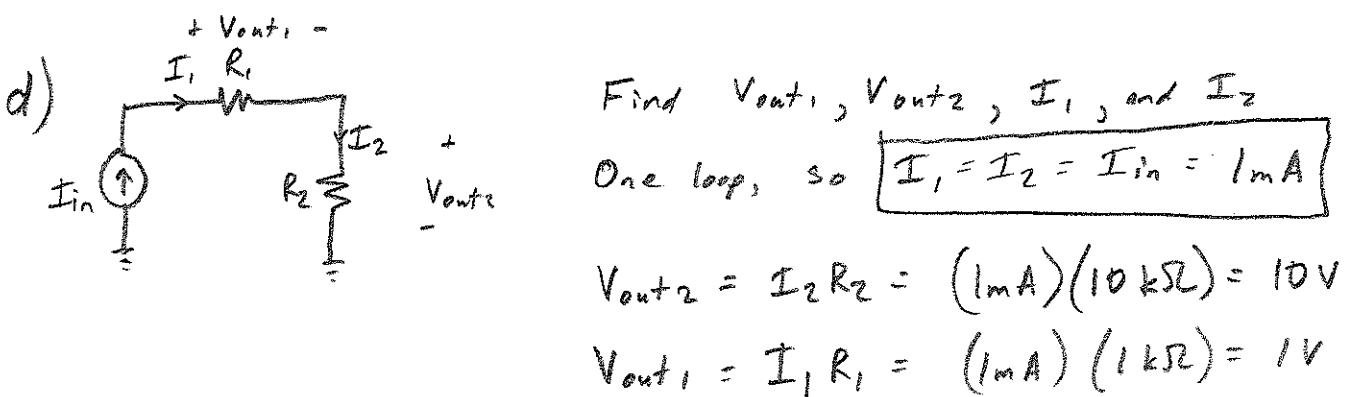


Find V_{out1} , V_{out2} , I_1 , and I_2

One loop, so $I_1 = I_2 = I_{in} = 1mA$

$$V_{out2} = I_2 R_2 = (1mA)(10k\Omega) = 10V$$

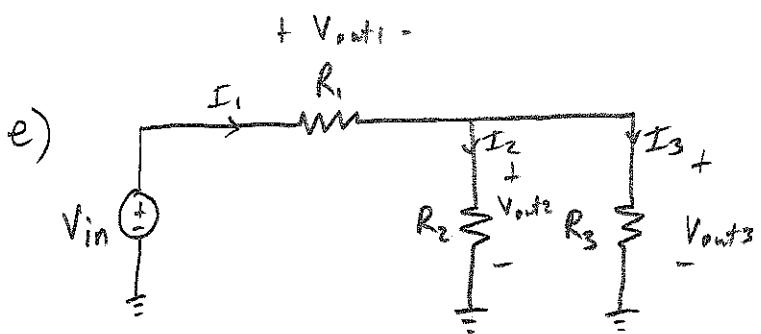
$$V_{out1} = I_1 R_1 = (1mA)(1k\Omega) = 1V$$



Find the Voltage across each resistor, and also find the current through each resistor

$$V_{out2} = V_{out} \quad (\text{in parallel})$$

$+ V_{out1}$

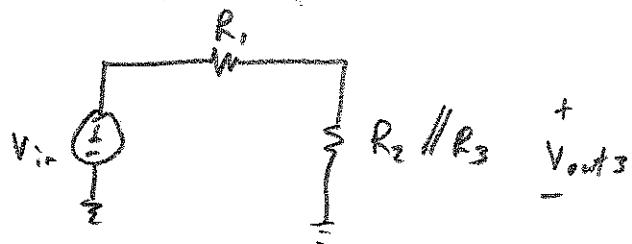

$$I_1 = \frac{V_{out1}}{R_1} = \frac{V_{in}}{R_1 + R_2 // R_3}$$

$$I_1 = \frac{1V}{1k\Omega + 5k\Omega} = 0.1667 \text{ mA}$$

$$I_2 = I_3 \quad (\text{same resistance values})$$

$$I_2 = I_1 \frac{R_3}{R_2 + R_3} \quad \text{Current Divider}$$

$$I_2 = \frac{V_{in}}{R_1 + R_2 // R_3} \frac{R_3}{R_2 + R_3} = \frac{1V}{6k\Omega} \frac{10k\Omega}{20k\Omega} = 0.0833 \text{ mA}$$


$$R_2 // R_3 = \frac{R_2 R_3}{R_2 + R_3} = 5k\Omega$$

$$\begin{aligned} V_{out1} &= V_{in} \frac{R_1}{R_1 + R_2 // R_3} \\ &= (1V) \frac{1k\Omega}{1k\Omega + 5k\Omega} = 0.1667V \end{aligned}$$

$$\begin{aligned} V_{out2} &= V_{in} \frac{R_2 // R_3}{R_1 + R_2 // R_3} = \\ &= (1V) \frac{5k\Omega}{6k\Omega} = 0.8333V \end{aligned}$$

For the following circuit, determine both Thevenin and Norton equivalents. Use the following values.
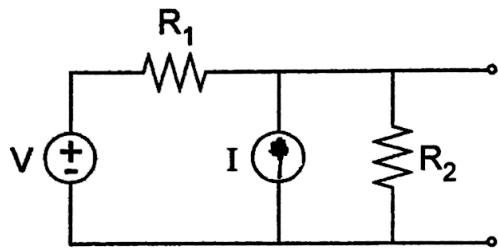
$$R_1 = 1\text{k}\Omega, R_2 = 3\text{k}\Omega, V = 2\text{V}, \text{ and } I = 1\text{mA}$$



$$\text{Find } R_{th} = R_N$$

→ Turn off all sources

$$R_{th} = R_1 \parallel R_2 = 750\Omega$$

Find the Thevenin voltage

⇒ Use Superposition

$$V \rightarrow 0\text{V}, I \rightarrow \text{OFF}$$


$$V_{th} = V \frac{R_2}{R_1 + R_2}$$

$$V \rightarrow \text{OFF}, I \rightarrow \text{ON}$$

$$V_{th} = I(R_1 \parallel R_2)$$

$$\therefore V_{th} = V \frac{R_2}{R_1 + R_2} + I(R_1 \parallel R_2) = 2.25\text{V}$$

Thevenin Equivalent

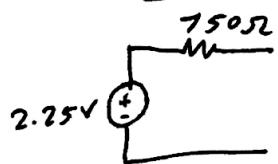

Find Norton short-circuit current

⇒ Use Superposition

$$V \rightarrow 0\text{V}, I \rightarrow \text{OFF}$$

$$I_{sc} = \frac{V}{R_1}$$

Note → R_2 is shorted out

$$\therefore I_{sc} = \frac{V}{R_1}$$

$$\Rightarrow I_N = \frac{V}{R_1} + I = 3\text{mA}$$

Norton Equivalent



$$V \rightarrow \text{OFF}, I \rightarrow \text{ON}$$

$$I_{sc} = I$$

Note → Both resistors are shorted out




$$\therefore I_{sc} = I$$

Double Check

→ Voltage at the output of the Norton Equivalent
 $(3\text{mA})(750\Omega) = 2.25\text{V}$


Agrees!

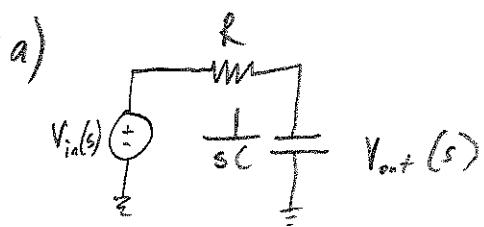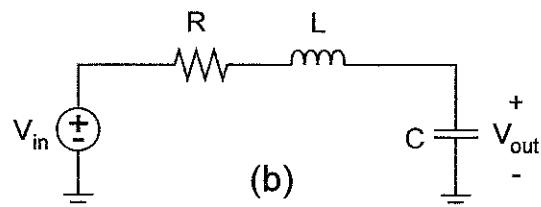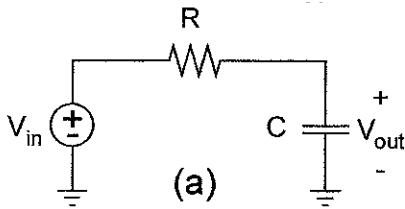Solve for the Laplace-domain transfer function of each of the following circuits.



$$V_{out}(s) = V_{in}(s) \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{RCs + 1}$$
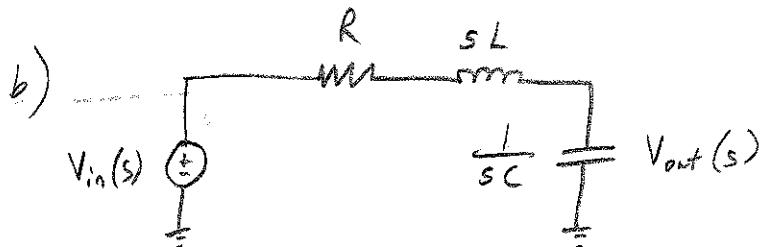
$$\therefore H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{RCs + 1}$$




$$V_{out}(s) = V_{in}(s) \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} = V_{in}(s) \frac{1}{LCs^2 + RCs + 1}$$


$$\therefore H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{LCs^2 + RCs + 1}$$

Determine an expression for both the input impedance and output impedance for the circuit shown below. Also, solve for the numerical values of the input and output impedances given that
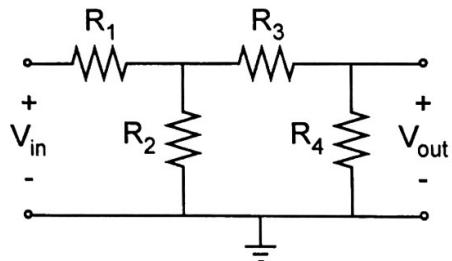
$$R_1 = 200\Omega, R_2 = 200\Omega, R_3 = 100\Omega, R_4 = 200\Omega$$



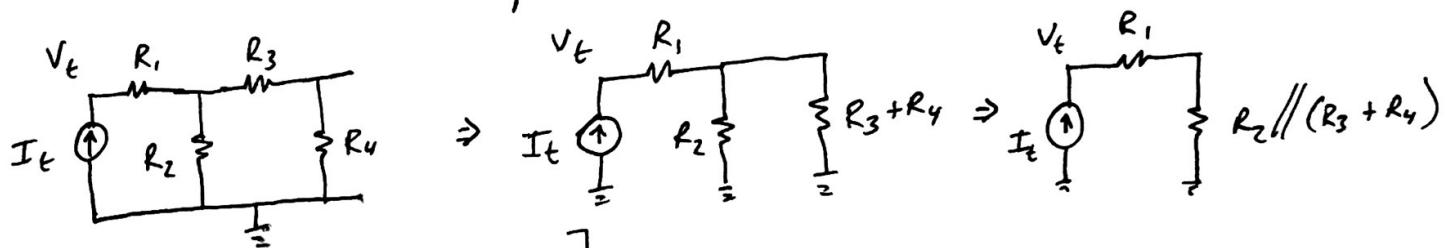
Input Impedance \rightarrow Apply a test current source at the input while the output floats. Measure the change in the input voltage



$$V_t = I_t [R_1 + R_2//(R_3+R_4)]$$

$$R_{in} = \frac{V_t}{I_t} = [R_1 + R_2//(R_3+R_4)] = 200\Omega + (200\Omega)/(300\Omega) = 320\Omega$$

Output Impedance \rightarrow Apply a test current source at the output while the input is shorted to ground. Measure the change in the output voltage $\Rightarrow R_{out} = \left. \frac{V_{out}}{I_t} \right|_{V_{in}=0}$

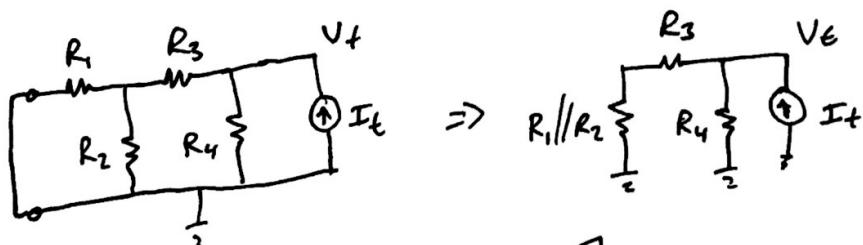

$$V_t = (I_t) [R_4//(R_3 + R_1//R_2)]$$



$$R_{out} = \left. \frac{V_t}{I_t} \right|_{V_{in}=0} = R_4//(R_3 + R_1//R_2) = (200\Omega)/(100\Omega + 200\Omega//200\Omega) =$$

$$R_{out} = 100\Omega$$

Determine an expression for both the input impedance and output impedance for the circuit shown below. Also, solve for the numerical values of the input and output impedances given that

$$R_1 = 200\Omega \text{ and } G_m = 0.1S$$
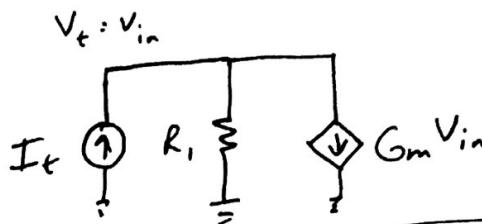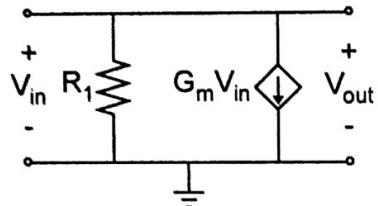
$$\underline{\text{Input Impedance}} \quad R_{in} = \frac{V_t}{I_t}$$



$$\underline{\text{KCL}} \quad I_t = \frac{V_t}{R_1} + G_m V_t$$


$$\therefore R_{in} = \frac{V_t}{I_t} = \frac{1}{\frac{1}{R_1} + G_m} = 9.52\Omega$$

Interesting point


\Rightarrow This is a voltage-controlled current source whose current is proportional to the voltage across it. This has the same properties of a resistor!

$$\text{Dependent current source symbol with V_in as the control voltage and G_m V_in as the output current.} = \frac{V_in}{Gm} \Rightarrow R_{in} = R_1 \parallel \frac{1}{Gm} = 9.52\Omega$$

$$\underline{\text{Output Impedance}} \quad R_{out} = \left. \frac{V_{out}}{I_{out}} \right|_{V_{in}=0}$$

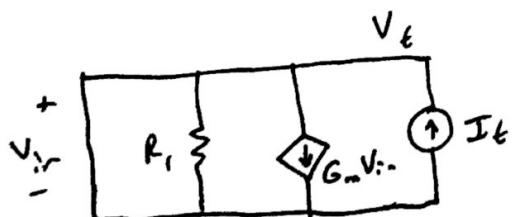

$$V_{in} = 0 \quad \therefore$$

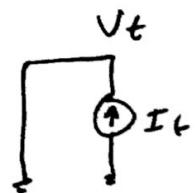

$$\therefore R_{out} = 0\Omega$$