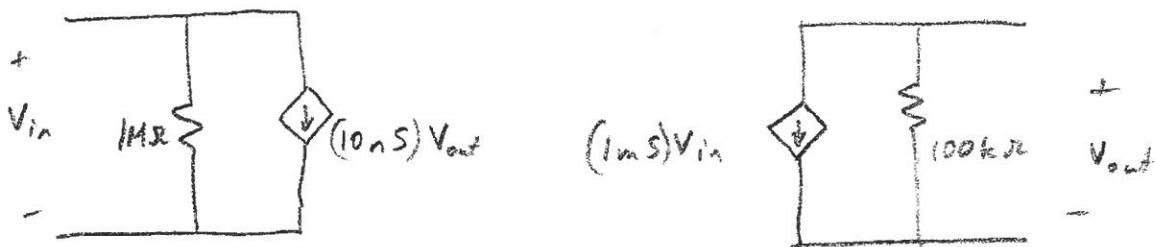


Draw the two-port amplifier model that is described below

- Forward transconductance = 1mS
- Reverse transconductance = 10nS
- Input impedance = 1MΩ
- Output impedance = 100kΩ

Determine the forward voltage gain of this amplifier.

Two-Port Model




$$\frac{V_{out}}{V_{in}} = -(1mS)(100k\Omega) = -100$$

Draw the two-port amplifier model that is described below


- $a_v = 10,000$
- $R_{in} = 10k\Omega$
- $R_{out} = 25k\Omega$

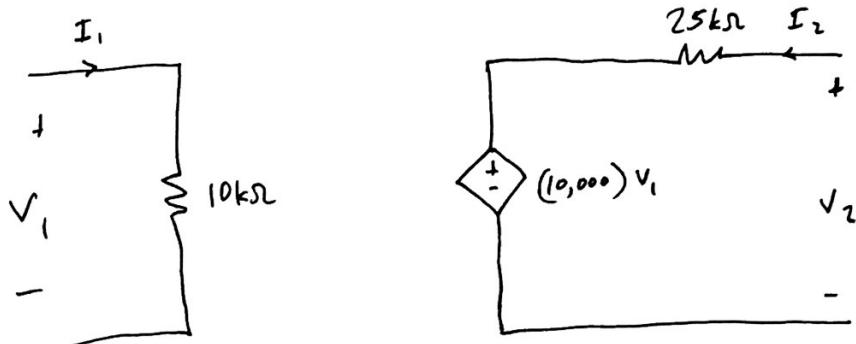Determine the unloaded gain of this amplifier. Also, redraw this two-port model with a Norton output. Determine the forward voltage gain of this amplifier.



$$\text{Unloaded gain} = a_v = 10,000$$

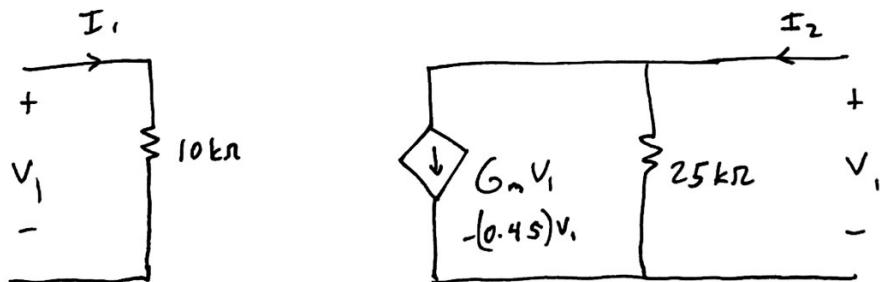Equivalent circuit with a Norton-style output




Find G_m

$$\text{Remember } a_v = -G_m R_{out}$$

$$\therefore G_m = \frac{-a_v}{R_{out}} = \frac{-10,000}{25k\Omega} = -0.4 S$$

For the following two-port models, determine the following information.

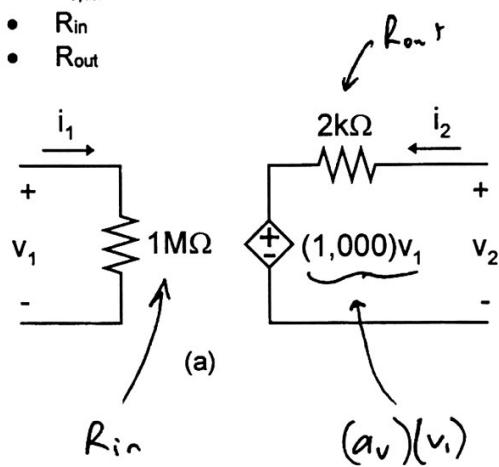- $a_{v,\text{unloaded}}$
- R_{in}
- R_{out}




$$\therefore a_{v,\text{unloaded}} = a_v = 1,000$$

$$R_{in} = 1M\Omega$$

$$R_{out} = 2k\Omega$$

$$(a_v)(v_i)$$

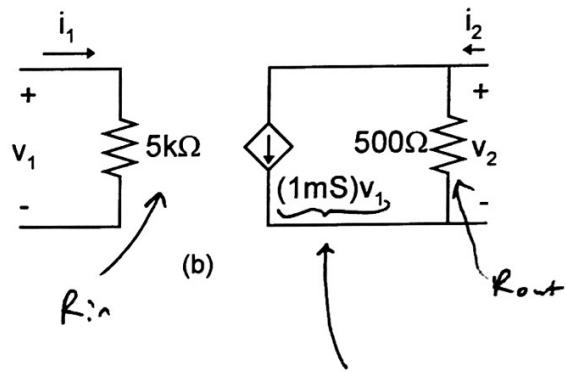

$$\xrightarrow{\text{unloaded } a_v}$$

$$a_v = -G_m R_{out} = (1mS)(500\Omega)$$


$$\therefore a_v = -0.5$$

$$R_{in} = 5k\Omega$$


$$R_{out} = 500\Omega$$

For each circuit below, the amplifier is drawn within the dotted lines. Determine the following information for each circuit.

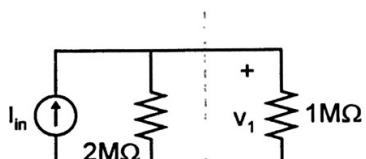
- Unloaded gain
- Overall gain (output/input), including loading effects



(a)

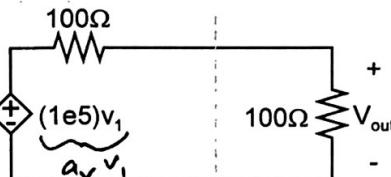

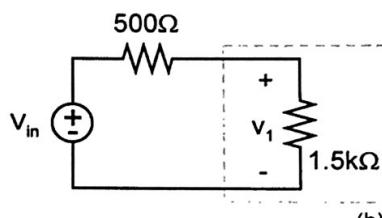a) Unloaded gain
(2-port network only)
 $a_v = 100,000$



(b)



Overall gain

$$\frac{V_{out}}{I_{in}} = \frac{V_1}{I_{in}} \cdot \frac{V_{out}}{V_1}$$

$$V_1 = (I_{in}) (2M\Omega // 1M\Omega) = (I_{in}) (667 k\Omega)$$

$$V_{out} = (a_v V_1) \frac{100\Omega}{100\Omega + 100\Omega} = 50,000 V_1$$

$a_v = 100,000$ ↑ voltage divider

$$\therefore \frac{V_{out}}{I_{in}} = \frac{(667 k\Omega)(I_{in})}{(I_{in})} \cdot \frac{(50,000)(V_1)}{V_1} = [3.335 \times 10^{-10} \Omega]$$

b) Unloaded gain (2-port network only) $\Rightarrow a_v = -G_m R_{out}$
 $a_v = - (10mS) (5k\Omega) = [-50]$


Overall Gain

$$\frac{V_{out}}{V_{in}} = \frac{V_1}{V_{in}} \cdot \frac{V_{out}}{V_1} = \left(\frac{1.5k\Omega}{1.5k\Omega + 500\Omega} \right) \left((-10mS) (5k\Omega // 1k\Omega) \right) = [-6.25]$$


Significantly
less than
the unloaded
case

For each circuit below, the amplifier is drawn within the dotted lines. Perform the following.

- Determine the unloaded voltage gain of the amplifier (i.e. ideal voltage source and load impedance)
- Determine the actual voltage gain of the amplifier (i.e. using the circuit shown below)
- Assuming we have control over the input/output impedances of the amplifier, but not the source and load, how can we design the amplifier to maximize the voltage gain
- Convert the amplifier of Part a to a voltage output (i.e. Thevenin). Convert the amplifier of Part b to a current output (i.e. Norton)

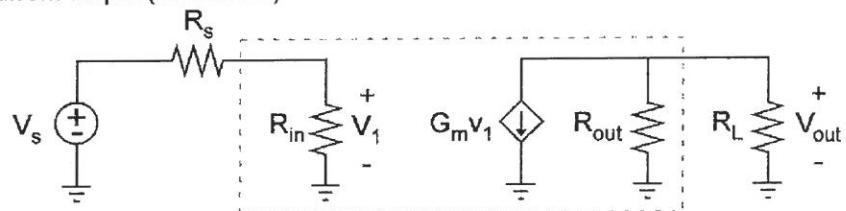

(a)

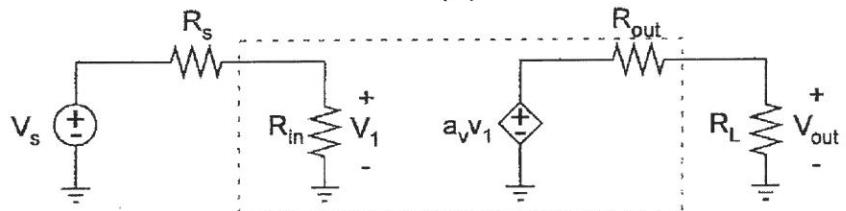

(b)

$$a) \text{ Unloaded gain} \rightarrow \frac{V_{out}}{V_{in}} = -G_m R_{out}$$


$$\begin{aligned} \text{Loaded gain} \rightarrow \frac{V_{out}}{V_s} &= \frac{V_1}{V_s} \cdot \frac{V_{out}}{V_1} = \left(\frac{R_{in}}{R_{in} + R_s} \frac{V_s}{V_1} \right) \left(\frac{-G_m R_{out} // R_L}{R_{in}} \right) = \\ &= \left(\frac{R_{in}}{R_{in} + R_s} \right) (-G_m R_{out} // R_L) = \\ &= \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(-G_m \frac{R_{out} R_L}{R_{out} + R_L} \right) \end{aligned}$$

We can maximize the voltage gain if

$$\left(\frac{R_{in}}{R_{in} + R_s} \right) \rightarrow 1 \Rightarrow \therefore R_{in} \rightarrow \infty$$


$$-G_m (R_{out} // R_L) \rightarrow -G_m R_L \quad \text{if } R_{out} \rightarrow \infty, \text{ Also increase } G_m$$

Thevenin output

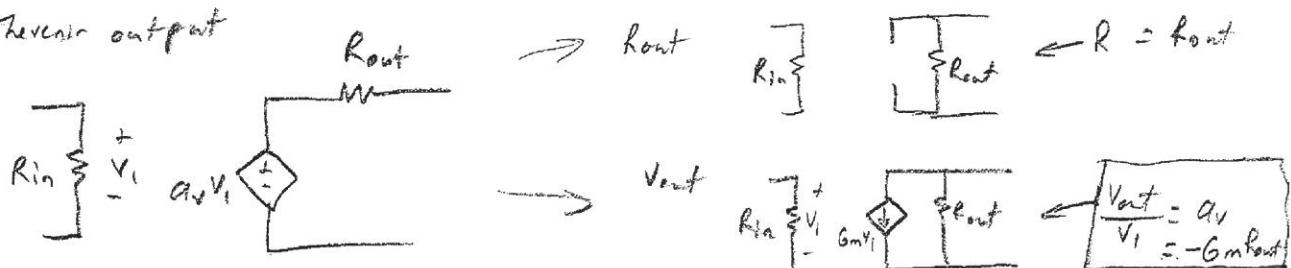

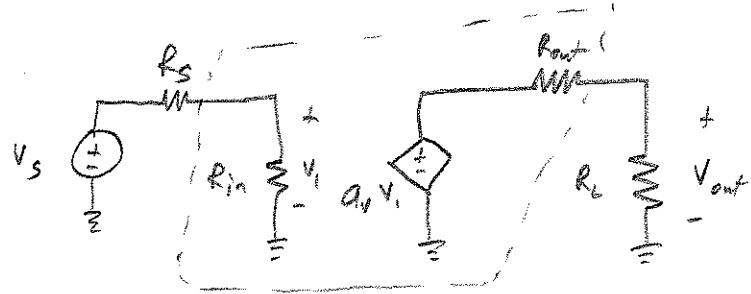b) Unloaded Gain \Rightarrow

$$\frac{V_{out}}{V_i} = \frac{a_v V_i}{V_i} = a_v$$



Loaded Gain

$$\begin{aligned} \frac{V_{out}}{V_s} &= \frac{V_i}{V_s} \cdot \frac{V_{out}}{V_i} = \left(\frac{R_{in}}{R_{in} + R_s} \cdot \frac{V_s}{V_s} \right) \left(\frac{R_L}{R_L + R_{out}} \frac{a_v V_i}{V_i} \right) = \\ &= \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(\frac{R_L}{R_L + R_{out}} a_v \right) \end{aligned}$$

To maximize the gain

$$\left(\frac{R_{in}}{R_{in} + R_s} \right) \rightarrow 1 \quad \therefore R_{in} \rightarrow \infty$$

$$\frac{R_L}{R_L + R_{out}} a_v \rightarrow \text{large} \quad \therefore a_v \text{ as large as possible} \\ R_{out} \rightarrow 0$$

Norton Output




Looking into the output of the original amplifier

set $V_i = 0$

$$6R_N = R_{out}$$

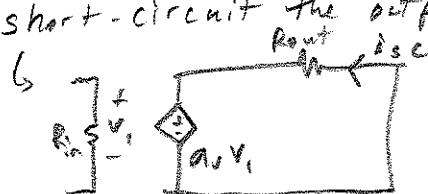short-circuit the output and measure the current



$$I_{sc} = -\frac{a_v V_i}{R_{out}} = 6m V_i$$

$$\therefore 6m = -\frac{a_v}{R_{out}}$$

A signal with a peak amplitude of $100\mu V$ needs to be amplified so that the resulting voltage has a peak amplitude of $5V$.

- Determine the voltage gain of an open-loop (i.e. no feedback) amplifier needed to perform this amplification.
- An amplifier with a gain of $a_v = 1,000,000$ is used in a negative feedback configuration to achieve the necessary overall amplification. What value of the feedback network is needed to produce the correct gain.

a) Open - Loop

$$a_v = \frac{V_{out}}{V_{in}} = \frac{5V}{100\mu V} = \boxed{50,000}$$

b) Still, an overall gain of 50,000 is needed from the closed-loop system

$$\frac{V_{out}}{V_{in}} = \frac{A}{1+AB}$$

Solve for B

$$(1+AB)\left(\frac{V_{out}}{V_{in}}\right) = A$$


$$B = \frac{\frac{A}{\frac{V_{out}}{V_{in}}} - 1}{A} = \frac{\frac{1 \times 10^6}{5 \times 10^4} - 1}{1 \times 10^4} = 0.000019$$

Sanity Check

For a large value of A, the closed loop gain is approximately $\frac{1}{B}$

$$\frac{1}{B} = 5.26 \times 10^4 \approx 5 \times 10^4 \quad \checkmark$$

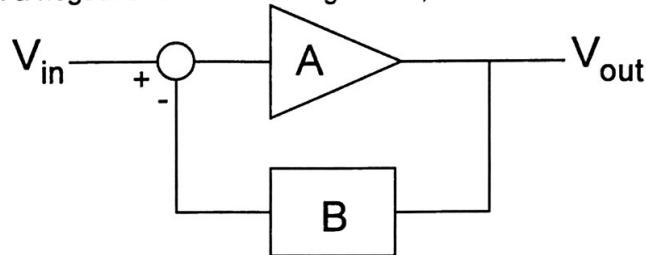An amplifier, A, is used in a negative feedback configuration, as shown below.



This amplifier has the following characteristics.

- $a_v = 10,000$
- $R_{in} = 10k\Omega$
- $R_{out} = 25k\Omega$

If the feedback network, B, has a value of 0.05, determine the following characteristics of the closed-loop system.

- a. The "loop gain" of this closed-loop system.
- b. The closed-loop gain of this system.
- c. The output voltage, if the input voltage is $v_{in} = 0.2\cos(200\pi t)$.
- d. The closed-loop input resistance.
- e. The closed-loop output resistance.

$$a) \text{ Loop Gain} = AB = (10,000)(0.05) = 500$$

$$b) \text{ Closed-Loop Gain} = \frac{A}{1 + AB} = \frac{10,000}{1 + 500} = \boxed{19.96}$$

This is close to the approximation of $\frac{1}{B} = 20$

$$c) V_{out} = (a_v)(V_{in}) = (19.96)(0.2 \cos(200\pi t)) = \boxed{3.938 \cos(200\pi t)}$$

$$d) R_{in,cl} = (R_{in,ok})(1 + AB) = (10k\Omega)(1 + 500) = \boxed{5.01 M\Omega}$$

Much bigger, which is good for reducing loading effects

$$e) R_{out,cl} = \frac{R_{out,ok}}{1 + AB} = \frac{25k\Omega}{1 + 500} = \boxed{49.95\Omega}$$

Much smaller, which is good for reducing loading effects