


Sketch the time-domain response to

$$V_{in}(t) = \sin(2\pi t)$$



$$\omega = 2\pi$$

$$\therefore f = 1 \text{ Hz}$$


$$V_A = 10$$

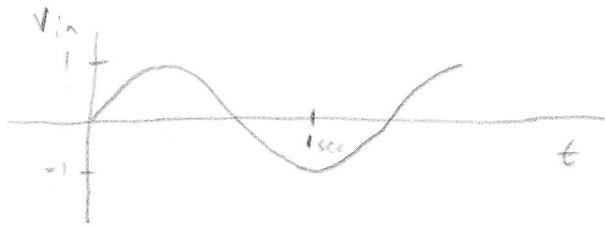


a)

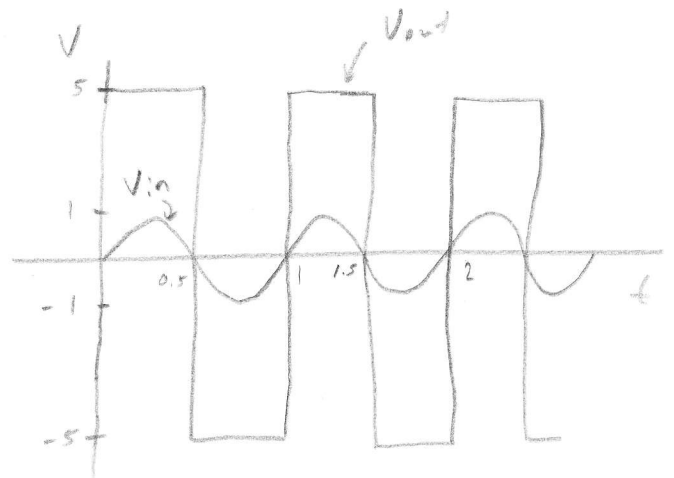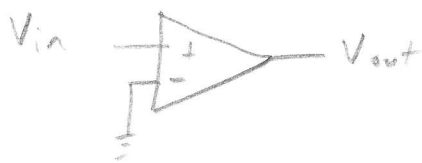


b)

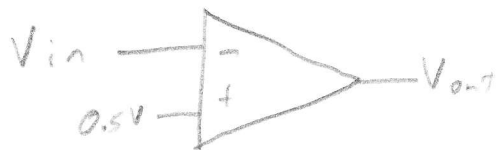

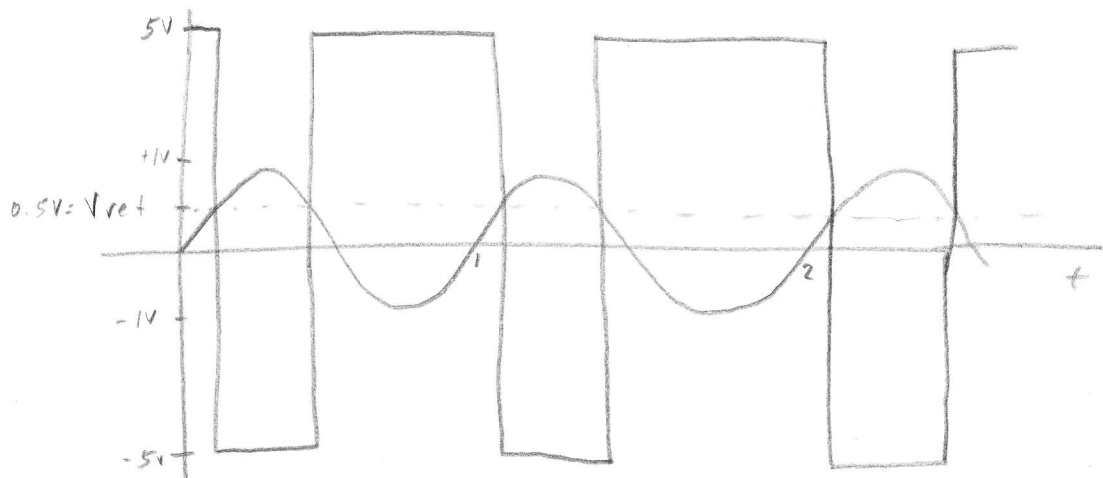When $V_{in} > 0.5 \Rightarrow V_{out} = -V_{sat}$



c)

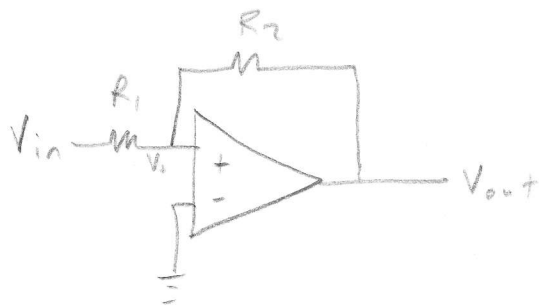

$$\frac{V_{in} - V_+}{R_1} + \frac{V_{out} - V_+}{R_2} = 0$$

$$V_{in} = -\frac{R_1}{R_2} V_{out} + \left(1 + \frac{R_1}{R_2}\right) V_+$$

Trip point when $V_+ = V_- = 0V$


And $V_{out} = \pm V_{sat}$

$$V_- = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{out}$$


$$V_+ = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{sat}$$

$$V_{in} = \mp \frac{R_1}{R_2} V_{sat} \quad \text{for the trip points}$$
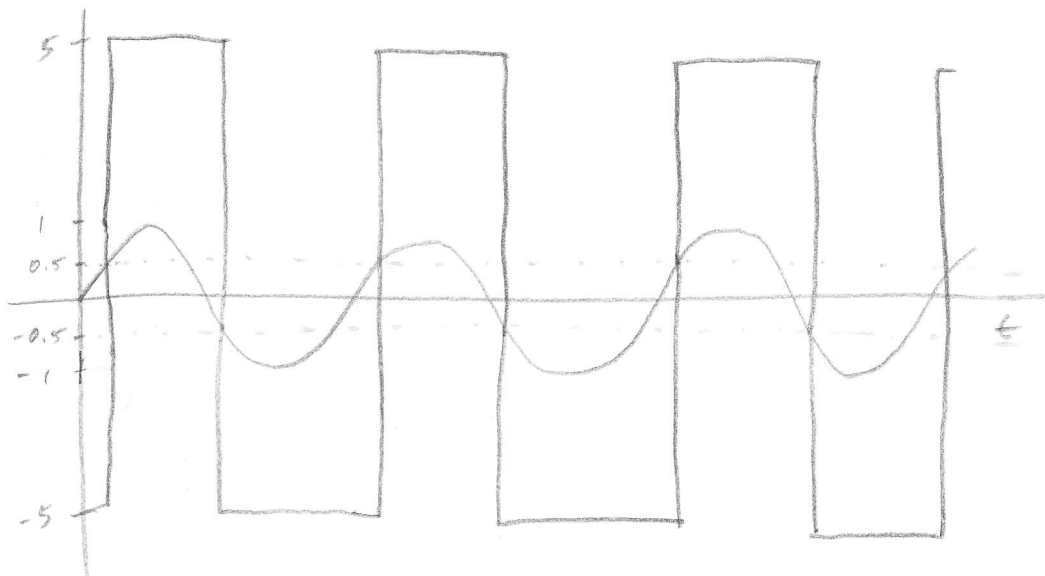
$$V_{trip} = \mp \frac{R_1}{R_2} V_{sat} = \mp \frac{1k\Omega}{10k\Omega} (5V) = \mp 0.5V$$



d)

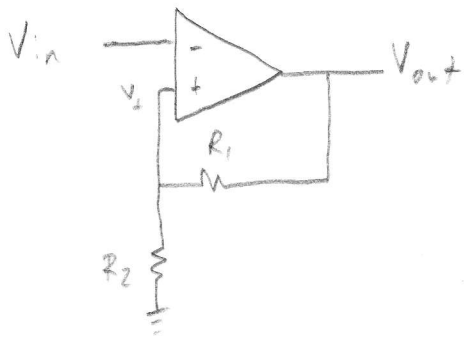


$$V_+ = V_{out} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$V_{out} = \pm V_{sat}$$



$$V_+ = \pm V_{sat} \left(\frac{R_2}{R_1 + R_2} \right)$$
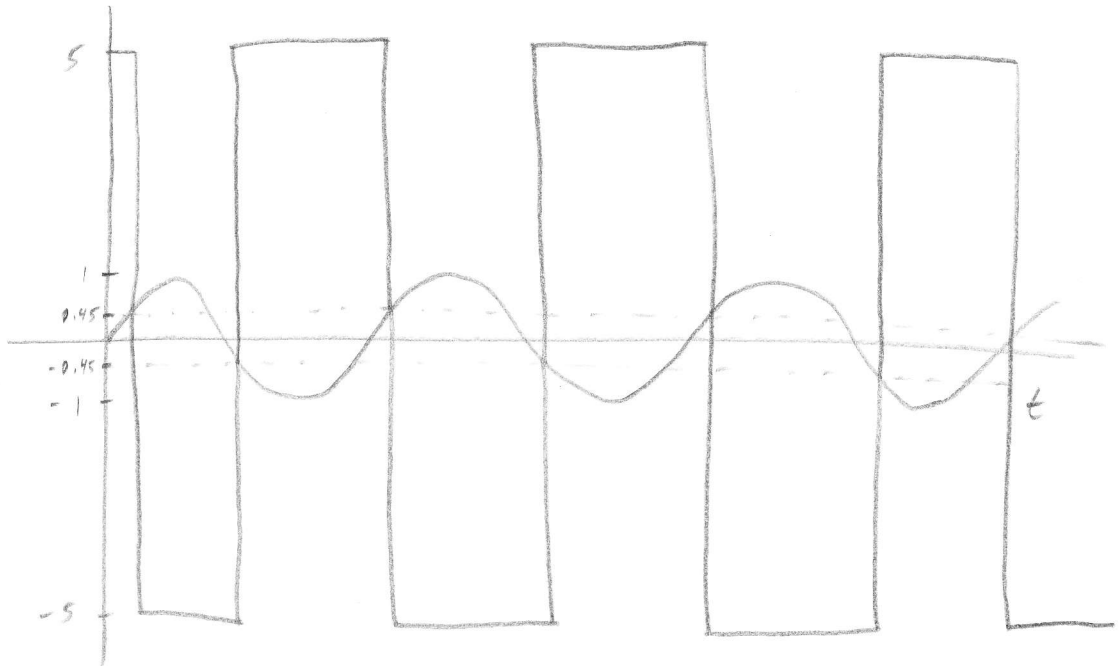
$$\begin{aligned} \therefore V_{trip} &= \pm V_{sat} \left(\frac{R_2}{R_1 + R_2} \right) = \\ &= (\pm 5V) \left(\frac{1k\Omega}{10k\Omega + 1k\Omega} \right) \\ &= \pm 0.45V \end{aligned}$$



If $V_{in} > V_+$, then $V_{out} = -V_{sat}$

e)

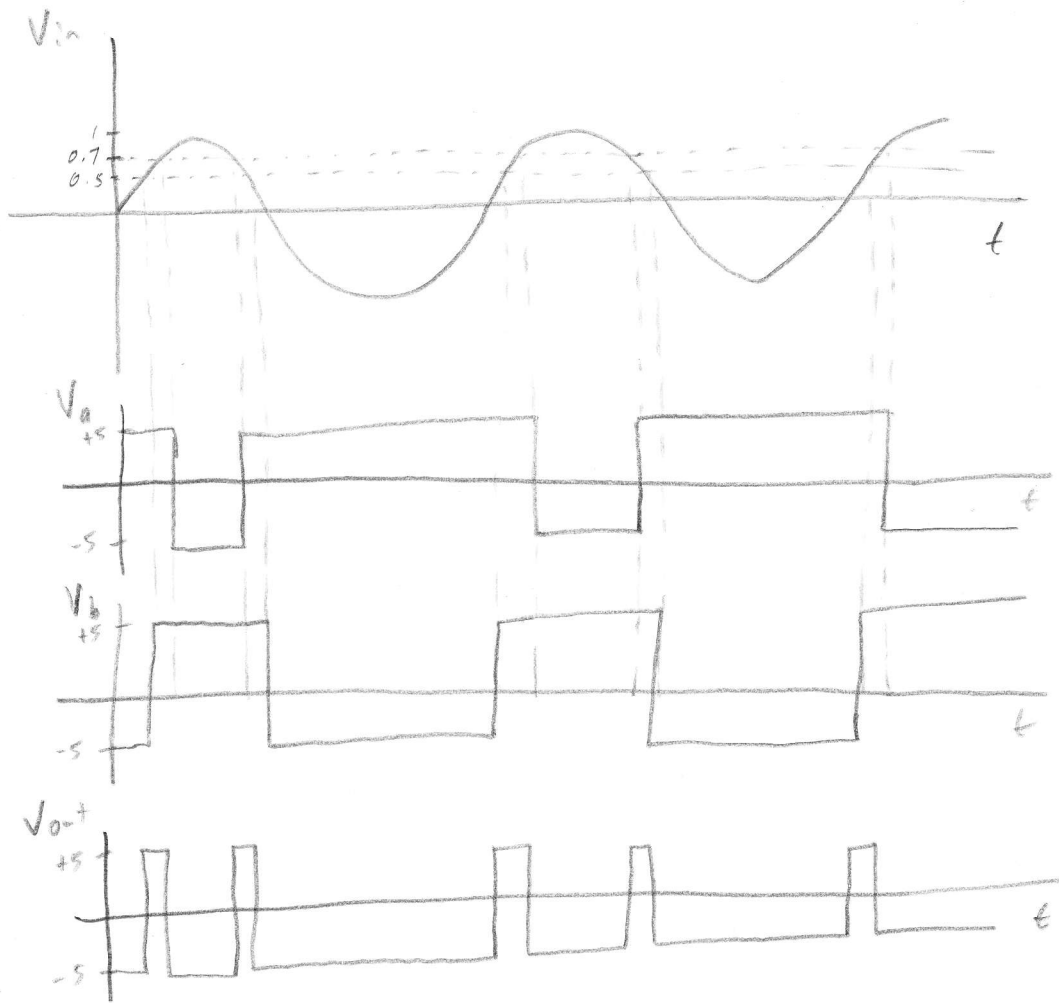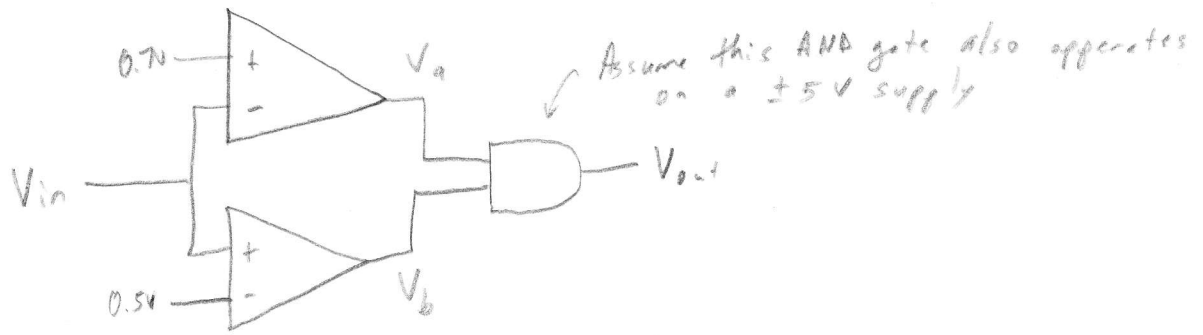


This circuit is called a Window Detector because it only ever outputs a high voltage when the input voltage is within a predefined range of voltages

Design Schmitt Triggers

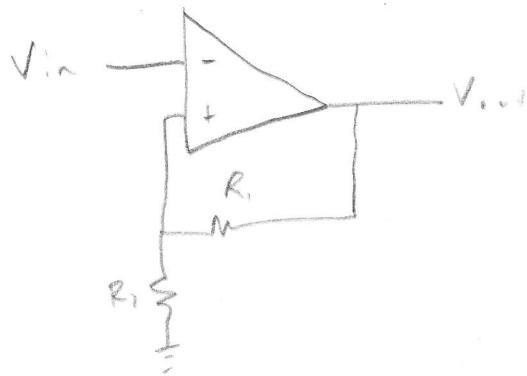a) Inverting Operation

Total hysteresis = 10 mV (± 5 mV) centered on 0V



← Inverting Schmitt Trigger
Need to solve for R_1 and R_2

$$V_{\text{trip}} = V_{\pm} = \pm V_{\text{sat}} \frac{R_2}{R_1 + R_2}$$

$$\therefore +V_{\text{trip}} = +V_{\text{sat}} \frac{R_2}{R_1 + R_2}$$

$$V_{\text{trip}} (R_1 + R_2) = V_{\text{sat}} R_2$$

$$R_1 = \frac{V_{\text{sat}}}{V_{\text{trip}}} R_2 - R_2$$

$$\therefore R_1 = \frac{5V}{5\text{mV}} R_2 - R_2 = 1000R_2 - R_2$$

$$R_1 = 999 R_2$$


Choose a value for R_2
(it can be any reasonable value)

$$\text{Let } R_2 = 100\Omega$$

$$\text{Then } R_1 = 99.9\text{ k}\Omega$$

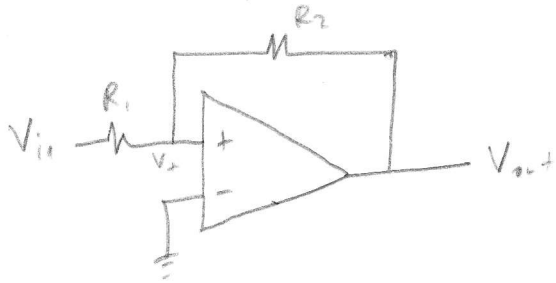b) Non-inverting Schmitt Trigger

1V total hysteresis ($\pm 0.5V$) centered at 0V



Noninverting configuration

Find values for R_1 and R_2

The output will trip when $V_+ = 0V$

$$V_{out} = \pm V_{sat}$$

$$\therefore V_{in} = \pm \frac{R_1}{R_2} V_{sat}$$

$$+V_{trip} = + \frac{R_1}{R_2} V_{sat}$$


$$\therefore R_1 = \frac{V_{trip}}{V_{sat}} R_2 = \frac{0.5V}{5V} R_2 = 0.1 R_2$$

Choose any reasonable value for R_2

Let $R_2 = 1k\Omega$
Then $R_1 = 100\Omega$

c) Design an inverting Schmitt Trigger with 100mV total hysteresis ($\pm 50\text{mV}$) centered around 1V.

Inverting Configuration

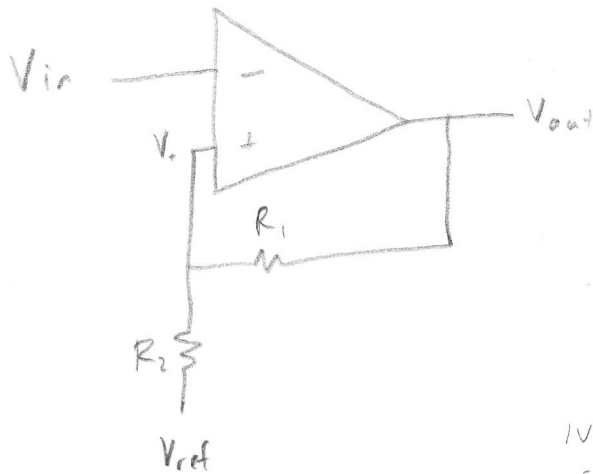

Find values for R_1 , R_2 , and V_{ref}

$$V_{+} = V_{out} \frac{R_2}{R_1 + R_2} + V_{ref} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = \pm V_{sat}$$

$$+V_{trip} = +V_{sat} \frac{R_2}{R_1 + R_2} + V_{ref} \frac{R_1}{R_1 + R_2}$$

\uparrow 5V $\underbrace{\hspace{2em}}$ $\underbrace{\hspace{2em}}$
 hysteresis portion offset

$$1\text{V} + 50\text{mV} = 1.05\text{V}$$

$$V_{offset} = V_{ref} \frac{R_1}{R_1 + R_2} = 1\text{V}$$

$$V_{ref} = \left(\frac{R_1 + R_2}{R_1} \right) V_{offset}$$

$$\Delta V_{hysteresis} = V_{sat} \frac{R_2}{R_1 + R_2} = 50\text{mV}$$

$$R_1 = \frac{V_{sat}}{\Delta V_{hysteresis}} R_2 - R_2 = \left(\frac{5\text{V}}{50\text{mV}} \right) R_2 - R_2$$

$$R_1 = 99 R_2$$

Choose $R_2 = 1\text{k}\Omega$
Then $R_1 = 99\text{k}\Omega$


$$V_{ref} = \frac{R_1 + R_2}{R_2} V_{offset} = 1.01\text{V}$$

Design a relaxation oscillator with the following specifications

Trip points at $\pm 1V$

$$C = 1\mu F$$

$$f_0 = 10 \text{ Hz}$$

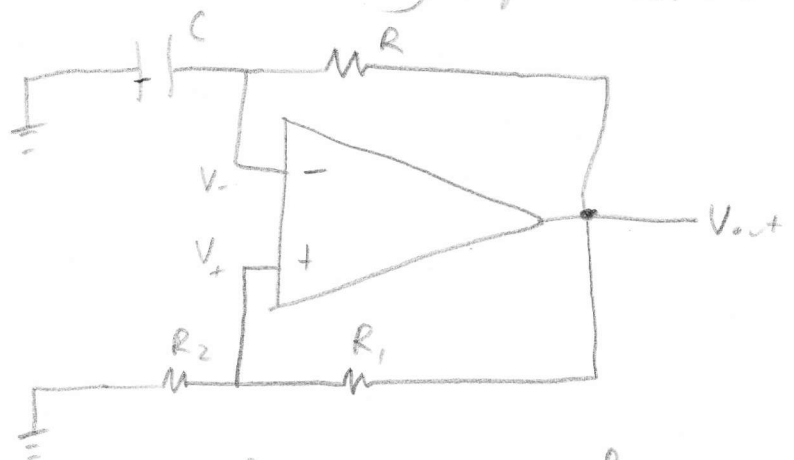

$$V_{out} = \pm V_{sat}$$

$$\text{Trip points when } V_- = V_+ = V_{out} \frac{R_2}{R_1 + R_2} = \pm V_{sat} \frac{R_2}{R_1 + R_2}$$

$$+V_{trip} = +V_{sat} \frac{R_2}{R_1 + R_2}$$

$$R_1 + R_2 = \frac{V_{sat}}{V_{trip}} R_2$$

$$R_1 = \frac{V_{sat}}{V_{trip}} R_2 - R_2 = \left(\frac{5V}{1V} \right) R_2 - R_2 = 4R_2$$

Choose $R_2 = 1k\Omega$
Then $R_1 = 4k\Omega$

$$f_0 = \frac{1}{2RC \ln\left(1 + \frac{2R_2}{R_1}\right)}$$

$$R = \frac{1}{2f_0 C \ln\left(1 + \frac{2R_2}{R_1}\right)} = \frac{1}{(2)(10\text{Hz})(1\mu F) \ln(1.5)}$$

$R = 123.32 k\Omega$