

### BJT Parameters

$$\beta=100, V^+=10V, V^-=-10V, V_{BE,ON}=0.7V, V_{CE,SAT}=0.2V, V_A=50V$$


$$I_s=10fA, k=1.38 \times 10^{-23} J/K, T=300K, q=1.602 \times 10^{-19} C$$

Determine the small-signal parameters ( $r_{\pi}$ ,  $g_m$ , and  $r_o$ ) for the following BJTs, assuming they operate in forward-active mode.

- a. npn BJT with  $I_C = 25mA$
- b. pnp BJT with  $V_{BE} = 0.71V$

$$V_T = \frac{kT}{q} = \frac{(1.38 \times 10^{-23} J/K)(300K)}{1.602 \times 10^{-19} C} \approx 25.84mV$$

A.

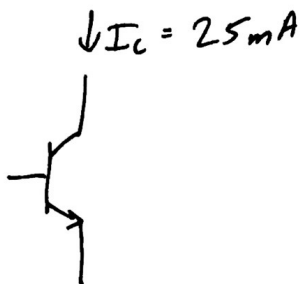

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{(100)(25.84mV)}{25mA} = 103.36 \Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{25mA}{25.84mV} = 0.9675 S$$

$$r_o = \frac{V_A}{I_C} = \frac{50V}{25mA} = 2 k\Omega$$

B.



$$I_C = I_s e^{V_{BE}/V_T} = (10fA) e^{0.71V/25.84mV} = 8.57mA$$


$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{(100)(25.84mV)}{8.57mA} = 301.52 \Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{8.57mA}{25.84mV} = 0.3317 S$$

$$r_o = \frac{V_A}{I_C} = \frac{50V}{8.57mA} = 5.8343 k\Omega$$

1

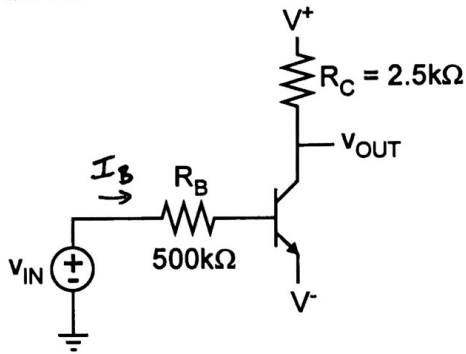For the following circuits, determine the small-signal voltage gain. You may assume the transistor operates in forward-active mode.  $V^+ = 15V$  and  $V^- = -15V$  for this problem. Let the DC value of the input voltage be  $1V$ .



$$KVL \Rightarrow V_{IN} = I_B R_B + V_{BE,ON} + V^-$$

$$I_B = \frac{V_{IN} - V_{BE,ON} - V^-}{R_B} = \frac{1V - 0.7V - (-15V)}{500k\Omega} = 30.6 \mu A$$

$$\therefore I_C = \beta I_B = 3.06 \text{ mA}$$


Note  $\rightarrow V^+ - I_C R_C = 15V - (3.06 \text{ mA})(2.5k\Omega) = 7.35V$   
 $V_{CE} = 7.35V - (-15V) > V_{CE,SAT}$   
 $\therefore$  Forward Active

$$r_{\pi} = \frac{\beta U_T}{I_C} = \frac{(100)(25.84 \text{ mV})}{3.06 \text{ mA}} = 844.44 \Omega$$


$$g_m = \frac{I_C}{U_T} = \frac{3.06 \text{ mA}}{25.84 \text{ mV}} = 118.42 \text{ mS}$$

$$r_o = \frac{V_A}{I_C} = \frac{50V}{3.06 \text{ mA}} = 16.34 \text{ k}\Omega$$

AC Equivalent + Ckt

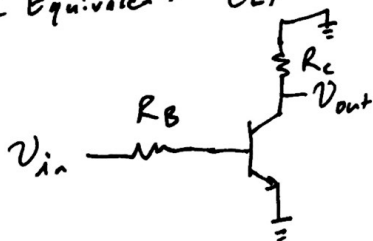

Small-Signal Model

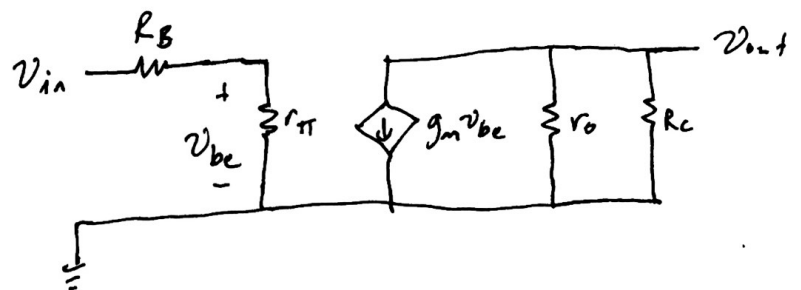



$$\frac{V_{out}}{V_{in}} = \frac{V_{be}}{V_{in}} \cdot \frac{V_{out}}{V_{be}} = \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right) \cdot \left( -g_m r_o \parallel R_C \right) =$$

$$= \left( \frac{844.44 \Omega}{844.44 \Omega + 500k\Omega} \right) \cdot \left( -(118.42 \text{ mS})(16.34 \text{ k}\Omega) \parallel (2.5 \text{ k}\Omega) \right) =$$


$$= \boxed{-0.4329}$$

Not very high gain!  $r_{\pi}$  is small

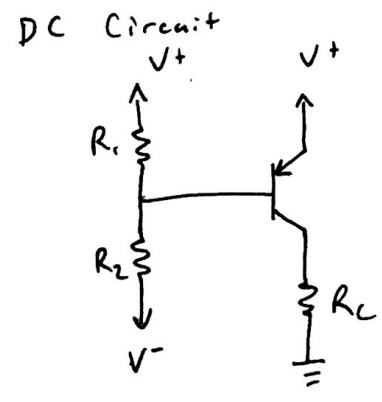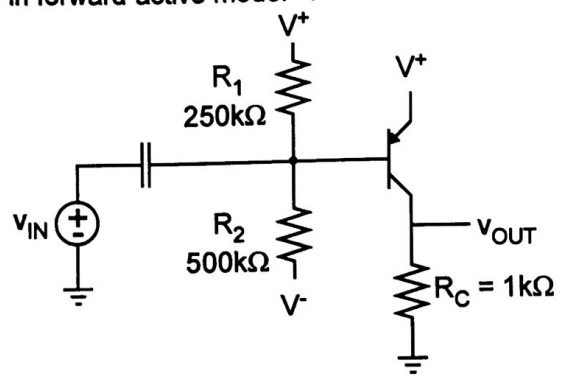For the following circuit, determine the small-signal voltage gain. You may assume the transistor operates in forward-active mode.  $V^+ = 15V$  and  $V^- = -15V$  for this problem.



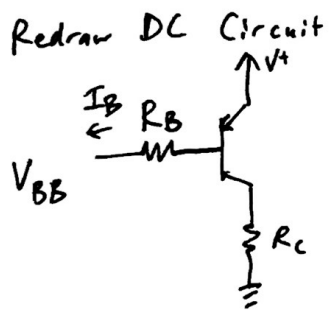Thevenin Equivalent looking out of the base  
 $R_B = R_1 \parallel R_2 = 166.67k\Omega$   
 $V_{BB} = V^+ \frac{R_2}{R_1 + R_2} + V^- \frac{R_1}{R_1 + R_2} = 5V$



KVL around E-B Loop

$$V^+ = V_{BB} + I_B R_B + V_{EB, ON}$$

$$I_B = \frac{V^+ - V_{BB} - V_{EB, ON}}{R_B} = \frac{9.3V}{166.67k\Omega} = 55.80 \mu A$$

$$\therefore I_C = \beta I_B = 5.58 mA$$

$$V_C = 0V + I_C R_C = 5.58V$$


$$V_{CE} = V^+ - V_C = 9.42V > V_{CE, SAT}$$

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{(100)(25.84mV)}{5.58mA} = 463.08\Omega$$


$$g_m = \frac{I_C}{V_T} = 215.94 mS$$

$$r_o = \frac{V_A}{I_C} = 8.96 k\Omega$$

AC Equivalent Circuit

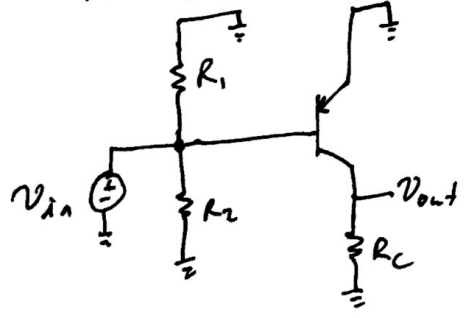


Small-Signal Model

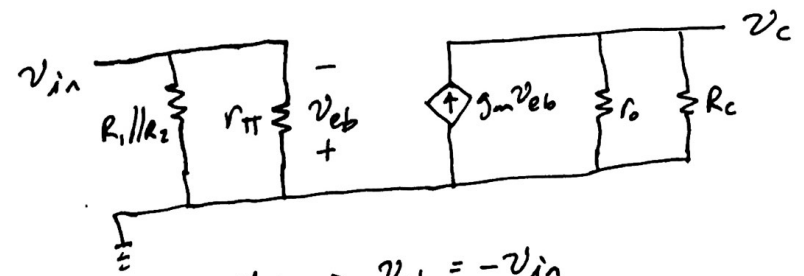

Note  $\rightarrow v_{be} = -V_{in}$   
 No voltage divider at the input


$$V_{out} = g_m v_{be} r_o \parallel R_C = -g_m V_{in} r_o \parallel R_C$$
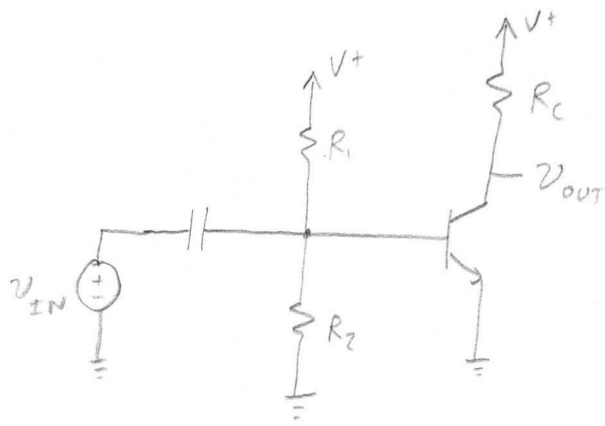
$$\therefore \frac{V_{out}}{V_{in}} = -g_m r_o \parallel R_C = \boxed{-194.26}$$



Need to find the DC bias to determine  $I_C \rightarrow$  for  $r_{\pi}, g_m, r_o$


DC Circuit

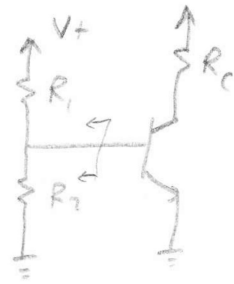

$$\text{Let } V_{BB} = V^+ \frac{R_2}{R_1 + R_2} = 2V$$

$$R_B = R_1 \parallel R_2 = 40k\Omega$$

Redraw DC Bias Circuit

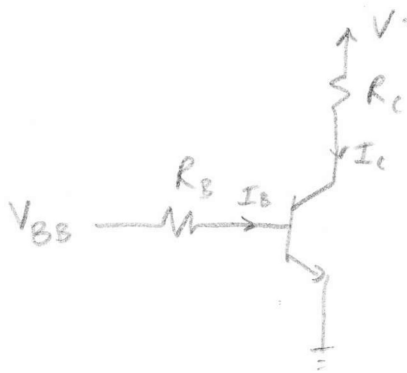

$$\text{KVL} \Rightarrow V_{BB} = I_B R_B + V_{BE, ON}$$

$$I_B = \frac{V_{BB} - V_{BE, ON}}{R_B} = 32.5 \mu A$$

$$I_C = \beta I_B = 3.25 \text{ mA (Assuming Forward Active)}$$

$$V_{CE} = V^+ - I_C R_C = 3.5 > V_{CE, SAT}$$

$\therefore$  It is, indeed, in forward active

Small-Signal Parameters


$$U_T = \frac{kT}{q} = 26 \text{ mV}$$

$$r_{\pi} = \frac{\beta U_T}{I_C} = 800 \Omega$$


$$g_m = \frac{I_C}{U_T} = 0.125 \text{ S} = 125 \text{ mS}$$

$$r_o = \frac{V_A}{I_C} = 15.4 \text{ k}\Omega$$

# AC Circuit

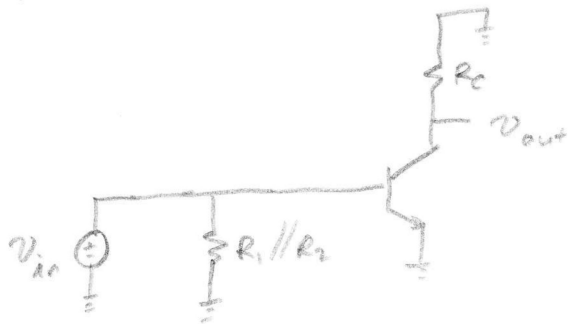

## Small-Signal Model

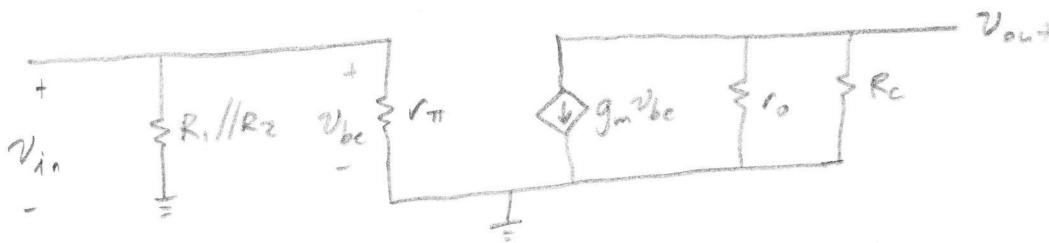

Note  $v_{be} = v_{in}$


KVL Loop

## Small-Signal Gain

$$a_v = \frac{v_{out}}{v_{in}} = -g_m r_o // R_C = -221$$

Two-Port Parameters  $\rightarrow R_{in}, R_{out}, G_m$

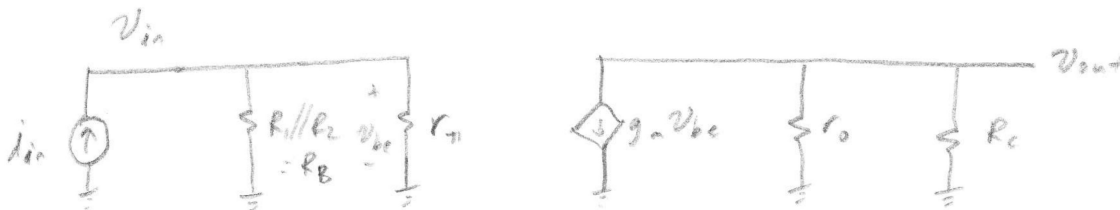
$$R_{in} = \frac{v_{in}}{i_{in}} \Rightarrow \text{Use a test current source}$$



$$v_{in} = i_{in} (R_B // r_{\pi})$$

$$R_{in} = \frac{v_{in}}{i_{in}} = R_B // r_{\pi} = 784.3 \Omega$$

$$R_{out} = \frac{v_{out}}{i_{out}} \Big|_{v_{in}=0}$$

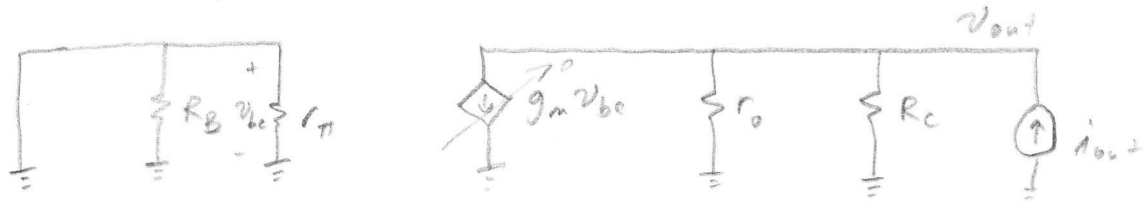


$v_{in} = AC \text{ ground}$

$$\therefore v_{be} = 0$$

$$\Rightarrow g_m v_{be} = 0$$


Resulting Circuit

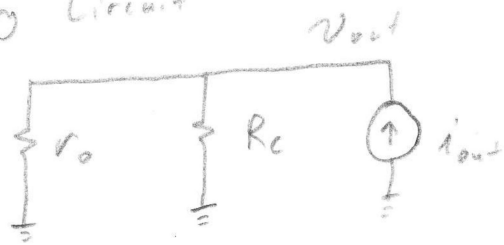

$$v_{out} = i_{out} r_o \parallel R_c$$

$$R_{out} = r_o \parallel R_c = 1.77 \text{ k}\Omega$$

$$G_m = \frac{i_{out}}{v_{in}} \Big|_{v_{out}=0}$$

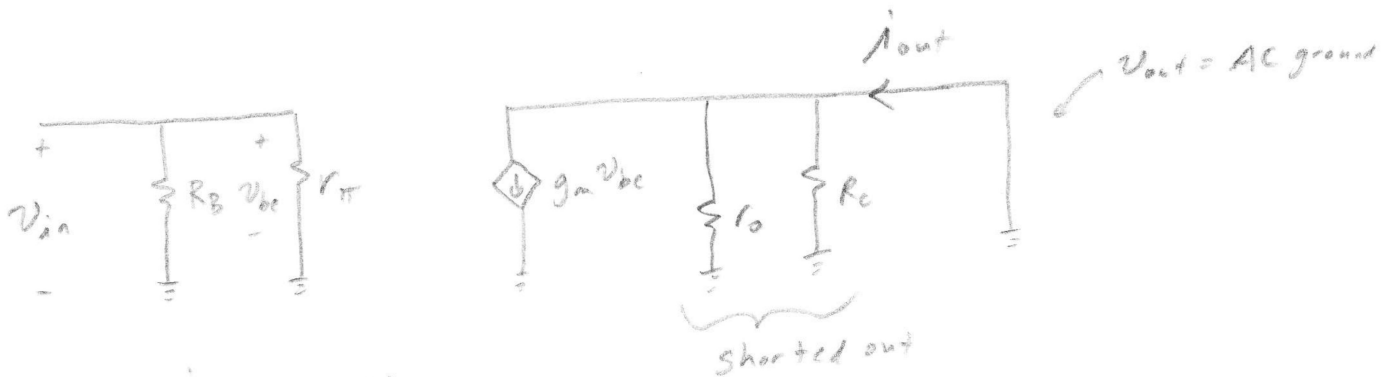

$$\therefore i_{out} = g_m v_{be} = g_m v_{in}$$


$$\Rightarrow G_m = \frac{i_{out}}{v_{in}} = g_m$$

Note

$$a_v = -G_m R_{out} = -g_m r_o \parallel R_c$$


$\Rightarrow$  Agrees with our previous solution for the gain

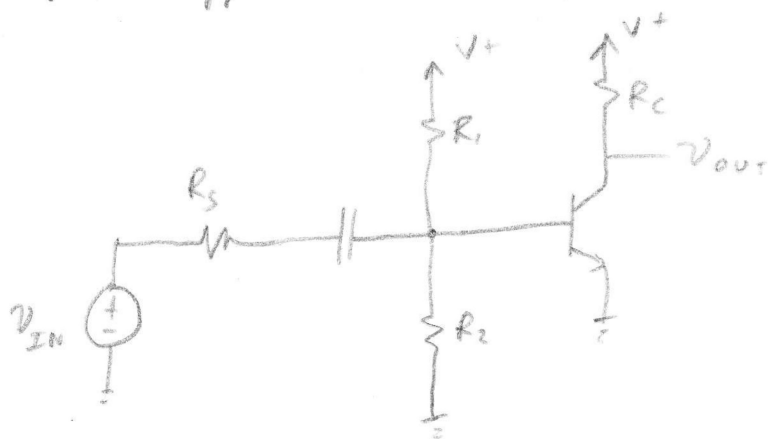What happens if the input voltage source is not ideal?



Note  $\rightarrow$  The DC circuit is exactly the same as it was previously  
 Therefore  $I_C$  is unchanged  
 $\Rightarrow r_{\pi}, r_o, g_m$  are also unchanged

### Small-Signal Model

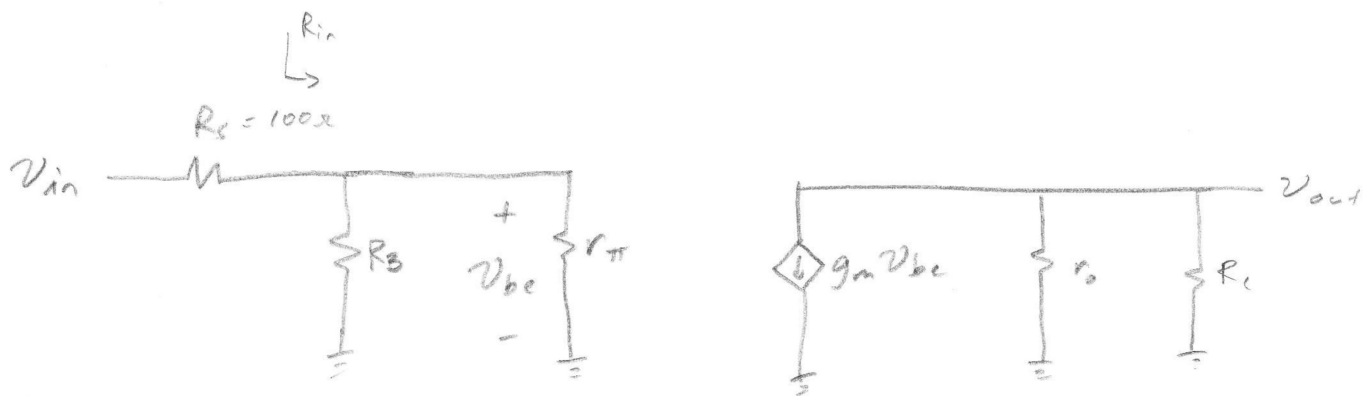

Note  $\rightarrow v_{be} = v_{in} \frac{R_B // r_{\pi}}{R_B // r_{\pi} + R_S} = 0.887 v_{in}$

$$a_v = \frac{v_{be}}{v_{in}} \cdot \frac{v_{out}}{v_{be}} = (0.887) [-g_m r_o // R_C] = -196$$

$\rightarrow$  smaller than before

$R_{out}$  is definitely unchanged

$R_{in}$  (from the right side of the voltage source) is unchanged

If you include  $R_S$ , then  $R_{in} = R_S + R_B // r_{\pi} = 843.35 \Omega$

$G_m$  (from the right side of the voltage source) is unchanged

If you include  $R_S$ , then  $G_m$  is decreased by the factor of the voltage divider (0.887)

$$G_m = (0.887)(g_m) = 0.111 \text{ S}$$