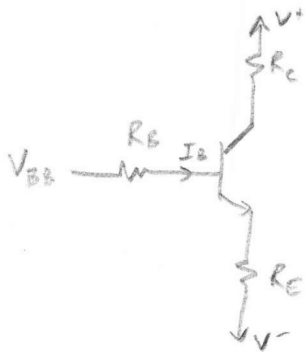


DC Bias Conditions

$$V_{BB} = V^+ \frac{R_2}{R_1 + R_2} + V^- \frac{R_1}{R_1 + R_2} = 0$$

$$R_B = R_1 \parallel R_2 = 50 \text{ k}\Omega$$

DC Circuit



$$V_{BB} = I_B R_B + V_{BE, on} + (\beta + 1) I_B R_E + V^-$$

$$I_B = \frac{V_{BB} - V_{BE, on} - V^-}{R_B + (\beta + 1) R_E} = 28.5 \mu\text{A}$$

This transistor operates in forward active (as given by the problem statement)


$$\therefore I_C = \beta I_B = 2.85 \text{ mA}$$

Small-Signal Parameters


$$r_{\pi} = \frac{\beta V_T}{I_C} = 912 \Omega$$

$$g_m = \frac{I_C}{V_T} = 0.1096 \text{ S} \quad r_o = \frac{V_A}{I_C} = 17.5 \text{ k}\Omega$$

Small-Signal Model

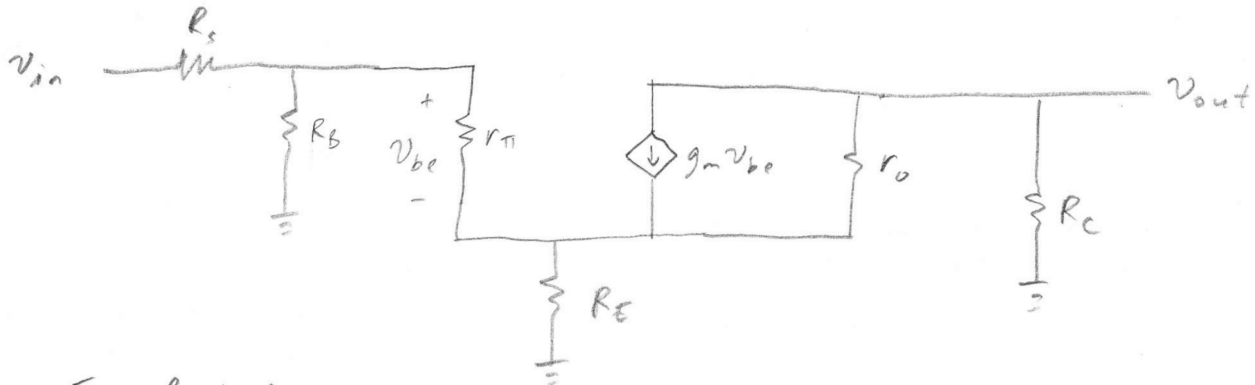

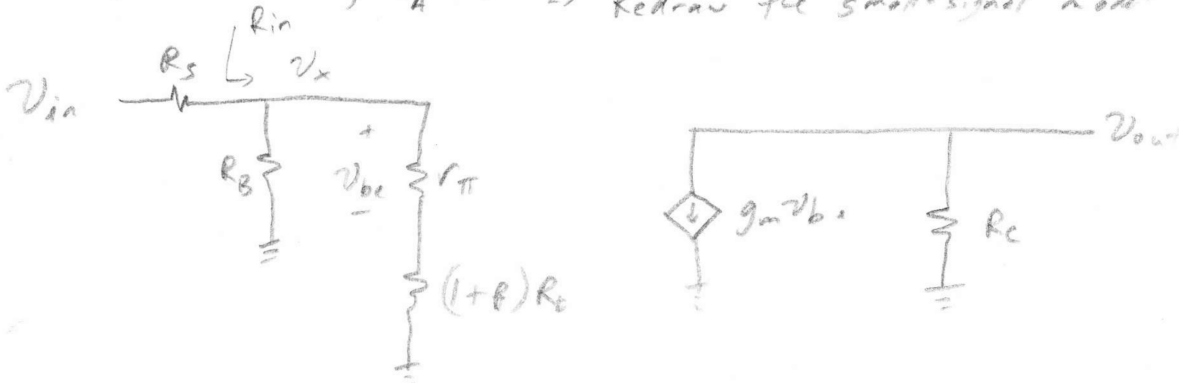For part c, $V_A \rightarrow \infty \Rightarrow$ redraw the small-signal model



$$\text{Let } R_{in} = R_B // (r_{\pi} + (1+\beta)R_E) = 33.5 \text{ k}\Omega$$

$$\therefore v_x = v_{in} \frac{R_{in}}{R_{in} + R_s} = v_{in} (0.985)$$

$$v_{be} = v_x \frac{r_{\pi}}{r_{\pi} + (1+\beta)R_E} = v_{in} \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(\frac{r_{\pi}}{r_{\pi} + (1+\beta)R_E} \right)$$


$$v_{out} = -g_m v_{be} R_C = -g_m v_{in} \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(\frac{r_{\pi}}{r_{\pi} + (1+\beta)R_E} \right) R_C$$

$$a_v = \frac{v_{out}}{v_{in}} = -g_m R_C \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(\frac{r_{\pi}}{r_{\pi} + (1+\beta)R_E} \right) = -1.93$$

Note, this is close to the approximation

$$a_v = -\frac{R_C}{R_E} = -2$$

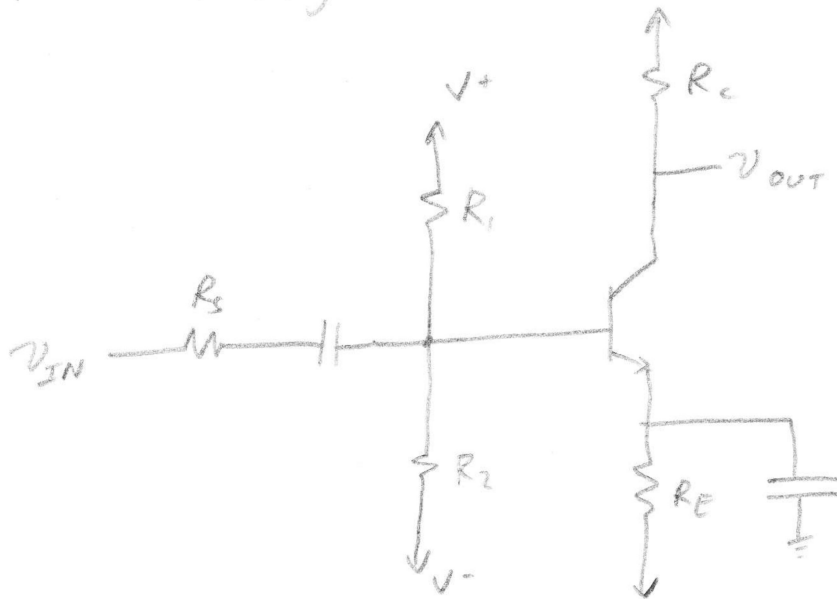How does the gain differ for the following circuit?




Note

The DC bias remains the same

$$\therefore I_C = 2.85 \text{ mA}$$

Also, r_π, g_m, r_o remain the same

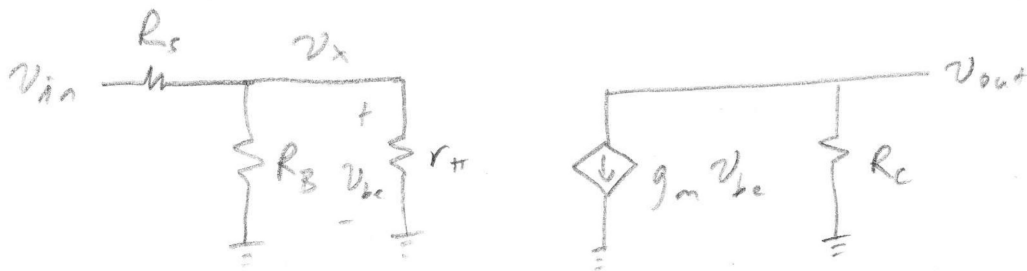Small-Signal Model (Assuming $V_A \rightarrow \infty$, like the previous problem)




→ This looks just like a "standard" CE Amp

$$a_v = \frac{v_{out}}{v_{in}} = -g_m R_C \left(\frac{R_{in}}{R_S + R_{in}} \right) = -140.67$$


(Much larger than the previous version of the amplifier)

Find the small signal gain

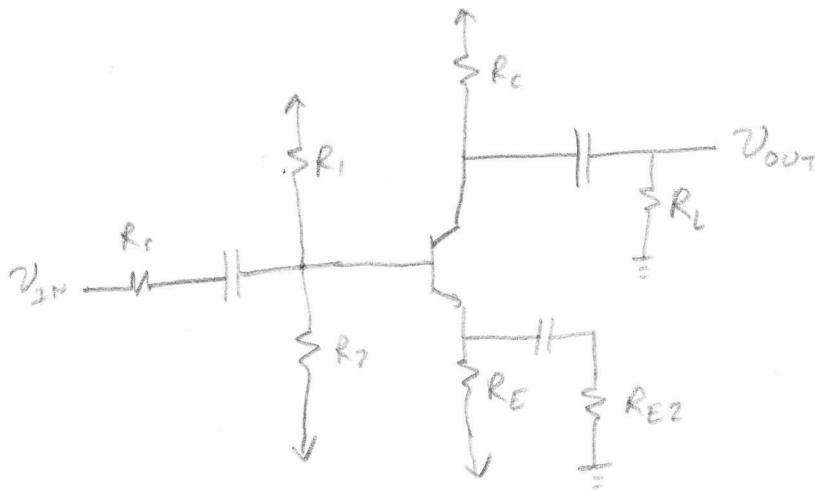

Note, the DC circuit is still the same
 $\therefore I_c = 2.85 \text{ mA}$
 r_{π}, g_m, r_o remain the same

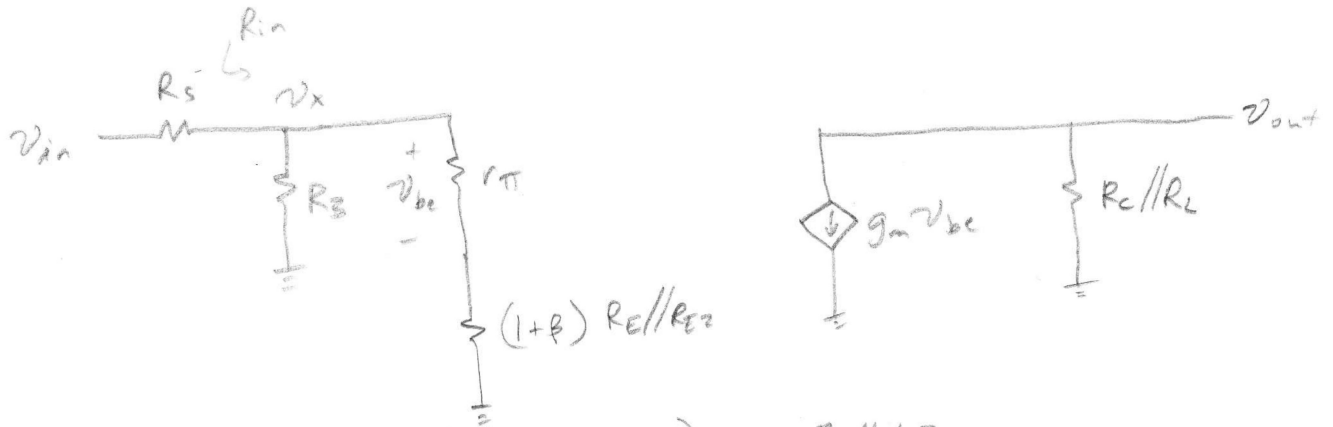Small-signal model (assume $V_A \rightarrow \infty$)



$$R_{in} = (R_B) // (r_{\pi} + (1+\beta) R_E // R_{E2}) = 8.4 \text{ k}\Omega$$

$$v_x = v_{in} \frac{R_{in}}{R_s + R_{in}} = v_{in} (0.944)$$

$$v_{be} = v_x \frac{r_{\pi}}{r_{\pi} + (1+\beta) R_E // R_{E2}} = v_x (0.09035)$$

$$a_v = \frac{v_{out}}{v_{in}} = -g_m v_{be} R_c // R_L = -18.3$$

This is slightly less than the approximate value of

$$\frac{v_{out}}{v_{in}} \approx -\frac{R_c}{R_{E2}}$$