
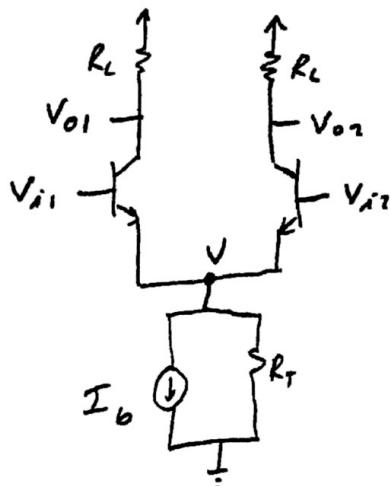


Find A_{dm} , A_{cm} , and CMRR.

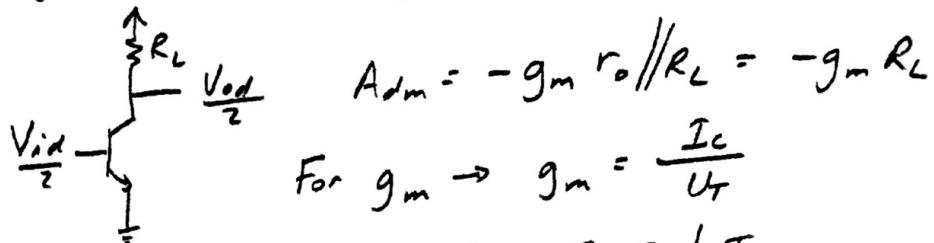

For $A_{dm} \rightarrow$ Differential Half Mode Circuit
(Node V is an AC ground) $r_o \rightarrow \infty$



$$A_{dm} = -g_m r_o // R_L = -g_m R_L$$

$$\text{For } g_m \rightarrow g_m = \frac{I_c}{U_T}$$

Note \rightarrow in DC, $I_{E1} = \frac{1}{2} I_b$


$$\therefore I_{c1} = \alpha I_{E1}$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} = 0.99$$

$$A_{dm} = -\frac{(\alpha) \frac{1}{2} I_b R_L}{U_T} = \frac{-(0.99)(1mA)(10k\Omega)}{(2)(25.9mV)}$$

$$\boxed{A_{dm} = 191}$$

Common-Mode Half Circuit

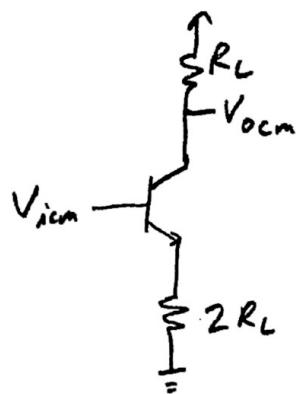

$$\text{Again } I_c = \frac{1}{2} \alpha I_b$$

$$A_{cm} = -\frac{\beta R_L}{r_{\pi} + (1+\beta)(2R_L)}$$

\rightarrow Similar to CE Amp with emitter degeneration


$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta U_T}{\alpha/2 I_b}$$

$$A_{cm} = \frac{-\beta R_L}{\frac{2\beta U_T}{\alpha/2 I_b} + (1+\beta)(2R_L)} =$$


$$= \frac{-(100)(10k\Omega)}{\frac{(2)(100)(25.9mV)}{(0.99)(1mA)} + (101)(2)(2k\Omega)} = \boxed{-2.44}$$

$$CMRR = \frac{|A_{dm}|}{|A_{cm}|} = \frac{191}{2.44} = \boxed{78.28}$$

Find A_{dm} , A_{cm} , and CMRR

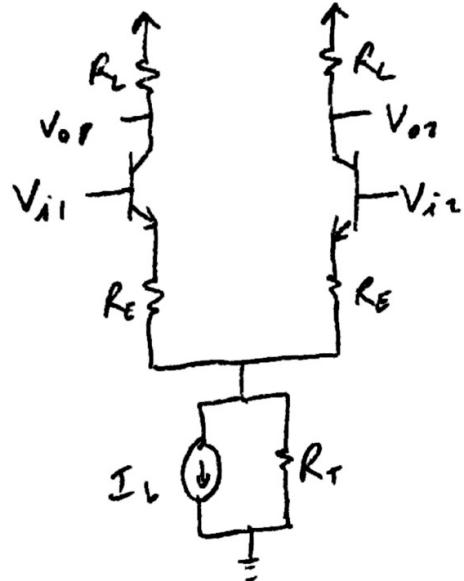

Differential Half-Mode Circuit

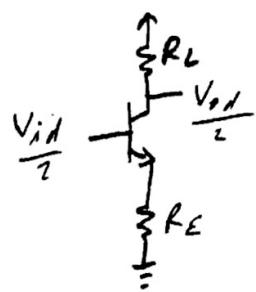

$$A_{dm} = \frac{-\beta R_L}{r_\pi + (1+\beta)(R_E)}$$


(looks like a CE Amp with
emitter degeneration)

$$\text{Note } r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C}$$

$$r_\pi = \frac{\beta V_T}{\frac{\alpha}{2} I_b} = 5.23 \pm 52$$

$$\therefore A_{dm} = -9.41$$

Common-Mode Half Circuit

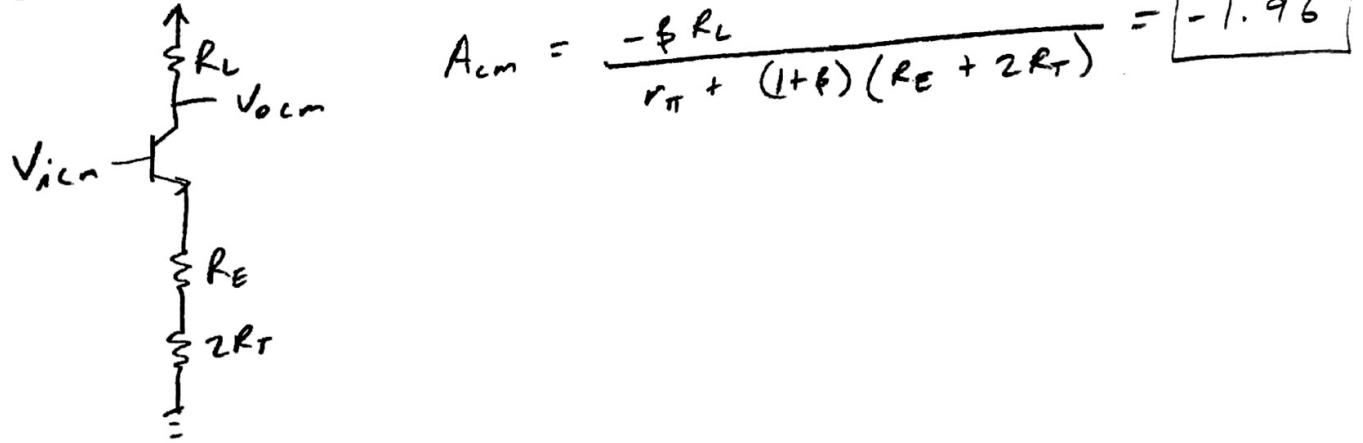


$$A_{cm} = \frac{-\beta R_L}{r_\pi + (1+\beta)(R_E + 2R_T)} = -1.96$$

$$CMRR = \frac{|A_{dm}|}{|A_{cm}|} = 4.8$$

Not nearly as large as the
previous case


Find A_{cm} , A_{dm} , and $CMRR$

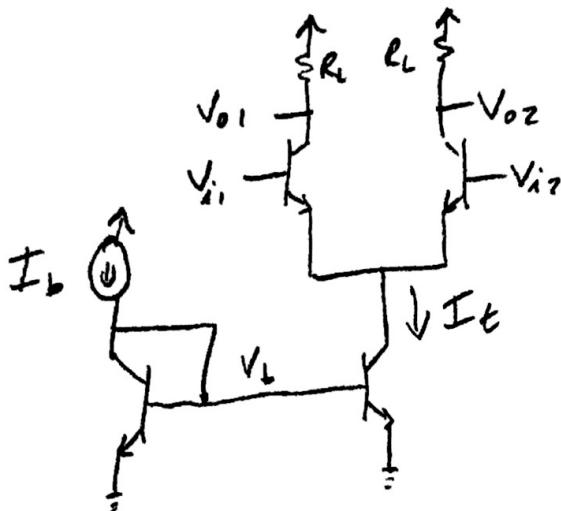

Note. I_b is a DC current source.
 $\therefore V_b$ is a constant DC voltage.

As a result, the output impedance of the current mirror is r_o .

Differential-Mode Half Circuit

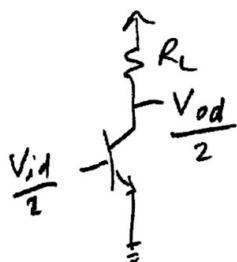

Same as part A
except for the
DC bias current

I_t = output current of the
current mirror

$$I_t = \frac{I_b}{1 + \frac{2}{\beta}} \quad (\text{current mirror equation})$$


$$\therefore I_t = \frac{1mA}{1 + \frac{2}{100}} = 0.98mA$$

$$\therefore g_m = \frac{I_c}{V_T} = \frac{\frac{1}{2}I_t}{V_T} = 18.93 \text{ mS}$$

$$r_\pi = \frac{\beta V_T}{\frac{1}{2}I_t} = 5.28 k\Omega$$

$$A_{dm} = -g_m R_L = \boxed{-189}$$

Common-Mode Half Circuit

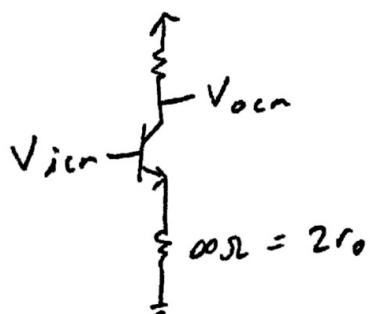


$$A_{cm} = \frac{-\beta R_L}{\frac{2 + V_T}{\alpha I_b} + (1 + \beta)(2 r_o)} = \boxed{0} \quad r_o \rightarrow \infty$$

$$CMRR = \frac{|A_{dm}|}{|A_{cm}|} = \boxed{\infty}$$

Determine which input (V_1 and V_2) corresponds to the non-inverting and inverting terminals of the following amplifier.

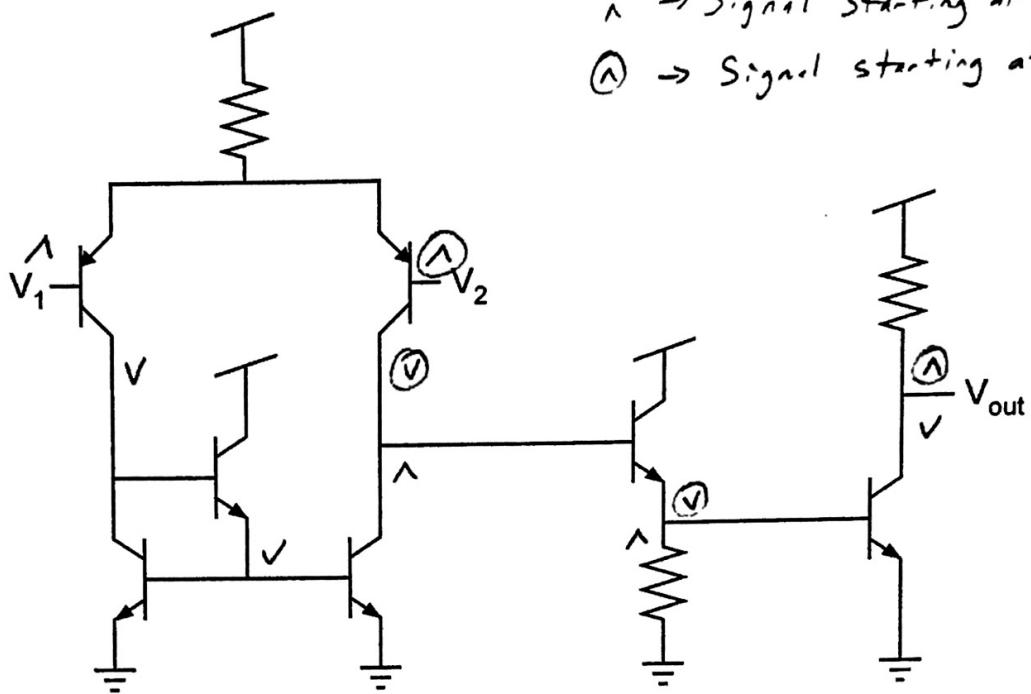^ → Signal starting at V_1
Ⓐ → Signal starting at V_2



$$\therefore V_1 = V_-$$

$$V_2 = V_+$$