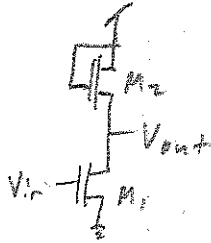



Find the voltage gain and the maximum signal swing of the following amplifier



$I_{D1} = I_{D2} = 10 \mu\text{A} \rightarrow$ Sub V_T operation

$$\left(\frac{W}{L}\right)_1 = \frac{50}{0.5} \quad \left(\frac{W}{L}\right)_2 = \frac{10}{0.5}$$

Small-Signal Model

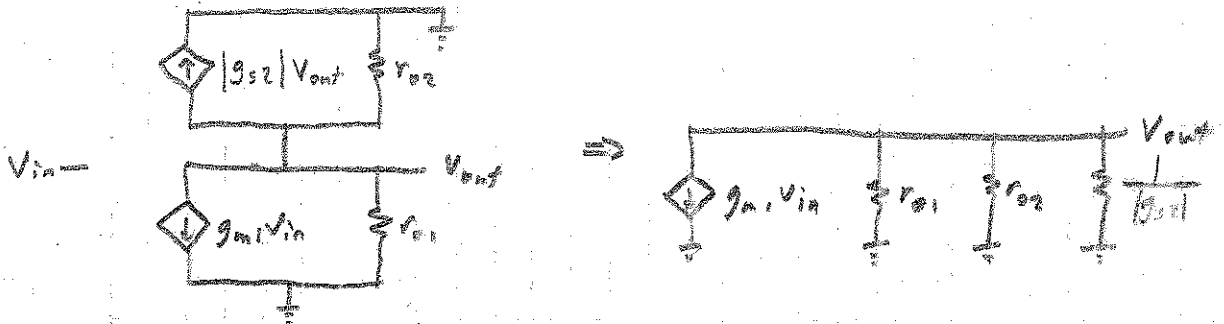

$$\frac{V_{out}}{V_{in}} = -g_{m1} r_{o1} \parallel r_{o2} \parallel \frac{1}{|g_{ss2}|} \approx -\frac{g_{m1}}{|g_{ss2}|} \quad \leftarrow \text{Is this approximation valid?}$$

$$r_{o1} = r_{o2} = \frac{V_A}{I} = \frac{50\text{V}}{10\mu\text{A}} = 5\text{G}\Omega$$

$$|g_{ss2}| = \frac{I}{V_T} = \frac{10\mu\text{A}}{25.9\text{mV}} = 3.86 \times 10^{-7} \text{ S} \Rightarrow \frac{1}{|g_{ss2}|} = 2.59 \text{ M}\Omega$$

Yes, this approximation is valid


$$\therefore \frac{V_{out}}{V_{in}} \approx -\frac{g_{m1}}{|g_{ss2}|} = -\frac{\frac{KI}{V_T}}{\frac{I}{V_T}} = -K = -0.65$$

Maximum signal swing

\rightarrow both transistors need to stay in saturation $\rightarrow \sim 100\text{mV}$ for each transistor


$$V_{swing} = V_{DD} - 2V_{sat} \approx V_{DD} - 200\text{mV}$$

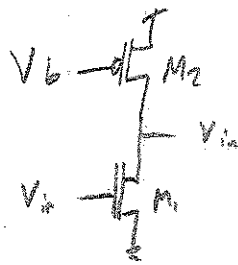Find the voltage gain and the maximum signal swing of the following amplifier



Biased such that $I_{D1} = I_{D2} = 500 \mu A \rightarrow$ Above V_T
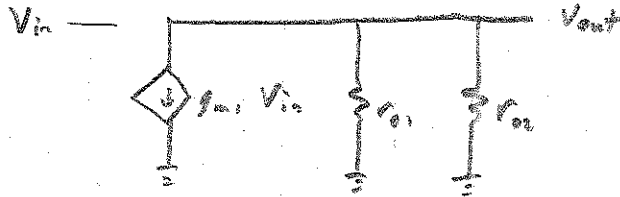
$$\left(\frac{W}{L}\right)_1 = \frac{50 \mu m}{0.5 \mu m} \quad \left(\frac{W}{L}\right)_2 = \frac{50 \mu m}{2 \mu m}$$



$$\frac{V_{out}}{V_{in}} = -g_{m1} r_{o1} // r_{o2}$$

$$g_{m1} = \sqrt{2KI} = \sqrt{2K_n \left(\frac{W}{L}\right)_1 I} = \sqrt{(2)(1.34 \times 10^{-4} A/V^2)(100)(500 \mu A)} = 3.66 \times 10^{-3} S$$

$$r_{o1} = \frac{V_{A1}}{I} = \frac{50V}{500 \mu A} = 100 k\Omega$$

We do not know V_{A2} because it has a different length. However, we know that

$$V_A \propto L \Rightarrow L_2 = 4L_1$$

$$\therefore V_{A2} = 4V_{A1} = 200V$$

$$r_{o2} = \frac{V_{A2}}{I} = \frac{200V}{500 \mu A} = 400 k\Omega$$

$$a_v = \frac{V_{out}}{V_{in}} = -g_{m1} r_{o1} // r_{o2} = -(3.66 \times 10^{-3} S)(80 k\Omega) = -292.8$$

Maximum signal swing

\rightarrow for the low end, assume M_1 is at the edge of ohmic region



\rightarrow for the high end, assume M_2 is at the edge of ohmic region

$$\therefore V_{GS} - V_T = V_{DS1} = V_{out} \rightarrow I_{D1} = K \left[(V_{GS} - V_T) V_{DS1} - \frac{1}{2} V_{DS1}^2 \right] = \frac{1}{2} K V_{out}^2$$

$$V_{out, low} = \sqrt{\frac{2I_{D1}}{K_1}} = \sqrt{\frac{(2) 500 \mu A}{(1.34 \times 10^{-4} A/V^2)(100)}} = 0.2732 V \quad (\text{low end})$$

$$V_{out, high} = \sqrt{\frac{2I_{D2}}{K_2}} = \sqrt{\frac{(2) 500 \mu A}{(4.0 \times 10^{-4} A/V^2)(25)}} = 1 V \Rightarrow V_{DD} - 1V \quad (\text{high end})$$
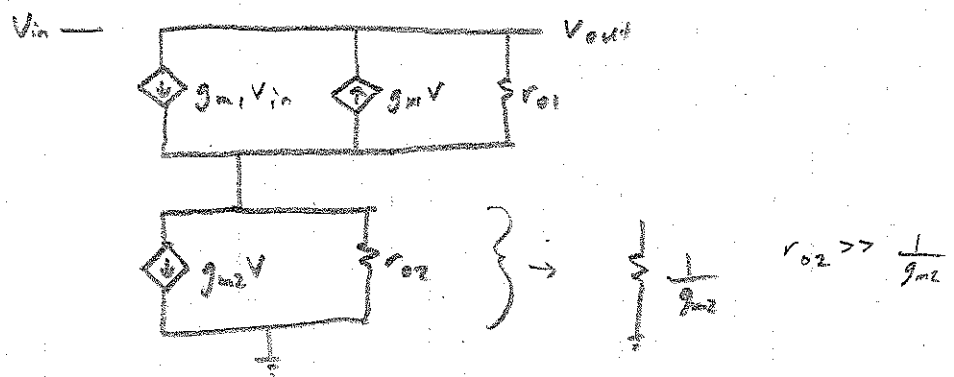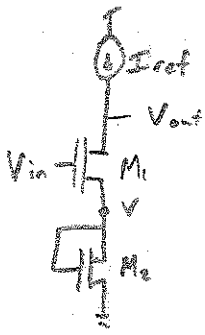
$$\text{Maximum signal swing} \Rightarrow 0.2732V < V_{out} < (V_{DD} - 1V)$$



This is simply a source-degenerated CS Amp with $R_s = \frac{1}{g_{m2}}$
 $r_{o1} \gg \frac{1}{g_{m2}}$

$\therefore R_{in} = \infty$

$$G_m = \frac{g_{m1}}{1 + g_{m1}R_s} = \frac{g_{m1}}{1 + \frac{g_{m1}}{g_{m2}}}$$

$$= \frac{g_{m1}}{1 + \frac{g_{m1}}{g_{m2}}} \quad \text{sub } V_T$$


$$= \frac{g_{m1}}{1 + \frac{g_{m1} + g_{m1}}{g_{m2}}}$$

$$R_{out} = r_{o1} + \frac{1}{g_{m2}} + \frac{g_{m1}r_{o1}}{g_{m2}} \approx r_{o1} \left(1 + \frac{g_{m1}}{g_{m2}} \right)$$


$$a_v = \frac{V_{out}}{V_{in}} = -G_m R_{out} = -\frac{g_{m1}}{1 + \frac{g_{m1}}{g_{m2}}} (r_{o1}) \left(1 + \frac{g_{m1}}{g_{m2}} \right)$$

$$= -g_{m1} r_{o1}$$

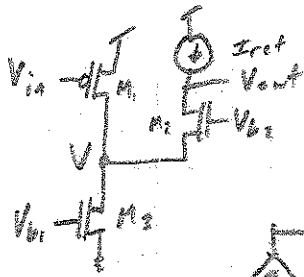
With an infinite load impedance, R_s has no effect on the small signal gain



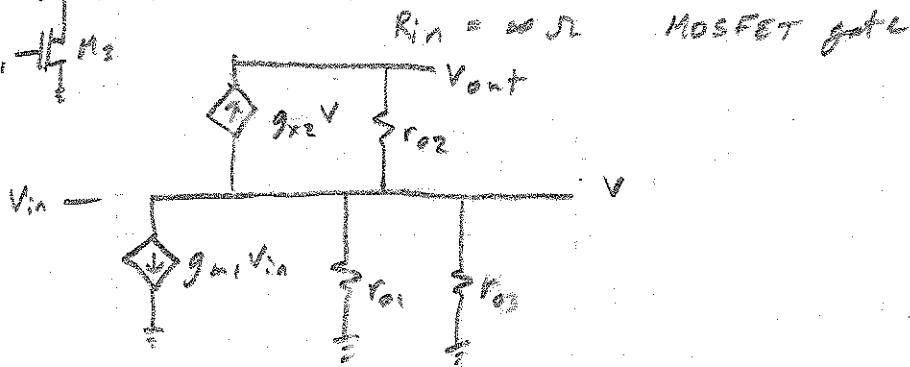Folded cascode structure with an ideal current source load




$R_{out} = \frac{V_{out}}{I_{out}} \Big|_{V_{in}=0}$ → This becomes the same as the output impedance of a source-degenerated CS Amp

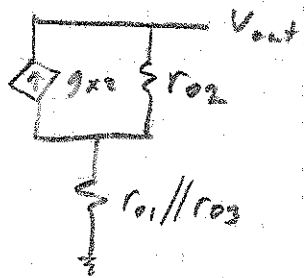

$R_{out} = r_{o2} + r_{o1} // r_{o3} + g_{x2} (r_{o1} // r_{o3}) r_{o2}$



→ less R_{out} than for a standard telescopic cascode structure

$G_m = \frac{I_{out}}{V_{in}} \Big|_{V_{out}=0}$

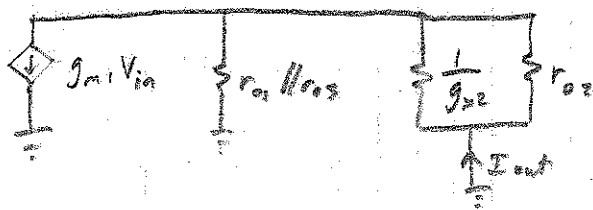

$I_{out} = \frac{g_{m1} V_{in} (r_{o1} // r_{o3})}{r_{o1} // r_{o3} + \frac{1}{g_{x2}} // r_{o2}} \Rightarrow G_m = \frac{g_{m1} r_{o1} // r_{o3}}{r_{o1} // r_{o3} + \frac{1}{g_{x2}} // r_{o2}} \approx g_{m1}$

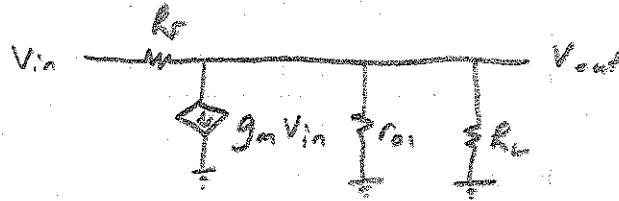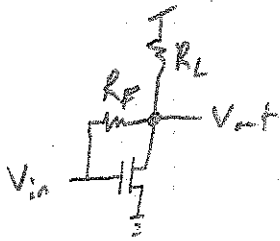$a_v = -G_m R_{out} \approx -g_{m1} (r_{o2} + r_{o1} // r_{o3} + g_{x2} (r_{o1} // r_{o3}) r_{o2})$
 $\approx \underbrace{-g_{m1} r_{o1} // r_{o3}}_{\text{gain of first stage}} \underbrace{g_{x2} r_{o2}}_{\text{gain of second stage}}$




KCL at V_{out}

$$\frac{V_{in} - V_{out}}{R_F} = g_m V_{in} + \frac{V_{out}}{r_o} + \frac{V_{out}}{R_L}$$

$$V_{in} \left(\frac{1}{R_F} - g_m \right) = V_{out} \left(\frac{1}{r_o} + \frac{1}{R_L} + \frac{1}{R_F} \right)$$


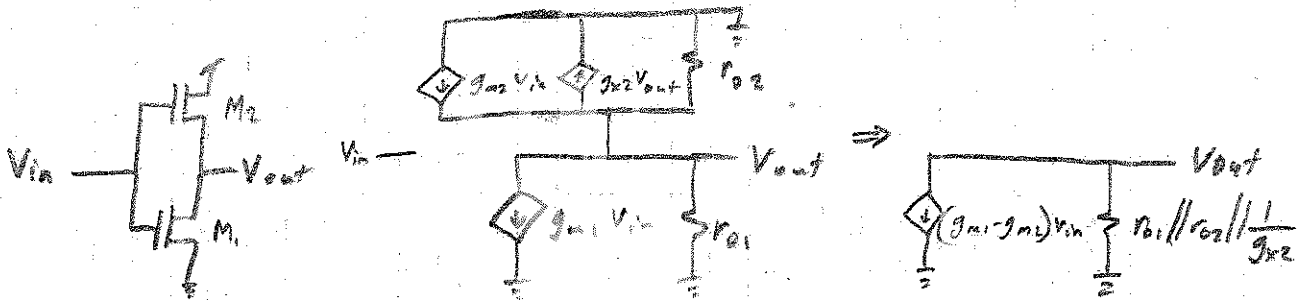
$$a_v = \frac{V_{out}}{V_{in}} = - \left(g_m - \frac{1}{R_F} \right) r_o \parallel R_L \parallel R_F$$



$$a_v = \frac{V_{out}}{V_{in}} = -(g_{m1} - g_{m2}) r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

$$= \frac{-(g_{m1} - g_{m2}) r_{o1} \parallel r_{o2}}{1 + g_{m2} r_{o1} \parallel r_{o2}} \approx \frac{-(g_{m1} - g_{m2})}{g_{m2}}$$

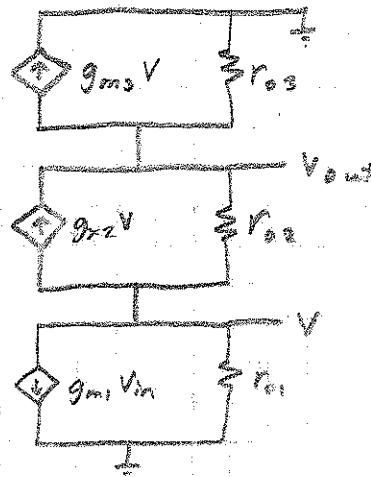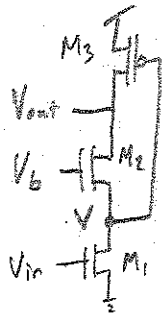Find the small-signal voltage gain of the following amplifier



The current flowing through each transistor is equal to each other.

$$g_{m1} V_{in} + \frac{V}{r_{o1}} = -g_{x2} V + \frac{V_{out} - V}{r_{o2}} = -\left(g_{m3} V + \frac{V_{out}}{r_{o3}}\right)$$

Transistor → ①

②

③

$$\text{②} = \text{③} \Rightarrow -g_{x2} V + \frac{V_{out} - V}{r_{o2}} = -\left(g_{m3} V + \frac{V_{out}}{r_{o3}}\right)$$

$$V_{out} \left(\frac{1}{r_{o2}} + \frac{1}{r_{o3}}\right) = V \left(\frac{1}{r_{o2}} + g_{x2} - g_{m3}\right)$$

$$V = \frac{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}{\frac{1}{r_{o2}} + g_{x2} - g_{m3}} V_{out}$$

$$\text{①} = \text{③} \Rightarrow g_{m1} V_{in} + \frac{V}{r_{o1}} = -\left(g_{m3} V + \frac{V_{out}}{r_{o3}}\right)$$

$$g_{m1} V_{in} + V \left(\frac{1}{r_{o1}} + g_{m3}\right) = -\frac{V_{out}}{r_{o3}}$$

$$g_{m1} V_{in} + \frac{V_{out} \left(\frac{1}{r_{o2}} + \frac{1}{r_{o3}}\right) \left(\frac{1}{r_{o1}} + g_{m3}\right)}{\frac{1}{r_{o2}} + g_{x2} - g_{m3}} = -\frac{V_{out}}{r_{o3}}$$

$$g_{m1} V_{in} = -V_{out} \left[\frac{1}{r_{o3}} + \frac{\left(\frac{1}{r_{o2}} + \frac{1}{r_{o3}}\right) \left(\frac{1}{r_{o1}} + g_{m3}\right)}{\frac{1}{r_{o2}} + g_{x2} - g_{m3}} \right]$$


$$g_{m1} V_{in} = -V_{out} \left[\frac{1}{r_{o3}} + \frac{(r_{o2} + r_{o3})(1 + g_{m3} r_{o1})}{r_{o1} r_{o3} (1 + (g_{x2} - g_{m3}) r_{o2})} \right]$$

$$g_{m1} V_{in} = -V_{out} \left[\frac{r_{o3} (1 + (g_{m2} - g_{m3}) r_{o2}) + (r_{o2} + r_{o3}) (1 + g_{m3} r_{o1})}{r_{o1} r_{o3} (1 + (g_{m2} - g_{m3}) r_{o2})} \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} r_{o1} r_{o3} [1 + (g_{m2} - g_{m3}) r_{o2}]}{r_{o3} [1 + (g_{m2} - g_{m3}) r_{o2}] + (r_{o2} + r_{o3}) (1 + g_{m3} r_{o1})}$$

$$= \frac{-g_{m1} r_{o1} r_{o3} [1 + (g_{s2} - g_{m3}) r_{o2}]}{r_{o3} [1 + (g_{s2} - g_{m3}) r_{o2}] + (r_{o2} + r_{o3}) (1 + g_{m3} r_{o1})} \quad (\text{Sub } V_7)$$
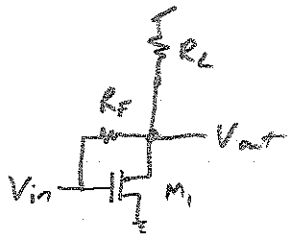
$$= \frac{-g_{m1} r_{o1} r_{o3} [1 + (g_{m2} + g_{mb2} - g_{m3}) r_{o2}]}{r_{o3} [1 + (g_{m2} + g_{mb2} - g_{m3}) r_{o2}] + (r_{o2} + r_{o3}) (1 + g_{m3} r_{o1})} \quad (\text{above } V_7)$$



Sketch V_{out} vs. V_{in} as V_{in} is swept from 0 to V_{DD}

Let $I_D = 0$ (no sub V_T current flow)

↳ When $V_{in} < V_T \rightarrow$ no current flow in M_1

$$R_F = 20k\Omega \quad R_L = 10k\Omega$$

When $V_{in} < V_T$



⇒ Resistive Divider with two voltage sources

- V_{in}
- V_{DD}

⇒ use Superposition

$$V_{out} = \underbrace{\frac{R_L}{R_L + R_F}}_{\text{Slope}} V_{in} + \underbrace{\frac{R_F}{R_L + R_F}}_{\text{Constant}} V_{DD} = \frac{1}{3} V_{in} + \frac{2}{3} V_{DD}$$

$$= 0.33V_{in} + 3.33V$$

For $V_{in} > V_T$, the transistor turns on

$$\text{At } V_{in} = V_T \rightarrow V_{out} = \frac{1}{3}(0.7V) + 3.33V = 3.57V$$

↳ Therefore when M_1 turns on, it will be in Saturation

M_1 is in saturation for $V_T < V_{in} < \frac{V_{out}}{V_{in} - V_T}$

Cannot use the small-signal model because we are looking at large-signal parameters

KCL at V_{out}

$$\frac{V_{in} - V_{out}}{R_F} + \frac{V_{DD} - V_{out}}{R_L} = I_D$$

At the edge of Saturation

$$V_{out} = V_{in} - V_T \Rightarrow V_{in} = V_{out} + V_T$$

$$I_D = \frac{K}{2} (V_{GS} - V_T)^2 = \frac{K}{2} (V_{in} - V_T)^2 = \frac{K V_{out}^2}{2} \quad \text{assume } V_D = \text{large}$$

$$\frac{V_{out} + V_T - V_{out}}{R_F} + \frac{V_{DD} - V_{out}}{R_L} = \frac{K}{2} V_{out}^2$$

$$\frac{K}{2} V_{out}^2 + \frac{1}{R_L} V_{out} - \left(\frac{V_{DD}}{R_L} + \frac{V_T}{R_F} \right) = 0$$

$$(25 \mu\text{A/V}^2) V_{\text{out}}^2 + (1 \times 10^{-4} \text{ S}) V_{\text{out}} - (5.35 \times 10^{-4} \text{ A}) = 0$$

solve for V_{out} (quadratic equation)

$$V_{\text{out}} = \frac{-(1 \times 10^{-4}) \pm \sqrt{(1 \times 10^{-4})^2 + (4)(25 \times 10^{-6})(5.35 \times 10^{-4})}}{(2)(25 \times 10^{-6})}$$

$$= -7.0398, 3.0398$$



The only valid value

V_{in} at the edge of ohmic

$$V_{\text{in}} = V_{\text{out}} + V_T = 3.7398 \text{ V}$$

