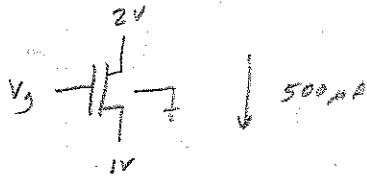


Determine the complete small-signal equivalent model for the following transistor



$$\begin{aligned}
 W &= 100 \mu\text{m} \\
 L &= 1 \mu\text{m} \\
 C_{ov} &= 0.1 \text{ fF}/\mu\text{m} \\
 C_{ox} &= 3.5 \text{ fF}/\mu\text{m}^2
 \end{aligned}$$

$$\begin{aligned}
 C_{sbo} = C_{dso} &= 100 \text{ fF} \leftarrow \text{includes area and sidewall} \\
 m &= 1 \\
 V_{bi} &= 0.7 \text{ V}
 \end{aligned}$$

$500 \mu\text{A} > I_{th} \Rightarrow$ Above V_T , ohmic or saturation?

V_A is relatively large so, $I \approx \frac{K}{2} V_{ov}^2$ (edge of ohmic/saturation)

$$V_{ov} \approx \sqrt{\frac{2I}{K}} = \sqrt{\frac{2(500 \mu\text{A})}{(100 \mu\text{m}/2)(100)}} = 0.3162 \text{ V} < V_{DS} = 1 \text{ V}$$

\Rightarrow saturation

$$g_m = \sqrt{2KI} = \sqrt{2K' \frac{W}{L} I}$$

$$= \sqrt{2(100 \mu\text{A}/\text{V}^2)(100)(500 \mu\text{A})} = 3.16 \text{ mA/V}$$

Low-Frequency Parameters

$$g_{mb} = \frac{\gamma g_m}{2\sqrt{V_{SB} + (2 \text{ fF})}} = \frac{(0.4)(3.16 \text{ mA/V})}{(2)\sqrt{1 \text{ V} + 0.7 \text{ V}}} = 4.8507 \times 10^{-4} \text{ A/V}$$

$$r_o = \frac{50 \text{ V}}{500 \mu\text{A}} = 100 \text{ k}\Omega$$

Need to find capacitance values $\rightarrow C_{gs}, C_{gd}, C_{gb}, C_{sbo}, C_{dso}, C_{sb}, C_{db}$

$$C_{ds} = 0 \text{ F}$$

$$\begin{aligned}
 C_{gs} &= \frac{2}{3} C_{ox} W \cdot L + C_{ov} W = \left(\frac{2}{3}\right)(3.5 \text{ fF}/\mu\text{m}^2)(100 \mu\text{m})(1 \mu\text{m}) + (0.1 \text{ fF}/\mu\text{m})(100 \mu\text{m}) \\
 &= 243.3 \text{ fF}
 \end{aligned}$$


$$C_{gd} = C_{ov} W = 10 \text{ fF}$$

$$C_{gb} \approx 0 \text{ F}$$


$$C_{sbo} = C_{dso} = 10 \text{ fF}$$

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{1 \text{ V}}{0.7 \text{ V}}}} = 6.42 \text{ fF}$$
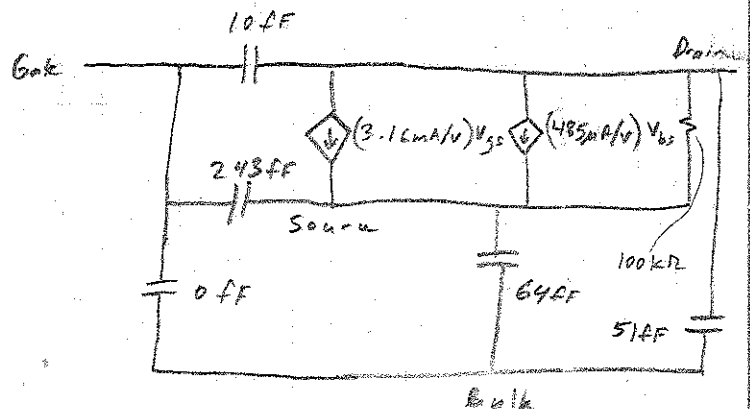
$$C_{db} = \frac{C_{dso}}{\sqrt{1 + \frac{2 \text{ V}}{0.7 \text{ V}}}} = 50.9 \text{ fF}$$


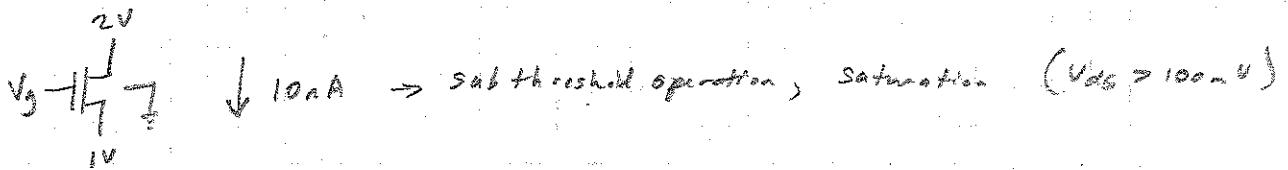
$$\begin{aligned}
 f_T &= \frac{g_m}{2\pi(C_{gs} + C_{gb} + C_{gd})} = \frac{3.16 \text{ mA/V}}{(2\pi)(243 \text{ fF} + 10 \text{ fF})} \\
 &= 1.99 \text{ GHz}
 \end{aligned}$$



$C_{sb}, C_{db} \rightarrow$ unchanged from above V_T case

$$C_{sb} = 64.2 fF, \quad C_{db} = 50.9 fF$$


$$g_m = \frac{\kappa I}{V_T} = \frac{(0.65)(10nA)}{0.0259mV} = 251 nA/V$$

$$g_s = -\frac{I}{V_T} = \frac{-10nA}{0.0259mV} = -386 nA/V$$

$$r_o = \frac{50V}{I} = \frac{50V}{10nA} = 5 G\Omega$$


$$C_{gs} = C_{gd} = C_{ov} W = 10 fF$$
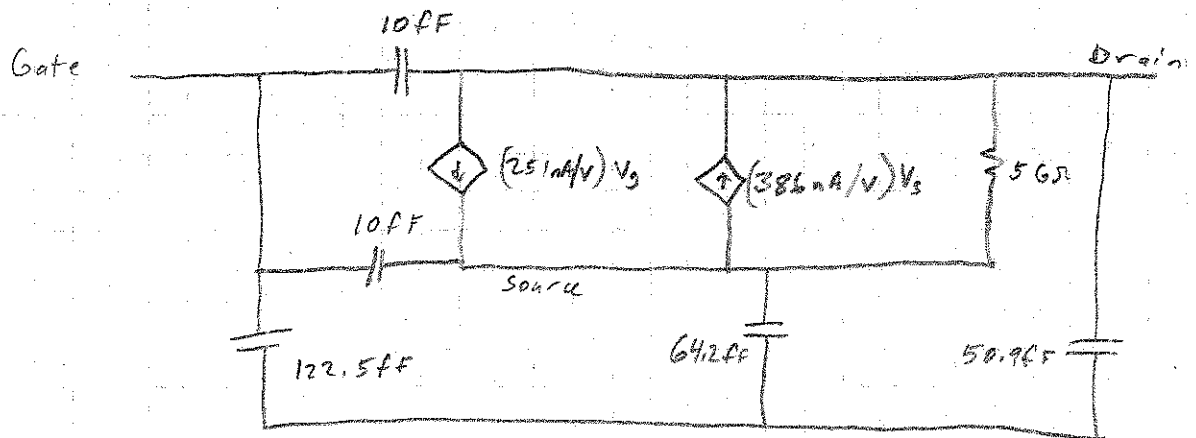
$$C_{gb} = (1-\kappa) C_{ox} W \cdot L = (0.35)(3.5 fF/\mu m^2)(100\mu m)(1\mu m) = 122.5 fF$$




$$f_T = \frac{g_m}{(2\pi)(C_{gs} + C_{gd} + C_{gb})} = \frac{251 nA/V}{(2\pi)(10fF + 10fF + 122.5fF)} = 280 kHz$$

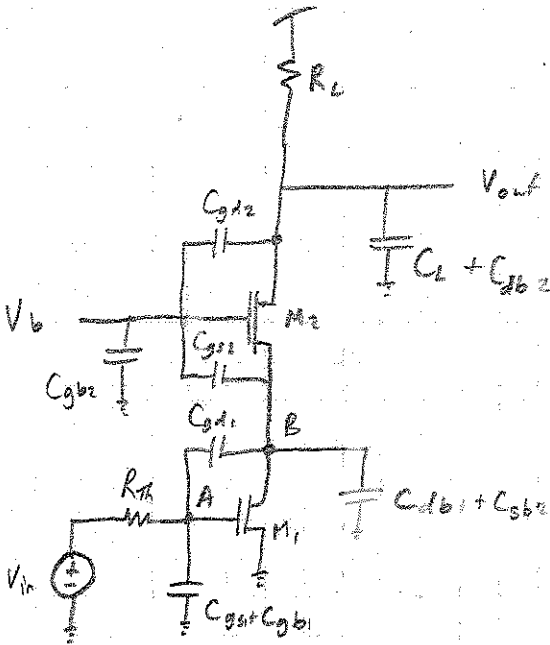Use the Miller Effect to estimate expressions for all three poles for a cascaded CS Amp with a resistive load.
 Explain why a cascode improve the frequency of operation.



What is the gain from A to B?

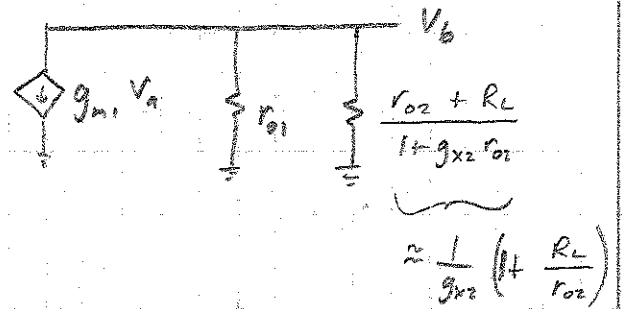

$$\frac{V_b}{V_a} = -g_{m1} r_{o1} \parallel \left(\frac{1}{g_{m2}} \left(1 + \frac{R_L}{r_{o2}} \right) \right)$$

if $R_L < r_{o2}$



$$\frac{V_b}{V_a} \approx -\frac{g_{m1}}{g_{m2}}$$

if $R_L \approx r_{o2}$ (e.g. r_o from a transistor)

$$\frac{V_b}{V_a} \approx -\frac{2 g_{m1}}{g_{m2}}$$

Assume R_L is relatively small. If not, there will only be a small error

Use Miller approximation

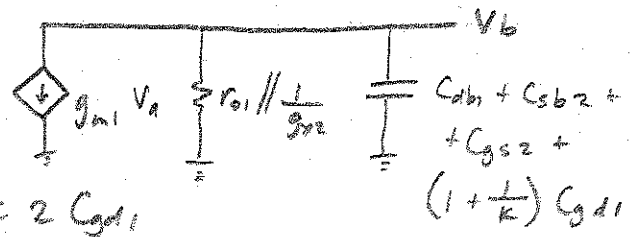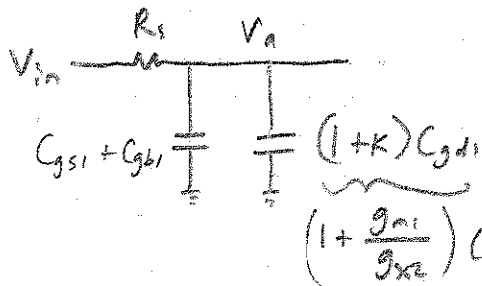

↳ much smaller than $g_{m1} r_{o1} C_{gd1}$

$$\omega_p = \frac{1}{R_{s, \text{eff}} C_{s, \text{eff}}} = \frac{1}{(R_s) \left(C_{gs1} + C_{gb1} + \left(1 + \frac{g_{m1}}{g_{m2}} \right) C_{gd1} \right)}$$

$$\omega_b = \frac{1}{R_{b, \text{eff}} C_{b, \text{eff}}} =$$

$$= \frac{1}{\left[r_{o1} \parallel \left[\frac{1}{g_{m2}} \left(1 + \frac{R_L}{r_{o2}} \right) \right] \right] \left[C_{db1} + C_{sb2} + C_{gs2} + \left(1 + \frac{g_{m2}}{g_{m1}} \right) C_{gd1} \right]}$$

$$\approx \frac{g_{m2}}{C_{db1} + C_{sb2} + C_{gs2} + \left(1 + \frac{g_{m2}}{g_{m1}} \right) C_{gd1}}$$

$$\omega_{\text{out}} = \frac{1}{R_{\text{out}, \text{eff}} C_{\text{out}, \text{eff}}} =$$

$$= \frac{1}{\left[R_L \parallel \left[r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} \right] \right] \left[C_L + C_{db2} + C_{gd2} \right]}$$

$$\approx \frac{1}{(R_L) (C_L + C_{db2} + C_{gd2})}$$

Speed increases


For a non-cascoded CS Amp,

$$\omega_{\text{in}} = \frac{1}{(R_s) \left(C_{gs} + C_{gb} + \underbrace{\left(1 + g_m r_o \right)}_{A_v \rightarrow \text{large}} C_{gd} \right)}$$

large effective capacitance

The cascode greatly reduces this associated time constant, moving the pole to a much higher frequency

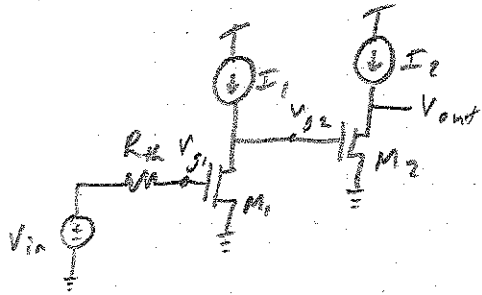Use the Miller Theorem to determine all poles in the following circuit



There is one pole for each node
 \therefore 3 poles

$$\text{pole} = -\omega_x$$


Pole frequency at V_{g1}

$$\begin{aligned} \omega_{V_{g1}} &= \frac{1}{R_{V_{g1}, \text{eff}} C_{V_{g1}, \text{eff}}} \\ &= \frac{1}{(R_{th}) (C_{gs1} + C_{gb1} + (1 + g_{m1} r_{o1}) C_{gd1})} \end{aligned}$$

$$\begin{aligned} \omega_{V_{g2}} &= \frac{1}{(r_{o1}) (C_{db1} + (1 + \frac{1}{g_{m1} r_{o1}}) C_{gd1} + C_{gs2} + C_{gb2} + (1 + g_{m2} r_{o2}) C_{gd2})} \\ &\approx \frac{1}{(r_{o1}) (C_{db1} + C_{gd1} + C_{gs2} + C_{gb2} + (1 + g_{m2} r_{o2}) C_{gd2})} \end{aligned}$$

$$\begin{aligned} \omega_{V_{out}} &= \frac{1}{(r_{o2}) (C_{db2} + (1 + \frac{1}{g_{m2} r_{o2}}) C_{gd2})} \\ &\approx \frac{1}{(r_{o2}) (C_{db2} + C_{gd2})} \end{aligned}$$

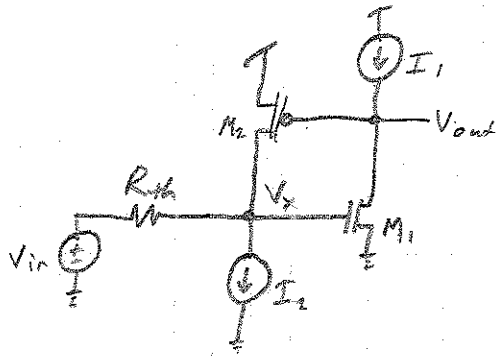Determine the transfer function of the following circuit including all parasitic capacitances




$$\text{Let } C_1 = C_{gs1} + C_{gb1} + C_{dwr2}$$

$$C_2 = C_{gd1} + C_{gd2}$$

$$C_3 = C_{db1} + C_{gs2} + C_{gw2}$$

Small-signal model

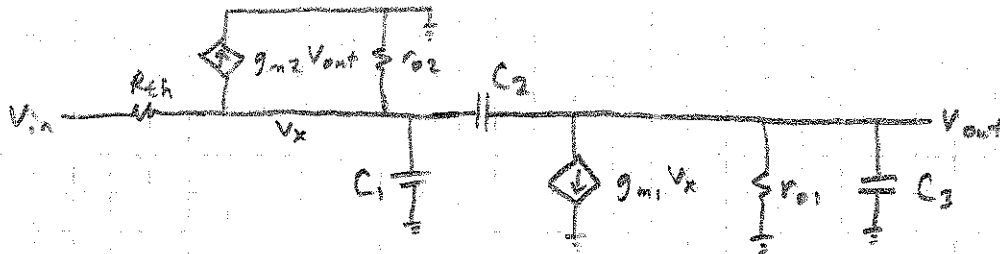

KCL at V_{out}

$$g_{m1} V_x + V_{out} \left(\frac{1}{r_{o1}} + s C_3 \right) + (V_{out} - V_x) s C_2 = 0$$

$$V_{out} \left(\frac{1}{r_{o1}} + s (C_2 + C_3) \right) = V_x (s C_2 - g_{m1})$$

KCL at V_x


$$\frac{(V_x - V_{in})}{R_{th}} + g_{m2} V_{out} + V_x \left(\frac{1}{r_{o2}} + s C_1 \right) + (V_x - V_{out}) s C_2 = 0$$

$$\frac{V_{in}}{R_{th}} = V_{out} (g_{m2} - s C_2) + V_x \left(\frac{1}{R_{th}} + \frac{1}{r_{o1}} + s (C_1 + C_2) \right)$$

$$\left(\frac{V_{in}}{R_{th}} \right) (s C_2 - g_{m1}) = V_{out} \left[(s C_2 - g_{m1}) (g_{m2} - s C_2) + \left(\frac{1}{r_{o1}} + s (C_2 + C_3) \right) \left(\frac{1}{R_{th}} + \frac{1}{r_{o2}} + s (C_1 + C_2) \right) \right]$$


$$\frac{V_{out}}{V_{in}} = \frac{\left(\frac{1}{R_{th}} \right) (s C_2 - g_{m1})}{s^2 [C_1 C_2 + C_1 C_3 + C_2 C_3] + s [C_2 (g_{m1} + g_{m2}) + \frac{1}{r_{o1}} (C_1 + C_2) + (C_1 + C_2) \left(\frac{1}{R_{th}} + \frac{1}{r_{o2}} \right) + \left(\frac{1}{r_{o1}} \right) \left(\frac{1}{R_{th}} + \frac{1}{r_{o2}} \right) - g_{m1} g_{m2}]}$$

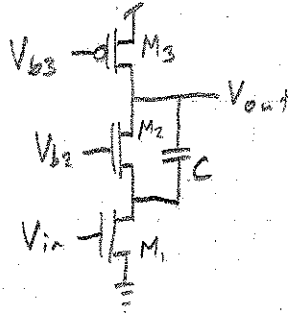Find the gain at very low frequencies and at high frequencies



At low frequencies

$C = \text{open circuit}$

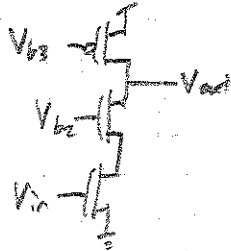


$$a_v = -g_{m1} (g_{m2} r_{o1} r_{o2} \parallel r_{o3})$$


$$\approx -g_{m1} r_{o3}$$

For high frequencies

$C = \text{short circuit}$

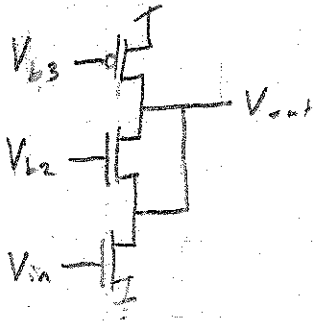


\Rightarrow

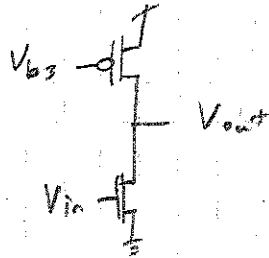


$$a_v = -g_{m1} r_{o1} \parallel r_{o3}$$

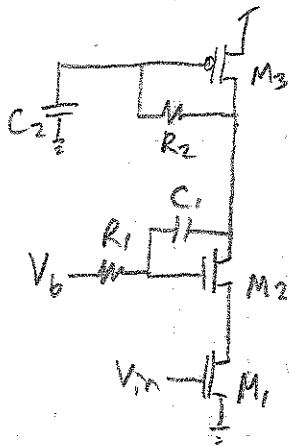Find the gain at very low frequencies and at high frequencies



Let $\sigma = 0$

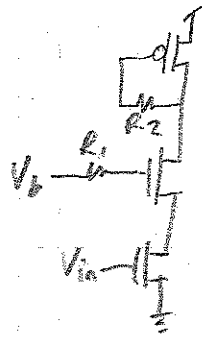Low frequencies $\rightarrow C_1 = C_2 = \text{open circuit}$




R_1 and R_2 have no effect


$$a_v = -g_{m1} (g_{m2} r_{o1} r_{o2} \parallel \frac{1}{g_{m3}})$$

$$= -g_{m1} g_{m3}$$

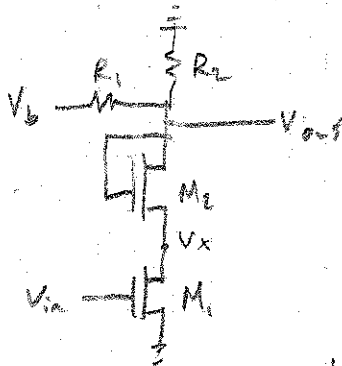High frequencies $\rightarrow C_1 = C_2 = \text{short circuits}$



Small-signal model

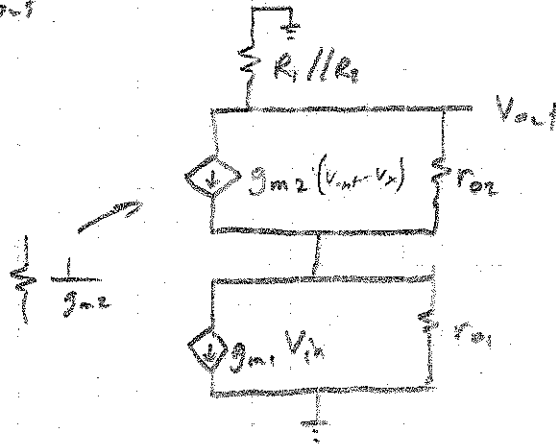


$\sigma = 0$

Use source-referred model

$$\frac{1}{g_{m2}} \parallel r_{o2} \approx \frac{1}{g_{m2}}$$

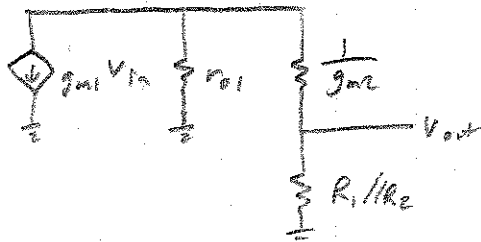Redraw the small-signal model
 \rightarrow use a current divider



$$V_{out} = -g_{m1} V_{in} \frac{r_{o1}}{r_{o1} + \frac{1}{g_{m2}} + R_1 \parallel R_2} (R_1 \parallel R_2)$$

Assuming $r_{o1} \gg R_1, R_2$

$$a_v \approx -g_{m1} R_1 \parallel R_2$$