
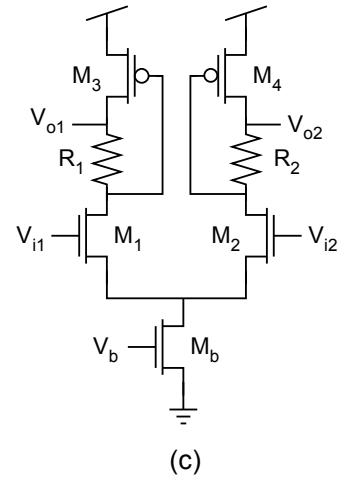
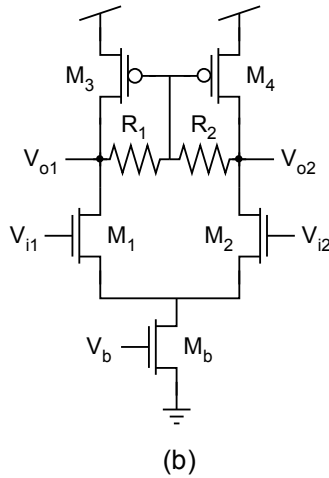


## EE 551 Linear Integrated Circuits Homework 6


Unless otherwise specified, use the following transistor parameters.

$$V_{T0} = 0.7\text{V}, \gamma = 0.4\text{V}^{1/2}, \phi_F = 0.35\text{V}, \kappa_n = \kappa_p = 0.65 \text{ (subthreshold)}, \mu_n = 1360\text{cm}^2/\text{Vs}, \mu_p = 460\text{cm}^2/\text{Vs}, K' = 100\mu\text{A}/\text{V}^2, I_0 = 1\text{pA}, I_0' = 0.1\text{pA}, I_{th} = 1\mu\text{A}, V_A = 50\text{V}, K_s = 11.8, \epsilon_0 = 8.854 \times 10^{-12}\text{F/m}, T = 300\text{K}, V_{dd} = 5\text{V}, V_{bi} = 0.7\text{V},$$

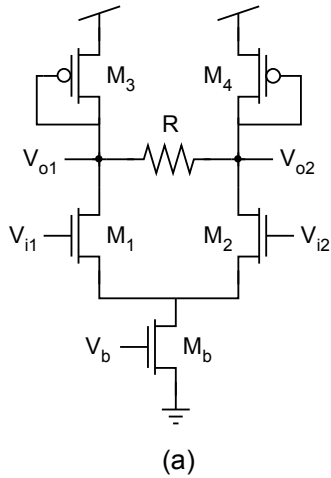1. For an nFET-based differential pair, answer the following questions. Assume that the input pair have  $W/L = 50\mu\text{m}/0.5\mu\text{m}$ ,  $I_b = 1\text{mA}$ , and that  $\lambda = 0$ .
  - a. What is the overdrive voltage of each transistor if  $V_{in} = 0$ ?
  - b. How is the bias current shared between the two input transistors if  $V_{in} = 50\text{mV}$ ?
  - c. For  $I_{out} = I_1 - I_2$  and  $V_{in} = 50\text{mV}$ , what is the effective transconductance of the differential pair? Assume that this input voltage is within the linear range of the circuit.
2. Calculate expressions for the small-signal differential voltage gain of each of the following circuits.



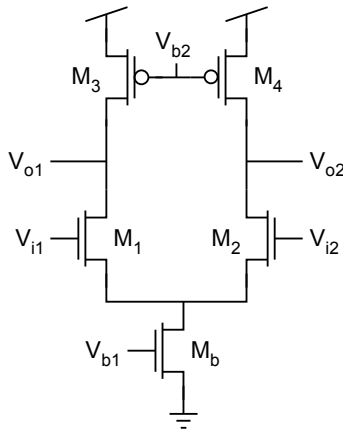3. For the following circuit, determine the following. Assume that M1-4 have  $W/L$  ratios of  $50\mu\text{m}/0.5\mu\text{m}$ ,  $I_b = 1\text{mA}$ , and  $\gamma = 0$ .



- a. Determine the small-signal differential voltage gain.
- b. Determine the maximum allowable output voltage swing of  $V_{in,cm} = 1.5\text{V}$ .

4. Calculate the following parameters given that  $I_{b1} = 100\text{nA}$ ,  $C_L = 1\text{pF}$ ,  $M_{1-10}$  and  $M_{b1}$  have  $W/L$  ratios of  $10\mu\text{m}/1\mu\text{m}$ , and  $M_{b2-5}$  are appropriately sized to set the bias voltages for  $M_9$  and  $M_{10}$  and have  $50\text{nA}$  flowing through them.
- Calculate the output resistance.
  - Calculate the small-signal differential voltage gain.
  - Calculate the slew rate.
  - Calculate the power dissipation.
  - Calculate the gain-bandwidth product, assuming that the output pole is the dominant pole.
  - Design the sizes of  $M_{b2-5}$  to appropriately bias transistors  $M_9$  and  $M_{10}$ .

