

For an nFET based differential pair with input transistors that are $W/L = 50/0.5 \mu\text{m}$ and a bias current of 1mA , (let $\lambda = 0$)

a) What is the overdrive voltage of each transistor? (let $V_{in} = 0$)

$$I = \frac{K' \frac{W}{L}}{2} \underbrace{(V_{gs} - V_T)}_{V_{ov}}^2$$

at $V_{in} = 0$, $I_1 = \frac{1}{2} I_b = I_2$

$$V_{ov} = \sqrt{\frac{2I}{K' \frac{W}{L}}} = \sqrt{\frac{2(0.5\text{mA})}{(100\text{mA/V}^2)(100)}} = \sqrt{0.1\text{V}^2} = \boxed{0.3162\text{V}}$$

b) How is the bias current shared between the two input transistors if $V_{in} = 50\text{mV}$?

$$I_1 = \frac{I_b}{2} + \frac{K' \frac{W}{L}}{4} V_{in} \sqrt{\frac{4I_b}{K' \frac{W}{L}} - V_{in}^2}$$

$$= 0.5\text{mA} + \frac{0.01\text{A/V}^2}{4} (50\text{mV}) \sqrt{\frac{(4)(1\text{mA})}{0.01\text{A/V}^2} - (50\text{mV})^2} =$$

$$= 0.5788\text{mA}$$

$$I_2 = \frac{I_b}{2} - \frac{K}{4} V_{in} \sqrt{\frac{4I_b}{K} - V_{in}^2} = 0.4212\text{mA}$$

c) For $I_{out} = I_1 - I_2$ and $V_{in} = 50\text{mV}$ (assume this is in the linear range), determine the effective transconductance of the differential pair

$$I_{out} = I_1 - I_2 = \frac{K}{2} V_{in} \sqrt{\frac{4I_b}{K} - V_{in}^2}$$


$$G_m = \frac{\partial I_{out}}{\partial V_{in}} = \frac{K}{2} \sqrt{\frac{4I_b}{K} - V_{in}^2} + \frac{\frac{1}{2} \left(\frac{K}{2} V_{in} \right) (-2V_{in})}{\sqrt{\frac{4I_b}{K} - V_{in}^2}} =$$

$$= \frac{K}{2} \frac{\frac{4I_b}{K} - V_{in}^2 - V_{in}^2}{\sqrt{\frac{4I_b}{K} - V_{in}^2}} = \frac{K}{2} \frac{\frac{4I_b}{K} - 2V_{in}^2}{\sqrt{\frac{4I_b}{K} - V_{in}^2}} =$$

$$= 3.1227\text{mS}$$

Calculate the small-signal differential voltage gain for the following circuits

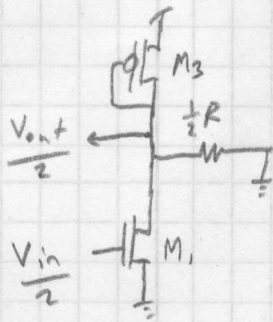a) We can use the differential half circuit for each of these three parts




$$a_v = -g_{m1} r_{o1} \parallel r_{o3} \parallel \frac{1}{2}R \parallel \frac{1}{g_{m3}}$$



$$\frac{1}{g_{m3}} \ll r_{o1}, r_{o3}$$

We don't know what R is
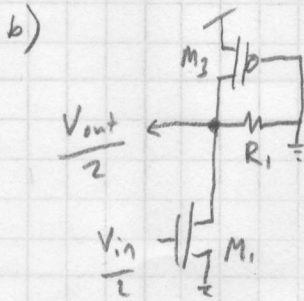
$$\therefore a_v \approx -g_{m1} \left(\frac{1}{g_{m3}} \parallel \frac{R}{2} \right)$$


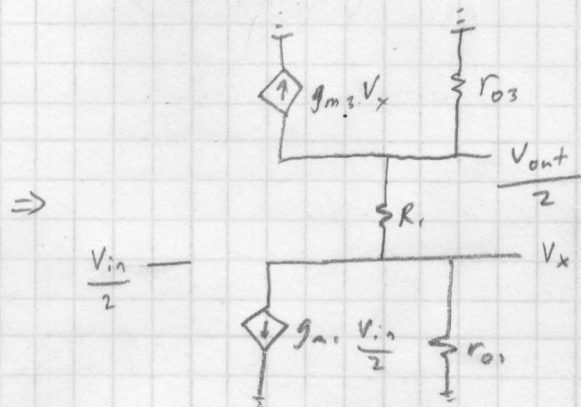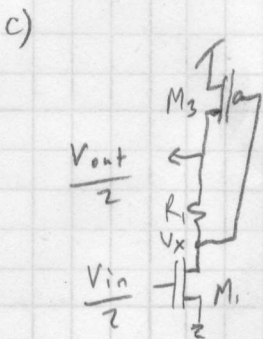
$$a_v = -g_{m1} r_{o1} \parallel r_{o3} \parallel R_1$$



$$\text{KCL at } V_x \rightarrow \frac{1}{2}g_{m1}V_{in} + \frac{V_x}{r_{o1}} + \frac{V_x - \frac{V_{out}}{2}}{R_1} = 0 \Rightarrow \frac{1}{2}g_{m1}V_{in} + V_x \left(\frac{1}{r_{o1}} + \frac{1}{R_1} \right) = \frac{V_{out}}{2R_1}$$

$$\text{KCL at } \frac{V_{out}}{2} \rightarrow g_{m3}V_x + \frac{1}{2} \frac{V_{out}}{r_{o3}} + \frac{\frac{1}{2}V_{out} - V_x}{R_1} = 0 \quad \frac{V_x(R_1 + r_{o1})}{r_{o1}R_1}$$


$$V_x = \frac{\frac{1}{2}V_{out} \left(\frac{1}{r_{o3}} + \frac{1}{R_1} \right)}{\frac{1}{R_1} - g_{m3}} = \frac{V_{out} (R_1 + r_{o3})}{2r_{o3} (1 - R_1 g_{m3})}$$

$$\frac{1}{2}g_{m1}V_{in} = \frac{1}{2}V_{out} \left[\frac{1}{R_1} - \frac{(R_1 + r_{o3})(R_1 + r_{o1})}{(r_{o1}r_{o3}R_1)(1 - R_1 g_{m3})} \right] = V_{out} \left[\frac{r_{o1}r_{o3} - r_{o1}r_{o3}R_1 g_{m3} - R_1(r_{o1}r_{o3} + r_{o1})}{r_{o1}r_{o3}R_1(1 - R_1 g_{m3})} \right]$$

$$a_v = \frac{V_{out}}{V_{in}} = \frac{-g_{m1}r_{o1}r_{o3}(1 - R_1 g_{m3})}{r_{o1} + r_{o3} + R_1 + r_{o1}r_{o3}g_{m3}}$$

Calculate the voltage gain of the following circuit

Let $\gamma = 0$

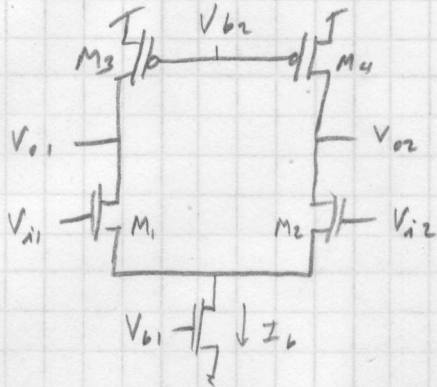

$$\text{Let } \frac{W}{L} \Big|_{1,4} = \frac{50 \mu\text{m}}{0.5 \mu\text{m}} = 100$$

$$I_b = 1 \text{ mA}$$

$$a_v = g_{m1} r_{o1} \parallel r_{o3}$$

$$r_{o1} = r_{o3} = \frac{V_A}{\frac{1}{2} I_b} = \frac{50 \text{ V}}{0.5 \text{ mA}} = 100 \text{ k}\Omega$$

$$g_{m1} = \sqrt{2 K \frac{1}{2} I_b} = \sqrt{K I_b} = \sqrt{(100 \mu\text{A}/\text{V}^2)(1 \text{ mA})(100)} = 3.162 \text{ mS}$$

$$\therefore a_v = -g_{m1} r_{o1} \parallel r_{o3} = -(3.162 \text{ mS}) [100 \text{ k}\Omega \parallel 100 \text{ k}\Omega] = -158.114$$

Find the maximum allowable output voltage swing if $V_{in,cm} = 1.5 \text{ V}$

$$\text{Maximum} \rightarrow V_{DD} - V_{ov3} \quad V_{ov3} = \sqrt{\frac{2I}{K}} = \sqrt{\frac{2(1 \text{ mA})}{(100 \mu\text{A}/\text{V}^2)(100)}} = 0.3162 \text{ V}$$

$$\hookrightarrow 5 - 0.3162 \text{ V} = 4.6838 \text{ V}$$

$$2 \frac{1}{2} I_b = I_b$$


$$\text{Minimum} \rightarrow V_{DD} - V_{sat3} - V_{sat1} + V_{gs1}$$

$$V_{in,cm} = V_{gs1} + V_{sat,b}$$

$$\therefore V_{in,cm} - V_{T1} = 1.5 \text{ V} - 0.7 \text{ V} = 0.8 \text{ V}$$

Calculate the following parameters given that $I_{b1} = 100\text{nA}$, $C_L = 1\text{pF}$, M_{1-10} and M_{b1} have W/L ratios of $10\mu\text{m}/1\mu\text{m}$, and M_{b2-5} are appropriately sized to set the bias voltages for M_9 and M_{10} and have 50nA flowing through them.

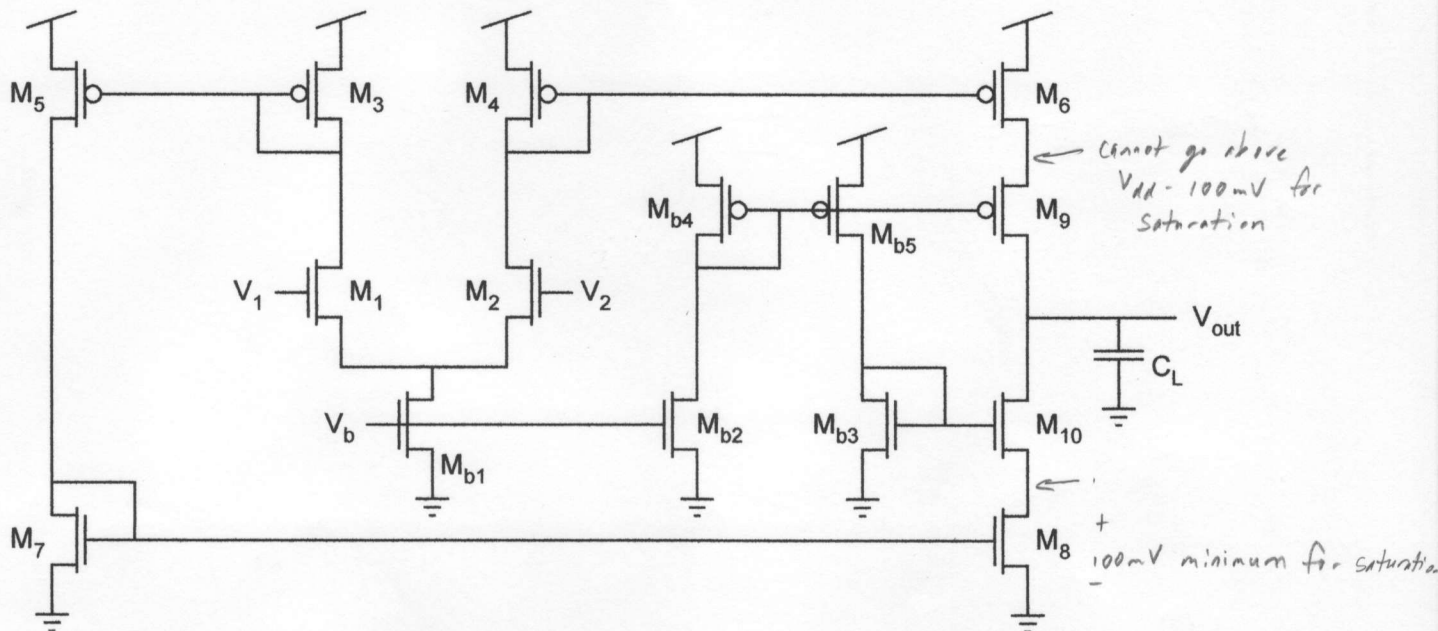- Calculate the output resistance.
- Calculate the small-signal differential voltage gain.
- Calculate the slew rate.
- Calculate the power dissipation.
- Calculate the gain-bandwidth product, assuming that the output pole is the dominant pole.
- Design the sizes of M_{b2-5} to appropriately bias transistors M_9 and M_{10} .



$$R_{out} = r_{o6} g_{m9} r_{o9} \parallel r_{o8} g_{m10} r_{o10} \quad g_{m9} = g_{m10} = |g_{m1}| = \frac{I_{b1}}{V_T} = \frac{50\text{nA}}{25.9\text{mV}} = 1.93\mu\text{S}$$

$$r_{o6} = r_{o8} = r_{o9} = r_{o10} = \frac{V_A}{I_b} = \frac{50\text{V}}{50\text{nA}} = 1\text{G}\Omega$$

$$R_{out} = \frac{1}{2} r_{o6} g_{m9} r_{o9} = \left(\frac{1}{2}\right) (1\text{G}\Omega) (1.93\mu\text{S}) (1\text{G}\Omega) = \boxed{965\text{G}\Omega}$$

$$a_v = -g_{m1} R_{out} \quad g_{m1} = \frac{K I_{b1}}{V_T} = \frac{(0.65)(50\text{nA})}{25.9\text{mV}} = 1.25\mu\text{S}$$

$$\therefore a_v = -(1.25\mu\text{S})(965\text{G}\Omega) = \boxed{-1.2 \times 10^6}$$

$$SR = \frac{I_b}{C_L} = \frac{100\text{nA}}{1\text{pF}} = 100\text{KV/s} = \boxed{0.1\text{V/ms}}$$

$$P_{diss} = (100\text{nA}) V_{DD} + (4)(50\text{nA}) V_{DD} = 1.5\mu\text{W} \quad \leftarrow \text{Must account for current through each branch (going to ground)}$$

$$GB = \frac{g_{m1}}{C_L} = \frac{g_{m1} R_{out}}{R_{out} C_L} = \frac{1.25\mu\text{S}}{1\text{pF}} = 1.25\text{MHz}$$

Design of M_{b2-5}

For $M_{10} \rightarrow V_{s10}$ cannot go below 100mV

$$\therefore I_{10} = I_0 e^{KV_{g10}/U_T} e^{-V_{s10}/U_T} \quad \leftarrow \text{with } V_A = 50V, \text{ the Early voltage will have minimal impact here}$$

$$\ln\left(\frac{I_{10}}{I_0}\right) = \frac{KV_{g10} - V_{s10}}{U_T} \quad \leftarrow 100mV$$

$$\therefore V_{g10} = \frac{1}{K} \left[U_T \ln\left(\frac{I_{10}}{I_0}\right) + V_{s10} \right] = \frac{1}{0.65} \left[25.9mV \ln \frac{50nA}{(0.1pA)(10)} + 0.100V \right]$$

$$= 0.5850V$$

$V_{g_{b3}} = V_{g_{10}} = 0.5850V \rightarrow$ Need to determine $\frac{W}{L}$ to achieve this voltage with 50nA

$$I_{b3} = I_0 e^{KV_{g_{b3}}/U_T} = I_0' \frac{W}{L} e^{KV_{g_{b3}}/U_T}$$

$$\frac{W}{L} = \frac{I_{b3}}{I_0' e^{KV_{g_{b3}}/U_T}} = \frac{50nA}{0.1pA e^{KV_{g_{b3}}/U_T}} = 0.21$$

Use reasonable sizes for $W+L$ (e.g. 0.5 μ m process)

$$\text{Let } L_{b3} = 4.8\mu m \rightarrow W_{b3} = 1\mu m$$

Let $M_{b4} = M_{b5} \rightarrow 1:1$ current mirror

Similar Design Procedure to above

V_{s9} cannot go above $V_{dd} - 100mV$

With the same parameters and biasing conditions as for M_{10}
 \rightarrow will be the same values

$$\text{Let } L_{b4} = L_{b5} = 4.8\mu m, W_{b4} = W_{b5} = 1\mu m$$

Finally $M_{b2} \rightarrow$ must have half the current as is flowing through M_{b1} with the same bias voltage

$$\therefore W_{b2} = \frac{1}{2} W_{b1} = 5\mu m$$

$$L_{b2} = L_{b1} = 1\mu m$$