
Opamps Part 2

Dr. David W. Graham

West Virginia University


Lane Department of Computer Science and Electrical Engineering

© 2009 David W. Graham

High Gain

- Goal of opamp design – High gain
- Previous opamps do not have very high gain
- Example – 5T Opamp
 - Gain = $-g_{m1}r_{o2}||r_{o4}$
 - Subthreshold operation – $|Gain| \approx 650$
 - Above threshold operation – $|Gain| \approx 50$
- Need much higher gain
 - Cascode structures provide high gain
 - Cascade of multiple amplifiers

Telescopic Opamps

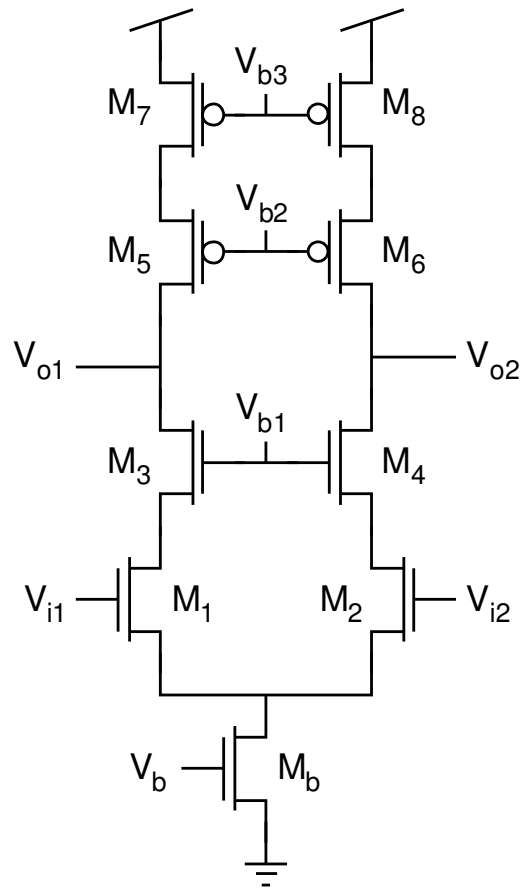

$$A_v = g_{m1} (r_{o2} g_{x4} r_{o4} \parallel r_{o8} g_{x6} r_{o6})$$



Approximately the square of the original gain

This is a high-speed opamp design

Major Drawback

- Very limited allowable signal swing
- Must ensure all transistors stay in saturation
- Limited signal swing at both the input and the output


Telescopic Opamps – Single-Ended Output

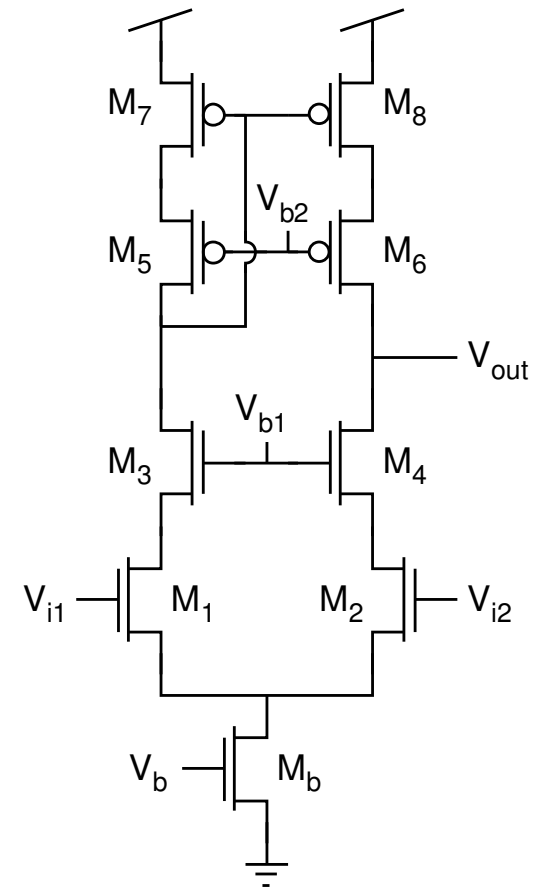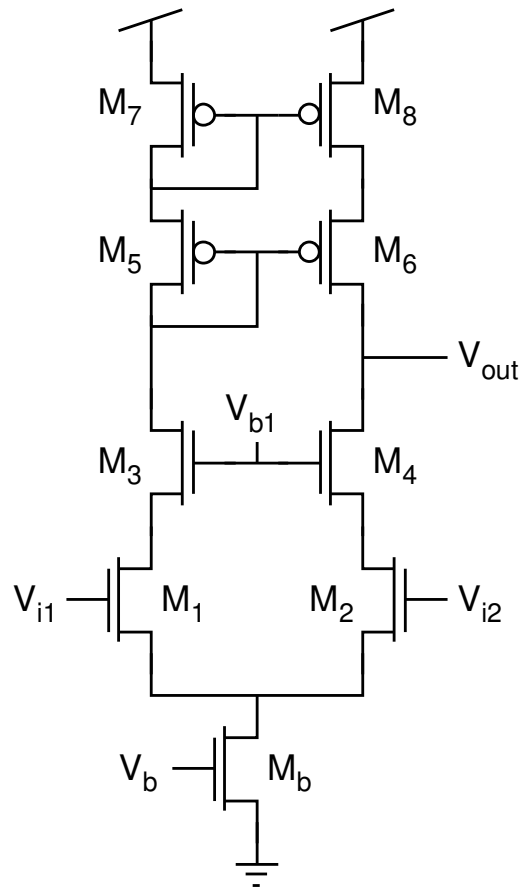

- Increased output signal swing
- Requires an additional bias


Folded Cascode Structure

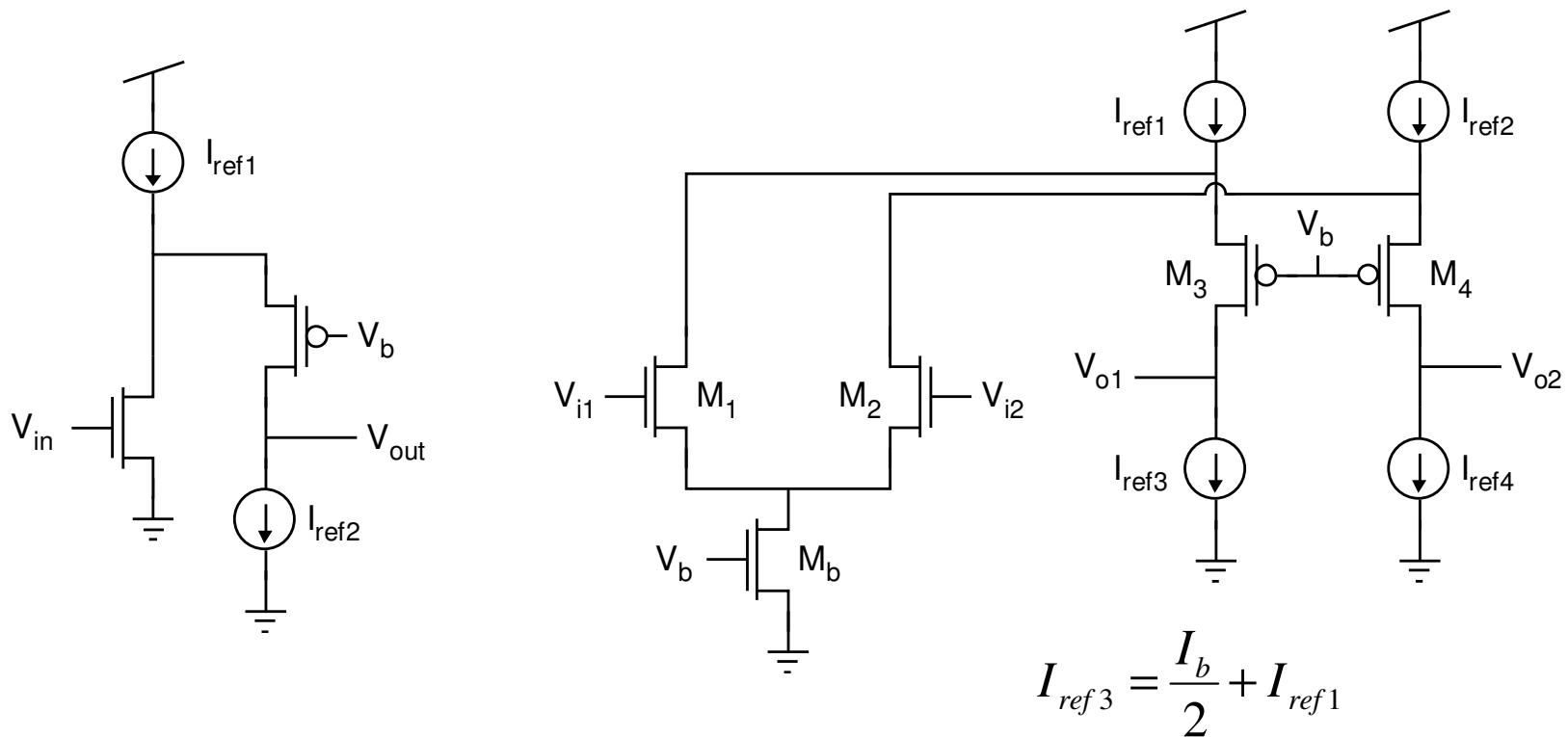Used in opamps to increase input/output voltage ranges




- I_{ref1} is typically greater than I_b to improve response after slewing
- Burns more power than the telescopic version

Folded Cascode Opamp

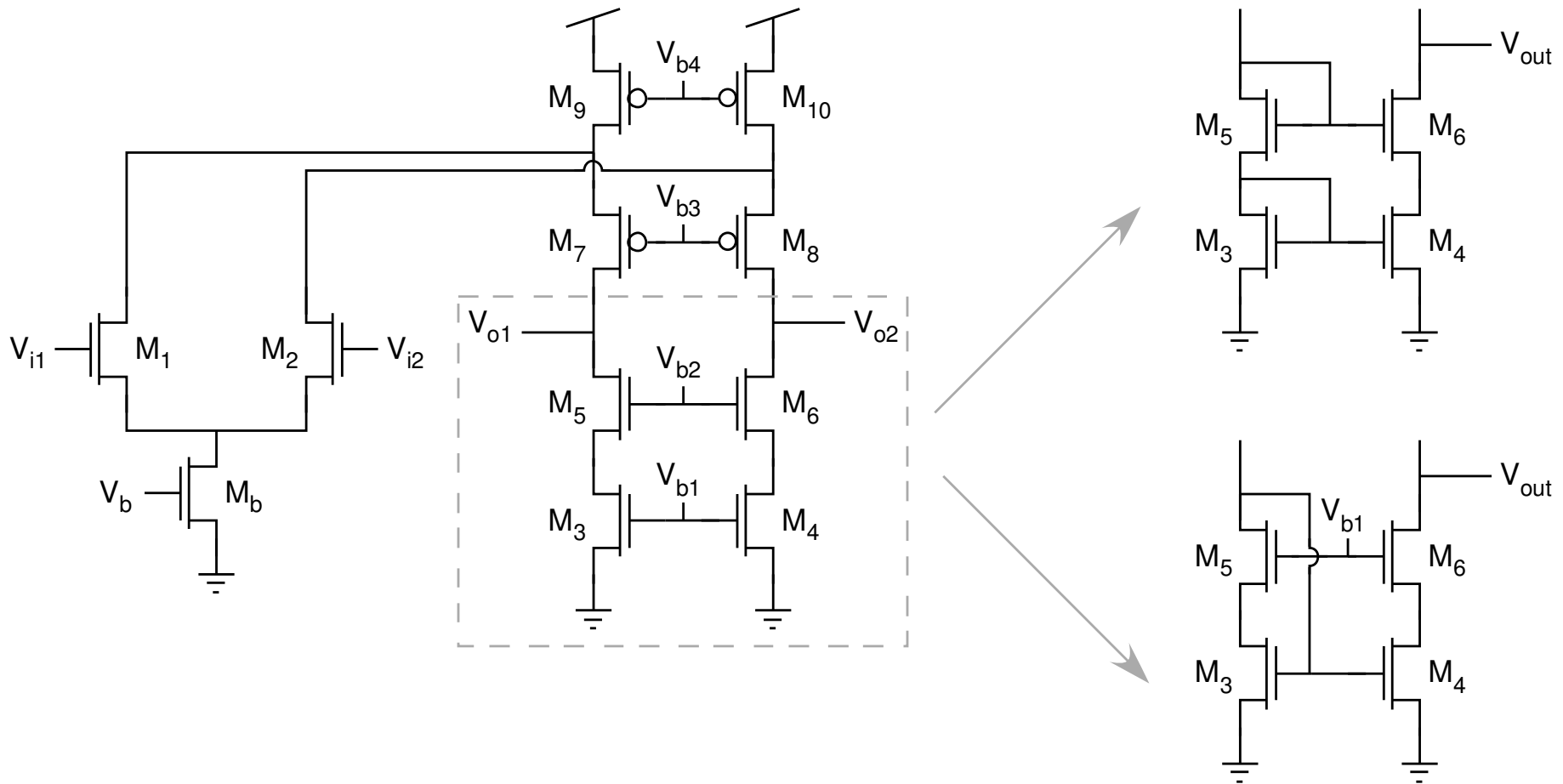

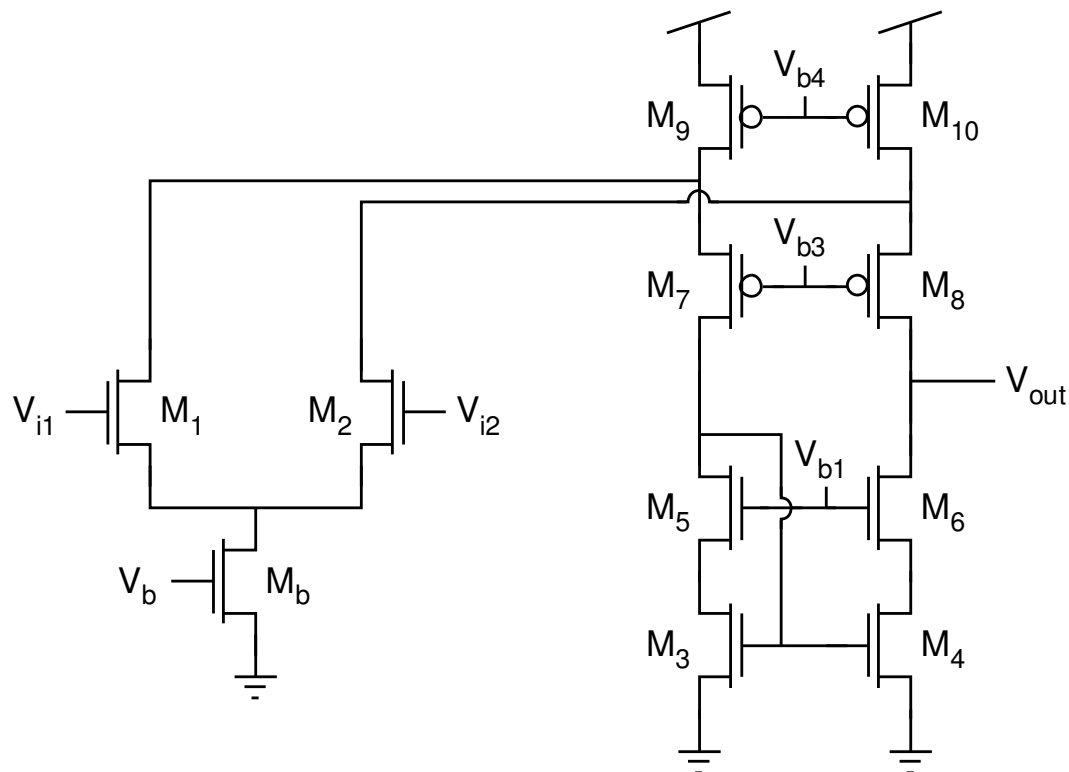Differential Gain of the Folded Cascode Opamp



- Resistance looking into the source of M_7 is much less than $r_{o1} || r_{o9}$
- Virtually all current flowing out of M_1 will flow into the source of M_7

$$A_v = g_{m1} \left[\underbrace{(r_{o8} g_{x8} (r_{o10} || r_{o2}))}_{\text{resistance looking into source of } M_7} || r_{o6} g_{x6} r_{o4} \right]$$

[Slightly] reduced gain from telescopic amplifier

ICMR

$$\begin{aligned} V_{gs1} + V_{sat,b} & \text{ to } V_{dd} - V_{sat,9} - V_{sat,1} + V_{gs1} \\ & = V_{dd} - V_{ov,9} + V_{T1} \end{aligned}$$

Can use pFET inputs for operation to ground

Output range

$$2V_{sat} \text{ to } V_{dd} - 2V_{sat}$$

Folded Cascode Summary


Comparison to Telescopic Opamp

- Larger input/output swings
- Can be used in unity-gain configuration
- One less voltage is *required* to be set
 - Do not need to worry about the CM voltage
- Decreased voltage gain
- Increased power consumption (plus, I_g should be $\sim 1.2-1.5$ times I_b)
- Lower frequency of operation
- More noise

Overall, the folded cascode opamp is a good, widely used opamp

Two-Stage Opamp

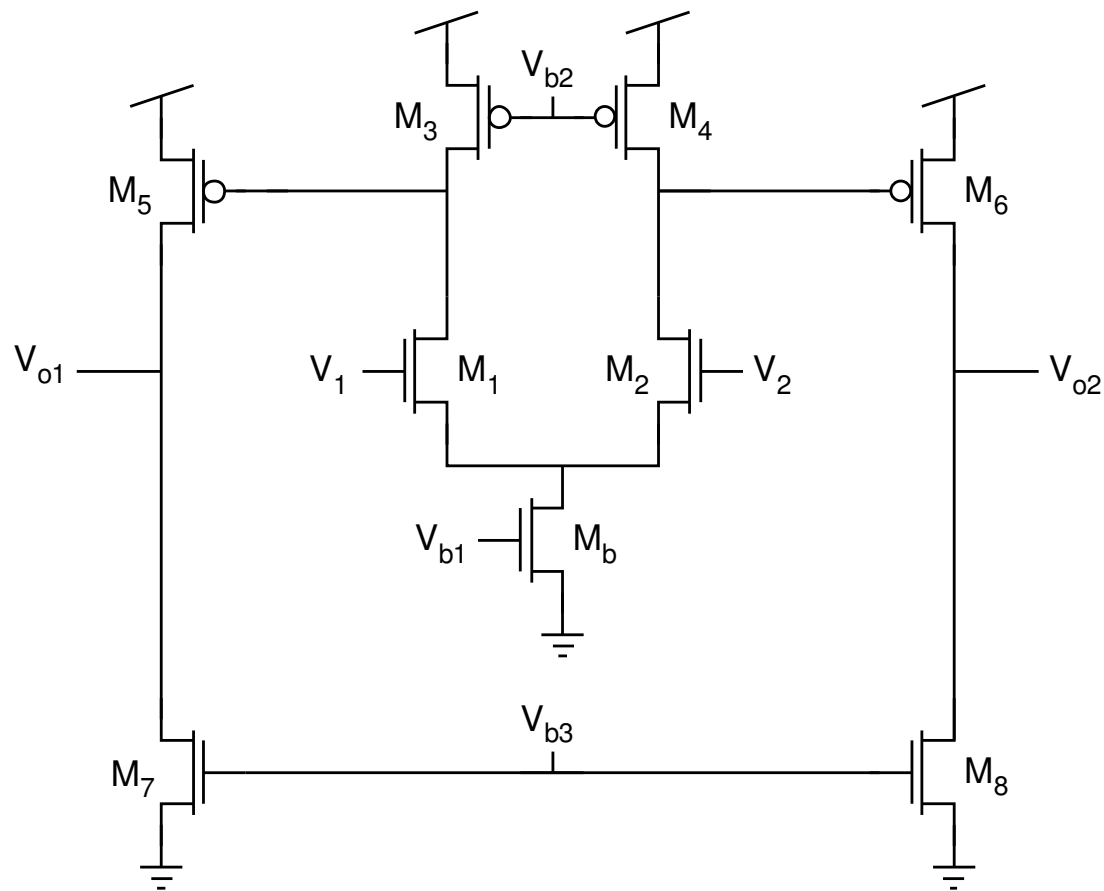- Cascade of two amplifier stages
 - First stage – Differential amplifier
 - Second stage – High-gain amplifier



Two-Stage Opamp (Single-Ended Output)

- Cascade of two amplifier stages


- First stage – Differential amplifier

$$A_{v1} = -g_{m1}r_{o2} \parallel r_{o4}$$

- Second stage – High-gain amplifier (CS Amp)



$$A_{v2} = -g_{m5}r_{o5} \parallel r_{o6}$$
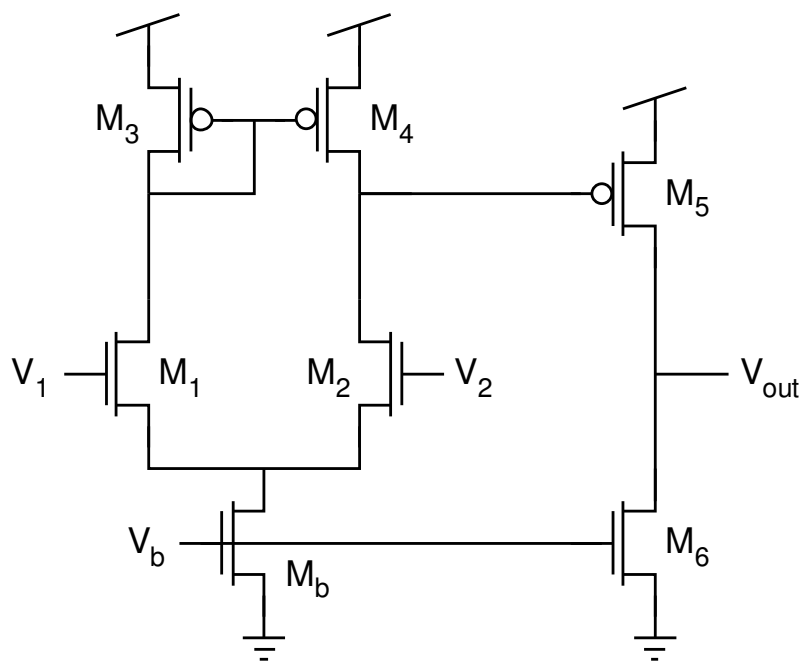
$$A_v = (g_{m1}r_{o2} \parallel r_{o4})(g_{m5}r_{o5} \parallel r_{o6})$$



- Large output swing ($V_{\text{sat},6}$ to $V_{\text{dd}} - V_{\text{sat},5}$)
- ICMR same as 5T opamp
- Unity-gain configuration sets a minimum voltage to $V_{\text{gs}1} - V_{\text{sat},b}$
- Can include cascodes, as well
- Adding an amplifier stage adds a pole
- Typically requires compensation to remain stable


Feedback Systems

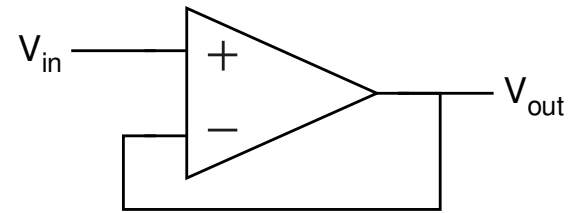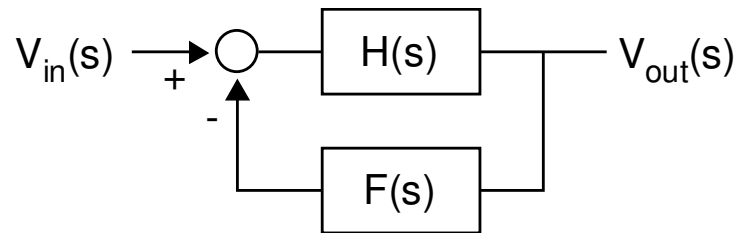

If $F(s)=1$, then unity gain feedback

Opamp Poles

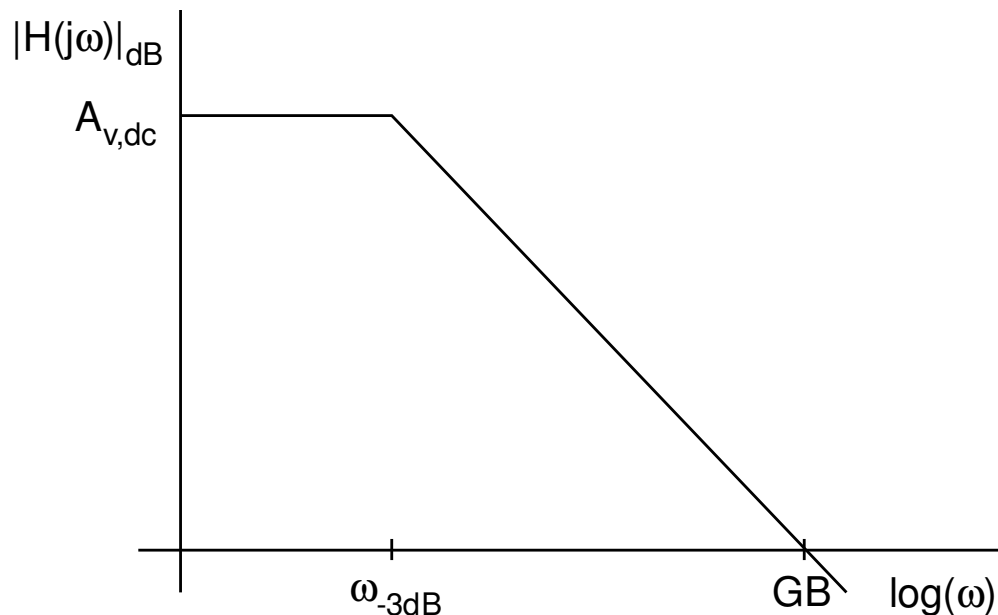- Several poles in an opamp
- Typically, one pole dominates
 - Dominant pole is closest to the origin (Re-Im Plot)
 - Dominant pole has the largest time constant
- Dominant pole is often associated with the output node in an unbuffered opamp
 - Large R_{out} and load capacitance




Gain Bandwidth, GB

$$\begin{aligned} GB &= A_{v,dc} \omega_{-3dB} \\ &= (-G_m R_{out}) \left(\frac{-1}{R_{out} C_{out}} \right) \\ &= \frac{G_m}{C_{out}} \end{aligned}$$

Multiple Poles

- For multi-pole systems, other poles may be close enough to the dominant pole to affect stability
- Typically two poles are of primary concern
- Typically, for a two-stage, unbuffered opamp
 - Pole at output of stage 1
 - Pole at output of stage 2
 - Dominant pole is usually associated with a large load capacitance (i.e. output node)


Multiple Poles

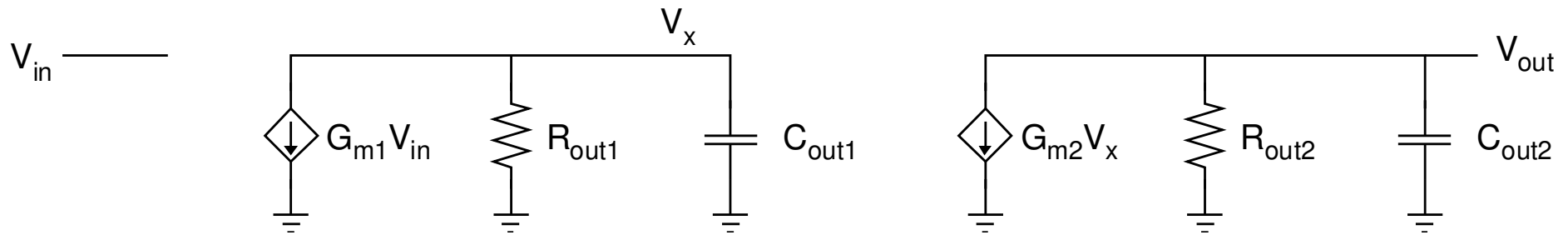

$$p_1 = \frac{-1}{R_1 C_1}$$
$$p_2 = \frac{-1}{R_2 C_2}$$

p_2 typically dominates because of the load capacitance

Multiple Poles

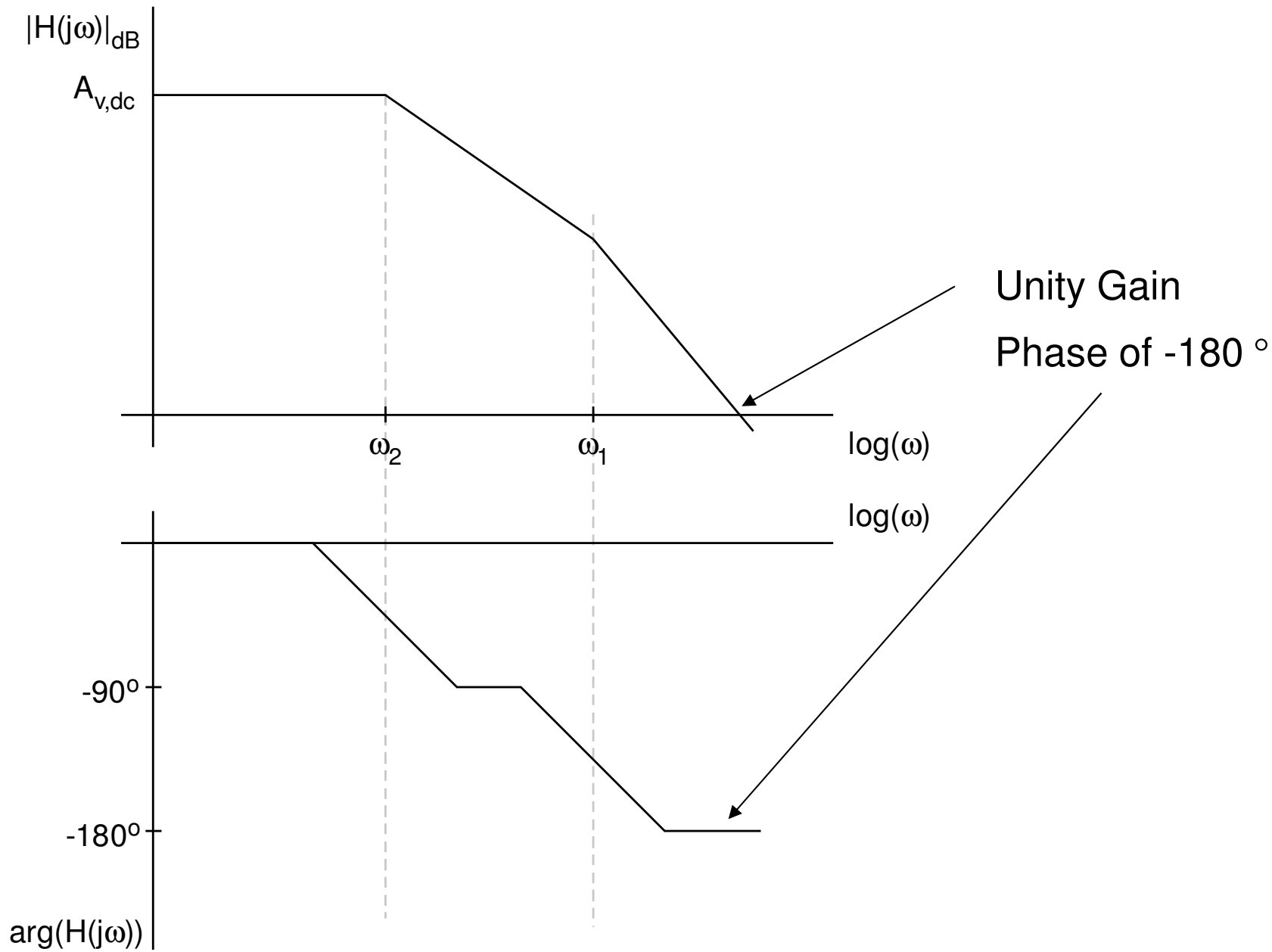

Negative Feedback

In negative feedback configuration, if

$$|H(j\omega)| \geq 1 \text{ and } \angle H(j\omega) = -180^\circ$$

Then, combined with subtraction (-180°) at the input

- Results in -360° phase shift
- This is addition (positive feedback)
 - Since the gain is > 1 at this frequency, the output will grow without bound
 - Therefore, this system is unstable at this frequency
- For stability, must ensure that


$$|H(j\omega)| < 1 \text{ for } \omega \text{ where } \angle H(j\omega) = -180^\circ$$

Phase Margin


- Typically, we like to design to provide a margin of error
 - These conditions (magnitude and phase) can deviate from their designed values due to processes like noise and temperature drift
- Phase margin
 - A measure of how far away from a complete 360° phase shift
 - Phase margin = $180^\circ - \arg(H(j\omega))$
 - Measure at ω where $|H(j\omega)| = 1$
- Typical designs call for Phase margins of greater than 45°
 - Often higher, e.g. $60^\circ - 90^\circ$

Miller Compensation

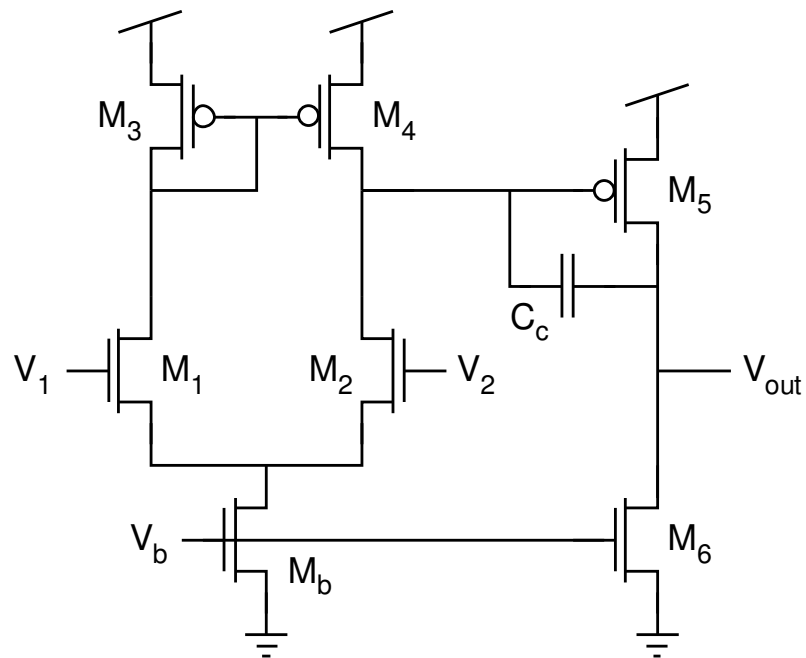- Need to spread the poles apart
- Add a capacitor from input to output of stage 2



Miller Compensation

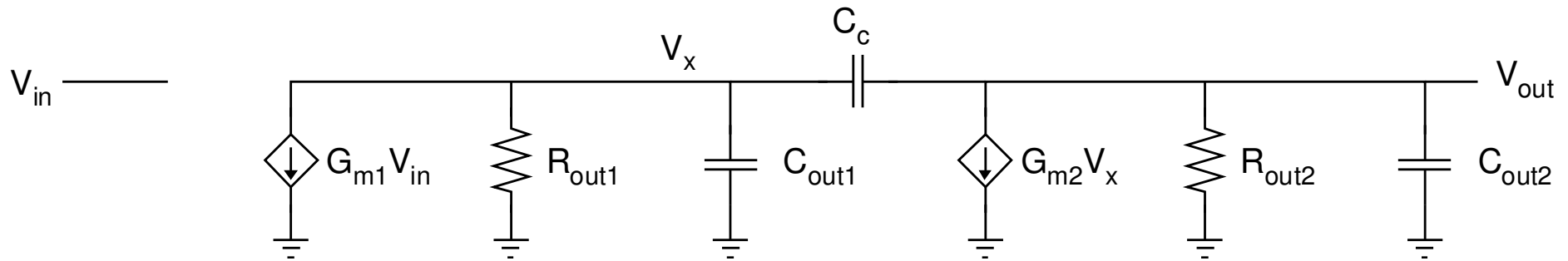


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{G_{m1} G_{m2} R_1 R_2 (1 - s C_2 / G_{m2})}{s^2 R_1 R_2 (C_1 C_2 + C_c C_1 + C_c C_2) + s [R_1 (C_1 + C_c) + R_2 (C_2 + C_c) + G_{m2} R_1 R_2 C_c] + 1}$$

$$p_1 \approx \frac{-1}{G_{m2} R_1 R_2 C_c}$$

$$p_2 \approx \frac{-G_{m2} C_c}{C_1 C_2 + C_2 C_c + C_1 C_c} \approx \frac{-G_{m2}}{C_2}$$

If $C_2 \gg C_1$ and $C_c > C_1$

Miller Compensation

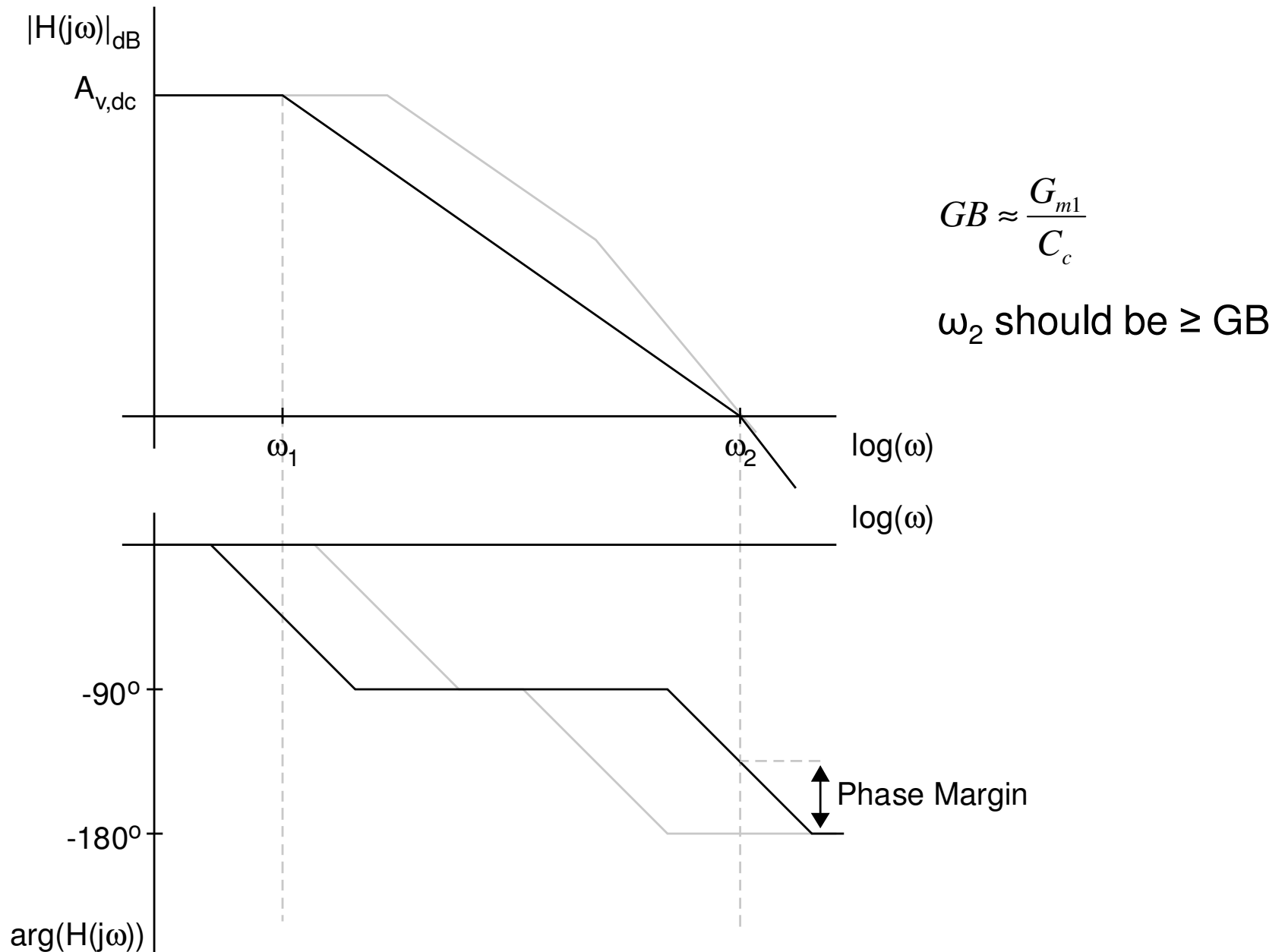

Opamp Comparison

| | Gain | Output Swing | Speed | Power Dissipation | Noise |
|----------------|--------|--------------|---------|-------------------|--------|
| Telescopic | Medium | Medium | Highest | Low | Low |
| Folded-Cascode | Medium | Medium | High | Medium | Medium |
| Two-Stage | High | Highest | Low | Medium | Low |