

# Integrated Circuit Simulation Using SPICE

David W. Graham

Lane Department of Computer Science and Electrical Engineering  
West Virginia University

© David W. Graham 2008

# Why Simulation?

- Theoretical calculations only go so far...
- Find out the circuit behavior in a variety of operating conditions
- It is currently the best way of designing a circuit (industry standard)
- Provides intuitive “feel” for circuit operation (without requiring expensive equipment)

# Simulator Options

Wide variety of circuit simulators

- Specialized simulators (typically discrete-time)
  - Multitude of digital simulators
  - Switcap (for switched-capacitor circuits)
- Generic simulators (analog / continuous-time circuits typically use these)
  - SPICE (Simulation Program with Integrated Circuit Emphasis)

# SPICE Options Available at WVU

- PSPICE
  - Schematic capture
  - Node limitation (9 nodes maximum)
- HSPICE
  - Good
  - Expensive
  - In departmental computer labs with linux machines (e.g. 756 ESB and 813 ESB)
- WinSPICE
  - Free! (Plus, it is good in many other ways)
  - In departmental computer labs with Windows machines (e.g. 813 ESB)

# WinSPICE

## Pros

- Free
- Small Size
- Can run it from MATLAB
- Works well
- No node limitations
- Can use the EKV model (good for subthreshold simulations)
- Works in Windows

## Cons

- No schematic capture (However, Xcircuit can perform schematic capture)
- Only works in Windows
- (Occasional convergence problems – but improving)

# How to Obtain WinSPICE

- Free download
- [www.winspice.com](http://www.winspice.com)
- Go to “Download”
  - Download “Current Full Version”
  - Then, download the current stable release (this is simply an update)

# HSPICE

## Pros

- Industry standard
- Very, very good numerical solver
- Many extra features
  - Incorporation into layout editors (like Cadence)
  - Parameterized sweeps
  - Solid functionality when using libraries
  - Many, many more
- Effectively no node limitations (limitation on the order of 100k nodes)
- Can use the EKV model (good for subthreshold simulations)
- Works in Windows/Linux/Unix

## Cons

- No schematic capture (However, Xcircuit and Cadence can perform schematic capture)
- Expensive
- Only in Linux machines in CSEE department

# HSPICE – How to Use in CSEE Department

- Location
  - Shell server (complete instructions for logging in can be found on the CAD page of the class website)
  - Linux computer labs (756 and 813 ESB)
- Cosmos Scope
  - Waveform viewer
  - Type `cscope` & at the prompt



# Writing SPICE Decks / Netlists

SPICE Deck/Netlist is a text description of a circuit



Consists of the following parts

- Header
- Circuit connections
- Subcircuit descriptions (if needed)
- Model descriptions (if needed – usually only for transistors)
- Analyses to be performed
- Outputs to be saved / displayed

# Basic Circuit Elements

- Resistor `R<label> node1 node2 value`
- Capacitor `C<label> node1 node2 value`
- Inductor `L<label> node1 node2 value`

## Examples

  

R1 1 2 100

Signifies resistor

Resistor "name"

CIN IN OUT 0.1u


Signifies "micro" (1e-6)

Nodes can be signified by words instead of numbers


# Independent Voltage and Current Sources

- Voltage Source    `V<name> n+ n- DC dcvalue AC acvalue`
- Current Source    `I<name> n+ n- DC dcvalue AC acvalue`

## Examples

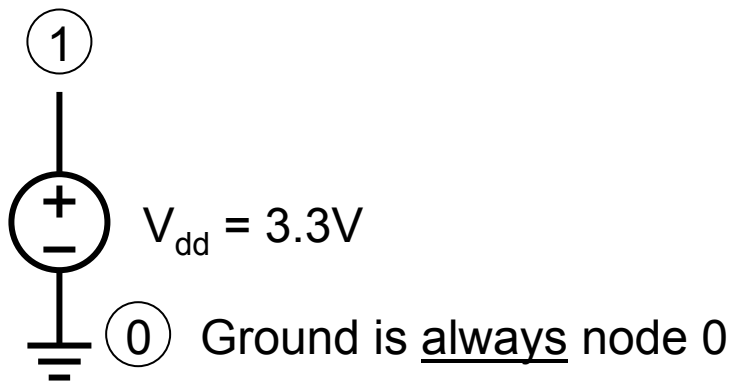


`VDD 1 0 DC 3.3 AC 0`

 

Direction of current flow  
`I1 1 0 DC 1n AC 0.5e-9`

$n = 1e-9$  (equivalent forms)

 

# Independent Voltage and Current Sources

Independent sources can also output functions

- PULSE – Pulse function
- PWL – Piecewise linear function
- SIN – Sinusoidal waveform
- EXP – Exponential waveform
- SFFM – Single-frequency FM

For more information, see the SPICE manual (WinSPICE manual)

Example – Sinusoidal voltage with a DC offset of 1V, an amplitude of 0.5V, and a frequency of 1kHz (between nodes 1 and 0)

```
V<name> n+ n- SIN(dcvalue amplitude frequency)
```

```
V1 1 0 SIN(1 0.5 1k)
```

# Dependent Voltage and Current Sources

- Voltage-controlled voltage source (VCVS)  
`E<label> n+ n- nref+ nref- gain`
- Current-controlled current source (CCCS)  
`F<label> n+ n- voltagesourceref gain`
- Voltage-controlled current source (VCCS)  
`G<label> n+ n- nref+ nref- transconductance`
- Current-controlled voltage source (CCVS)  
`H<label> n+ n- voltagesourceref transconductance`
  
- Voltage-controlled sources reference the voltage across two nodes
- Current-controlled sources reference the current flowing through a voltage source
  - Can be a “dummy” voltage source
  - A voltage source with no voltage supplied
  - `VDUMMY 3 4 DC 0 AC 0`
- Current sources flow from n+ to n-

# Transistors


- nFETs

M<name> drain gate source bulk modelname W=value L=value


- pFETs

M<name> drain gate source well modelname W=value L=value

 **Examples** (Assume models “NFET” and “PFET” are defined elsewhere)



 Assume the bulk connection is tied to ground



M1 2 1 0 0 NFET W=100u L=4.8u

M2 0 1 2 3 PFET W=100u L=4.8u

# Model Files

Two major models for simulating transistors

- BSIM
  - Great for above threshold simulations
  - Essentially empirical fits
  - Many, many parameters (upwards of hundreds)
  - Does not do subthreshold very well, at all
- EKV Model
  - Mathematical model of the MOSFET operation
  - Much fewer parameters
  - Does subthreshold operation very well

# EKV Model

- Enz, Krummenacher, and Vittoz Model
  - (3 Swiss engineers who wanted a better MOSFET model, specifically for low-current applications)
- Model is a “single expression” that preserves continuity of the operation
- Based on the physics of the MOS device (not just empirical fits)
- We will be using the 0.5 $\mu$ m model available at the EKV website
  - [http://legwww.epfl.ch/ekv/ekv26\\_0u5.par](http://legwww.epfl.ch/ekv/ekv26_0u5.par)
- More information can be found at
  - <http://legwww.epfl.ch/ekv/>
  - Liu, et al. pg 86-89
- Level
  - Level = 5 in PSPICE
  - Level = 44 in WinSPICE
  - Level = 55 in HSPICE



# Analysis

Several types of analyses can be performed

- Operating point
- DC sweep
- AC sweep
- Transient analysis
- Additional useful analyses – distortion, noise, pole-zero, sensitivity, temperature, transfer function

We will be making use of these analyses extensively

# Analysis

Analysis declaration is given by a line of code near the end of the SPICE deck

- Operating point analysis (.OP)
  - Provides DC operating point (capacitors shorted, inductors opened)
  - .OP
- DC sweep (.DC)
  - Can sweep a DC voltage or current to determine a DC transfer function
  - .DC sourcename startval stopval incrementval
  - e.g. → .DC VIN 0 5 0.1 (This would sweep source VIN from 0V to 5V with steps of 0.1V)

# Analysis

- AC analysis (.AC)
  - Can sweep an AC voltage or current over a specified frequency range to determine the transfer function / frequency response
  - Does not take distortion and nonlinearities into account
  - `.AC {DEC,OCT,LIN} numpoints freqstart freqstop`
    - DEC – `numpoints` per decade
    - OCT – `numpoints` per octave
    - LIN – linear spacing of points, `numpoints` = total number of points
  - e.g. → `.AC DEC 10 10 1E5`
    - AC sweep from 10Hz to 100kHz, points spaced logarithmically, 10 simulation points per decade
  - Must have a source with an AC component in the circuit

# Analysis

- Transient analysis (.TRAN)
  - Determines the response of a circuit to a transient signal / source (sine wave, PWL function, etc.)
  - Allows you to achieve the most results with a simulation (distortion, nonlinearity, operation, etc.)
  - `.TRAN timestep timestop {timestart {maxstepsize}} {UIC}`
  - Optional arguments
    - `timestart` = start time (default is 0)
    - `maxstepsize` = maximum time increment between simulation points
    - `UIC` – “Use Initial Conditions” – allows the user to define initial conditions for start of simulation, e.g. initial voltage on a capacitor
  - e.g. `→ .TRAN 1n 100n`
    - Perform a transient analysis for 100nsec (100e-9 seconds) with a step increment of 1nsec


# Displaying Outputs

- Saving variables
  - Saving the values of the voltages / currents for use in later plotting them
  - `.SAVE variable1 variable2 ...`
  - Examples
    - `.SAVE V(1)` (Saves the voltage at node 1)
    - `.SAVE VIN VOUT @M1[ID]` (Saves the voltages at nodes VIN and VOUT, also saves the drain current through transistor M1)
    - `.SAVE ALL` (Saves all variables)
  - WinSPICE does not save anything as a default
  - HSPICE saves everything as a default (assuming you use the `.OPTIONS POST` line included)

# Displaying Outputs

- Plotting variables
  - Plot type depends on the analysis performed
  - `.PLOT analysistype variable1 variable2 ...`
  - Examples
    - `.PLOT DC V(1) V(2)` (Plots the voltages at nodes 1 and 2 on the same graph. The x axis is voltage (DC sweep))
    - `.PLOT AC VDB(3)` (Plots the decibel value of the voltage at node 3. The x axis is frequency (AC analysis))
    - `.PLOT TRAN I(VIN)` (Plots the current through the voltage source VIN. The x axis is time (transient analysis))
  - (Must use Cosmos Scope (`cscope`) to view waveforms for HSPICE)

# A Circuit Example

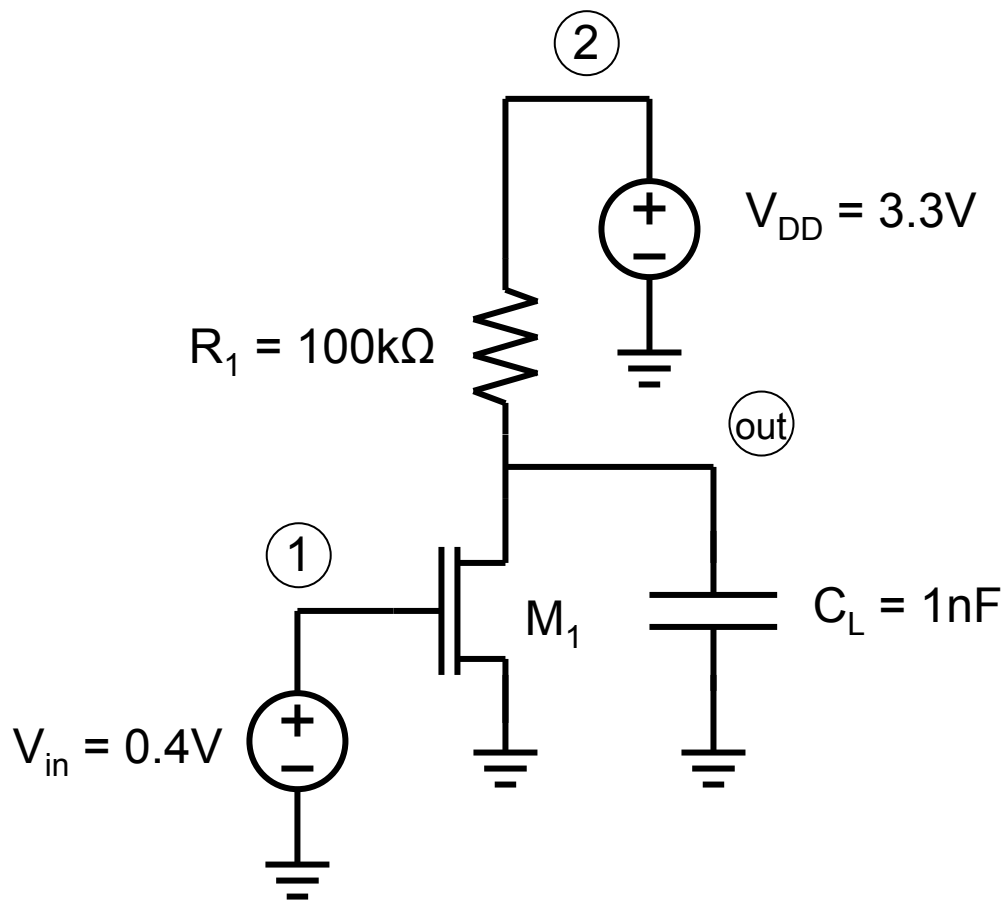

COMMON SOURCE AMPLIFIER

\*BEGIN CIRCUIT DESCRIPTION

```
VIN 1 0 DC 1 AC 0
```

```
VDD 2 0 DC 3.3 AC 0
```

```
R1 OUT 2 100K
```

```
CL OUT 0 1N
```

```
M1 OUT 1 0 0 NFET L=10U
```

```
W=100U
```

<Insert Model Statements Here>

```
.OPTIONS POST ← Only needed for HSPICE
```

```
.OP
```

```
.DC VIN 0 3.3 0.01
```

```
.PLOT DC V(OUT)
```

```
.END
```

# A Circuit Example

Header – First line is always a title / comment

```
COMMON SOURCE AMPLIFIER
```

\* Comments out the entire line

```
*BEGIN CIRCUIT DESCRIPTION
```

```
VIN 1 0 DC 1 AC 0
```

```
VDD 2 0 DC 3.3 AC 0
```

```
R1 OUT 2 100K
```

```
CL OUT 0 1N
```

```
M1 OUT 1 0 0 NFET L=10U
```

```
W=100U
```

```
<Insert Model Statements Here>
```

Only needed for HSPICE (viewing waveforms)

```
.OPTIONS POST ← Only needed for HSPICE
```

Analyses and outputs to be displayed

```
.OP
```

```
.DC VIN 0 3.3 0.01
```

```
.PLOT DC V(OUT)
```

Must end with a .END command

```
.END
```



# WinSPICE – Running a Simulation

- Save your SPICE Deck as a .cir file
- Simply double-click on the file – WinSPICE will automatically run
- As long as WinSPICE is open, every time you save the .cir file, WinSPICE will automatically re-simulate
- The WinSPICE executable must be in a path with no “spaces” in it

# Controlling Simulations with MATLAB

One nice feature of WinSPICE is that it can be controlled from MATLAB. This allows post-processing of the simulation results to be done in the easy-to-use MATLAB environment.

- Download the MATLAB .m file from the class website named `runwinspice.m`
- Place a copy of the WinSPICE executable file (.exe file) in the same directory as your .cir file
- Make sure you save the variables you want to view with the `.SAVE` command (the fewer variables you save, the faster the simulation runs)
- Comment out / remove all lines that display outputs (plots) in the .cir file
- Run the simulation from MATLAB using
  - `[data, names] = runwinspice('mycircuit.cir');`
  - `data`
    - Matrix of all variables that were saved with the `.SAVE` line
    - Each variable is saved as a column
    - In AC analyses, two columns are required for each variable
      - Odd-numbered columns are the real part of the simulation data
      - Even-numbered columns are the imaginary part of the simulation data
  - `names`
    - List of the names of the variables corresponding to each column in “data”
    - In AC analyses, there are half as many “names” as there are columns in “data”

# HSPICE – Running a Simulation

- At the command line in Linux
  - `hspice input_filename.sp > output_filename.lis`
  - Returns `hspice job concluded` at successful completion of simulation
- Many new files will be created. Examples include
  - `filename.tr0` Transient response data
  - `filename.sw0` DC sweep response data
  - `filename.fr0` AC sweep (frequency) response data
- View simulated waveforms with Cosmos Scope
  - Open with `cscope` &
  - Permits viewing of node voltages and currents

# HSPICE MATLAB Toolbox

- For post-processing of simulation data
- Downloadable at <http://www-mtl.mit.edu/researchgroups/perrottgroup/tools.html#hspice>
- Makes output binary files (e.g. sw0, tr0, fr0) readable in MATLAB
- Useful functions
  - `x = loadsig('hspice_output_filename');`  
Reads in simulation data into variable x
  - `lssig(x)`  
Lists all plottable signals (e.g. time, node voltages, currents, etc.)
  - `y = evalsig(x, 'nodename');`  
Writes one particular signal to a variable for postprocessing
  - `plotsig(x, 'plot_expression', 'optional_plotspec')`  
Built-in plot function for viewing signals

# Advanced Features in SPICE

- Subcircuits (for reusable circuit elements)
- Global lines
- “Include” statements
- Many, many more (see the SPICE manual)

# Subcircuits

- Creates a reusable circuit so you do not have to unnecessarily write identical lines of code over and over again
- Has external nodes (for connections)
- Has internal nodes (for the operation of the subcircuit)
- Usage

```
.SUBCKT subcktname extnode1 extnode2 ...  
<Internal circuit connections>  
.ENDS subcktname
```
- Connection to the circuit (Subcircuit calls)

```
X<label> node1 node2 ... subcktname
```

# Subcircuit Example

- Define a subcircuit with the following lines of code

```
.SUBCKT INV 1 2
M1 2 1 3 3 PFET W=1.5 L=1.5U
M2 2 1 0 0 NFET W=1.5 L=1.5U
VSUPPLY 3 0 DC 3.3 AC 0
.ENDS INV
```

- Call the subcircuit `INV` in the circuit declaration part of the `SPICE` deck using the following line

```
X1 8 9 INV
```

Declares this subcircuit will be `INV`

Nodes to connect to in the overall circuit

Subcircuit label "1"

Declares this will be a subcircuit

# Global Lines

- Global nodes are valid in all levels of the circuit, including the subcircuits
- Especially useful for power supplies ( $V_{DD}$ )
- Usage
  - `.GLOBAL node1 node2 ...`



# Include Statements

- Useful for adding large, reusable lines of code
  - Model files
  - Subcircuits
  - Large, specific input signals (PWL)
- Usage
  - `.INCLUDE filename`
  - Effectively replaces the `.INCLUDE` line with the lines of code in the file